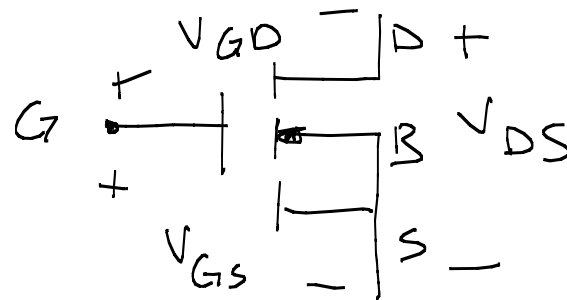


Boundary between Triode and Saturation

$$V_{GD} = V_{to}$$

KVL

$$-V_{GS} + V_{GD} + V_{DS} = 0$$



At the boundary $\Rightarrow V_{GD} = V_{to}$

$$-V_{GS} + V_{to} + V_{DS} = 0$$


$$\boxed{V_{GS} = V_{to} + V_{DS}}$$

Using Saturation Region Equation


$$i_D = K (V_{GS} - V_{to})^2 = K (V_{to} + V_{DS} - V_{to})^2$$

$$\boxed{i_D = K V_{DS}^2}$$

Equation for the boundary

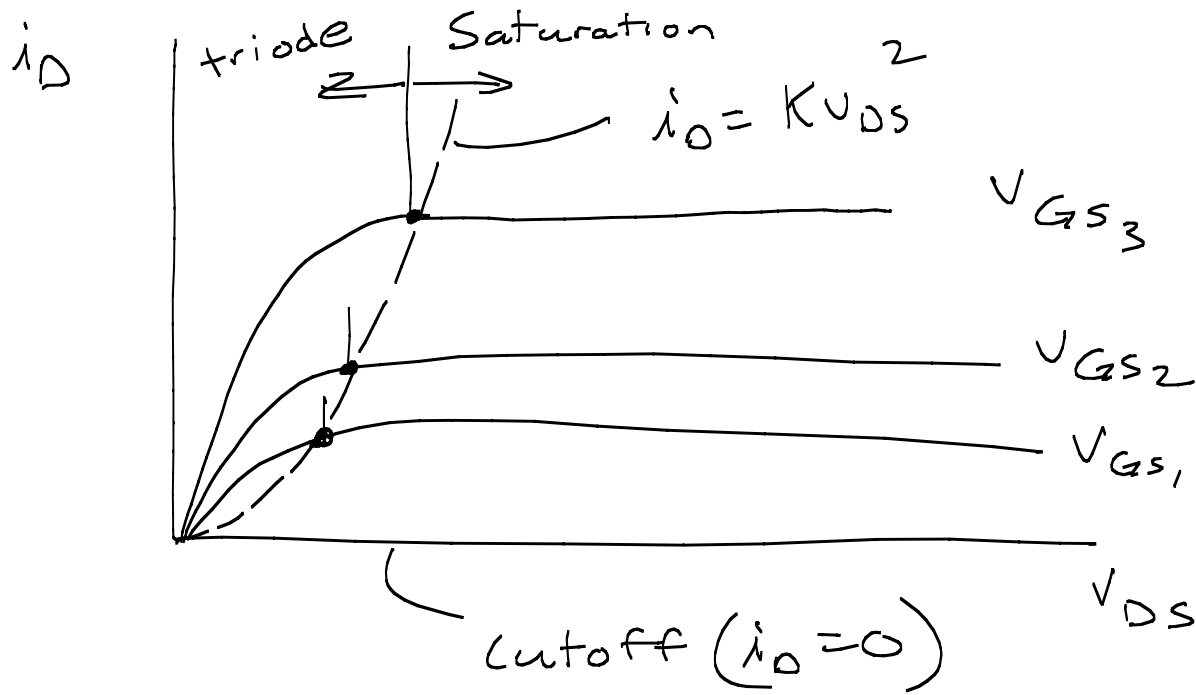

Load-Line Analysis

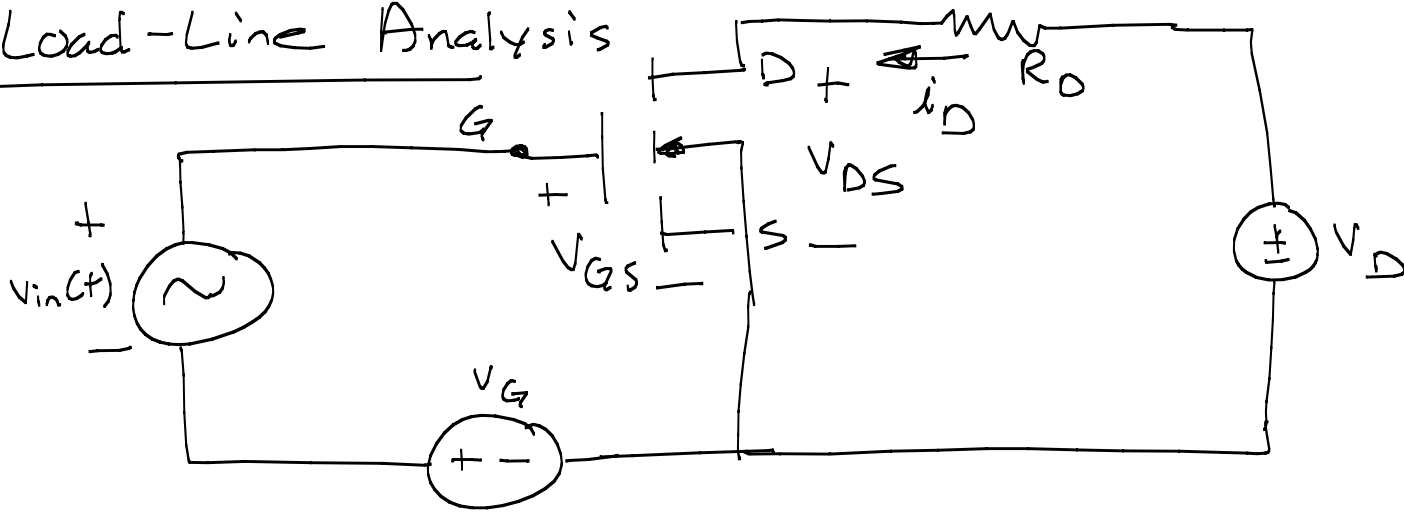

Input

KVL (Left)

$$-V_G - v_{in}(t) + V_{GS} = 0$$


$$V_{GS} = V_G + v_{in}(t)$$

Output

KVL (Right)


$$-V_{DS} - i_D(R_D) + V_D = 0$$

$$V_D = R_D i_D + V_{DS}$$

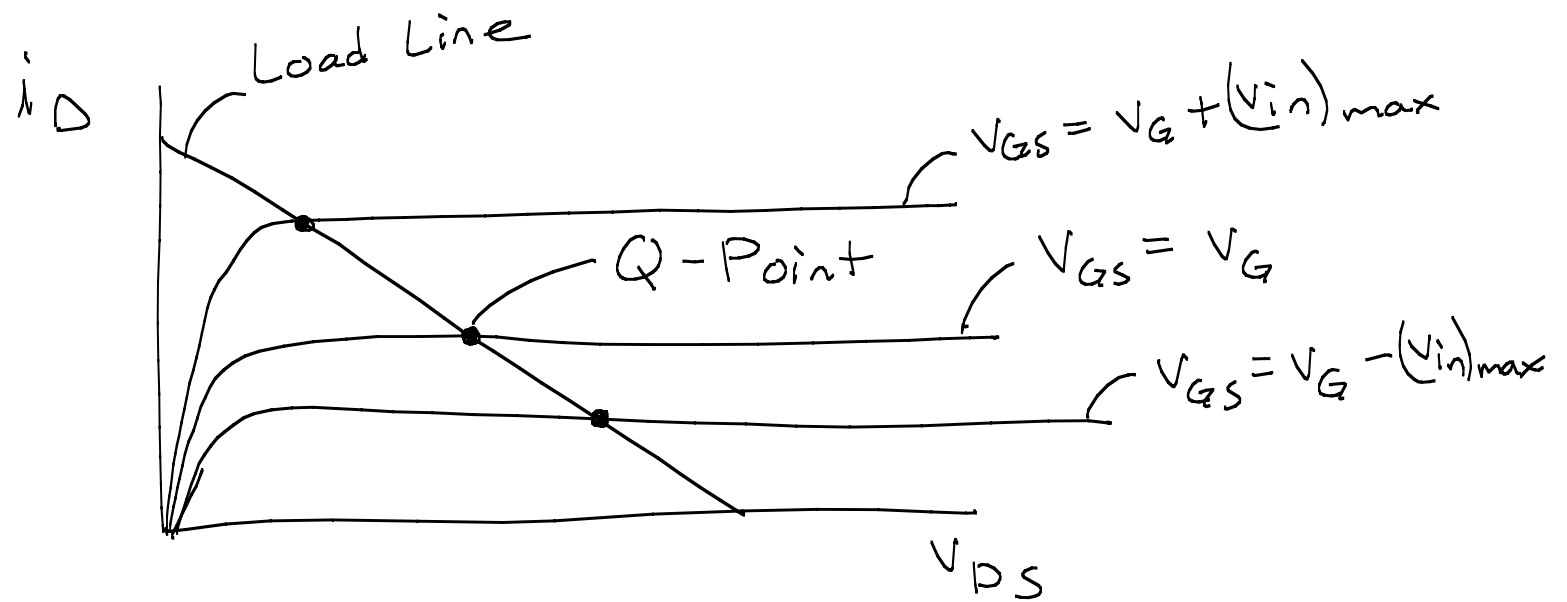

Bias Circuit

Fixed-Plus Self-Bias Circuit

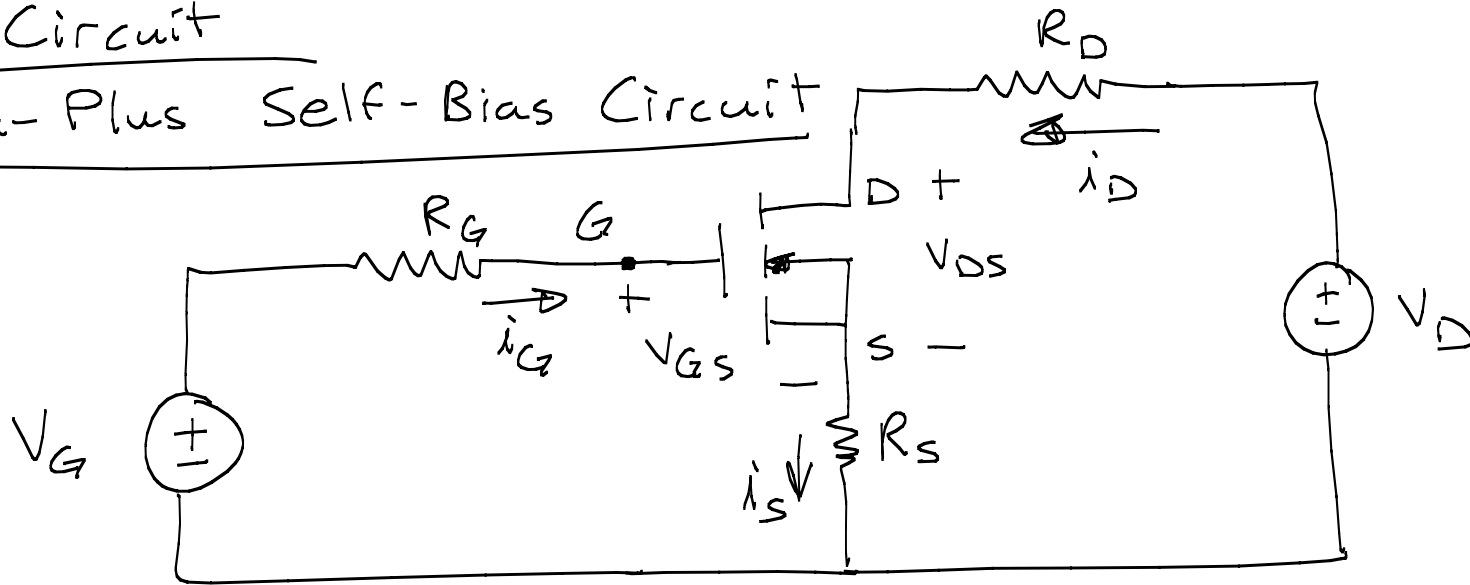

Assume: i_G is small ≈ 0

$$i_D = i_S$$

KVL (Left)

$$-V_G + V_{GS} + i_D R_S = 0$$

$$\boxed{V_G = V_{GS} + i_D R_S} \quad (1)$$


For this circuit, typically want the saturation region

$$i_D = K (V_{GS} - V_{to})^2 \quad (2)$$

Two Equations, Two unknowns (i_D , V_{GS})

\Rightarrow Operating Point

i_D Extraneous Root

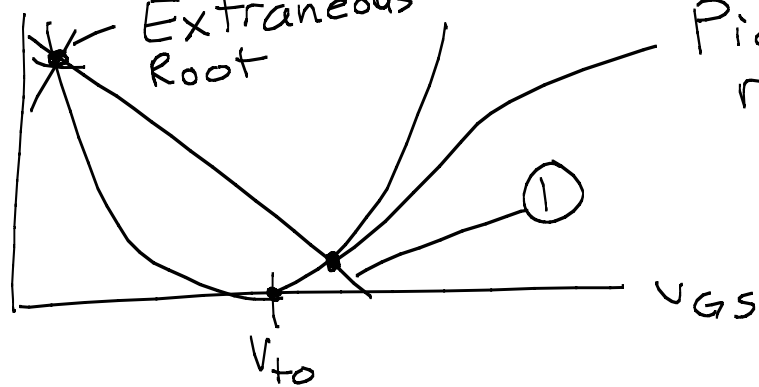

Pick the larger root

KVL (Right)

$$-V_{DS} - i_D R_D + V_D - i_D R_S = 0$$

$$V_{DS} = V_D - i_D (R_S + R_D)$$

Verify Saturation Region

$$V_{GS} > V_{to}$$

$$V_{DS} > V_{GS} - V_{to}$$

Procedure

① Convert the circuit into ^{the} standard model

② KVL (Left) assuming $i_G = 0$

③ ^{Assume} Saturation Region $\Rightarrow i_D = K(V_{GS} - V_{to})^2$

④ Two equations, Two Unknowns \Rightarrow Solve for i_D & V_{GS}

⑤ KVL Right $\Rightarrow V_{DS}$

⑥ Verify Saturation Region

$$V_{GS} > V_{to}, \quad V_{DS} > V_{GS} - V_{to}$$