

CIRCUITS II

Ch 10 Sinusoidal Steady-State Power Calculations

Instantaneous Power



$$P = V_i \text{ amplitude differs}$$

$$\begin{aligned} \text{Let } v &= V_m \cos(\omega t + \theta_v) \\ i &= I_m \cos(\omega t + \theta_i) \end{aligned} \quad \begin{array}{l} \text{phase angle} \\ \text{differs} \end{array}$$

- For steady-state, the reference ^(zero) time ($t=0$) is arbitrary.
- In practice select zero time such that the current is peak

$$(\omega t + \theta_i) = 0 \Rightarrow \omega t \Rightarrow \text{shift by } \theta_i$$

$$i = I_m \cos \omega t$$

$$v = V_m \cos(\omega t + \theta_v - \theta_i)$$

$$P = V_m I_m \cos(\omega t + \theta_v - \theta_i) \cos \omega t$$

Apply trigonometric identities

$$\begin{aligned} P &= \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t \\ &\quad - \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t \end{aligned}$$

or Let $\underline{P} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) \Rightarrow$ average (real) power
units = Watts (W)

$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i) \Rightarrow \text{reactive power}$$

units = volt-amp reactive (VAR)

②

CIRCUITS II

$$p = P + P \cos 2\omega t - Q \sin 2\omega t$$

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} p dt$$

Purely Resistive Circuits

Current and voltage responses possess the same phase angle $\theta_v = \theta_i$

$$Q = 0$$

$$p = P + P \cos 2\omega t$$

Instantaneous real power

$$\text{reactive power} = 0$$

Purely Inductive Circuits

$$\theta_i = \theta_v - 90^\circ \quad \text{or} \quad \theta_v - \theta_i = 90^\circ$$

$$P = 0$$

$$p = -Q \sin 2\omega t$$

$$\text{average power} = 0$$

Purely Capacitive Circuits

$$\theta_i = \theta_v + 90^\circ \quad \theta_v - \theta_i = -90^\circ$$

$$p = Q \sin 2\omega t$$

$$\text{average power} = 0$$

average power \Rightarrow electric energy \Rightarrow thermal energy
reactive power \Rightarrow energy extracted from or stored in electric fields

③


CIRCUITS IIPower Factor

power factor angle = $\theta_v - \theta_i$
 - influences the average and reactive power computations

power factor (pf) $\Rightarrow \cos(\theta_v - \theta_i)$
 reactive factor (rf) $\Rightarrow \sin(\theta_v - \theta_i)$

Drill Exercise 10.1

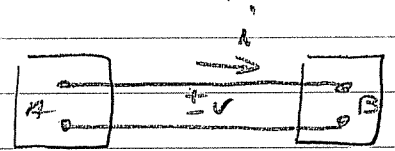Calculate - average & reactive power
 - Indicate power flow




(a) $v = 100 \cos(\omega t - 45^\circ) \text{ V}$, $i = 20 \cos(\omega t + 15^\circ) \text{ A}$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$= \frac{(100\text{V})(20\text{A})}{2} \cos(-45^\circ - 15^\circ)$$
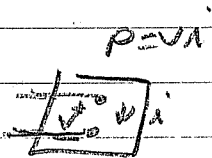
$$P = 500 \text{ W} \quad (P = v i) \\ (A \text{ to } B)$$



$$Q = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

$$Q = \frac{(100\text{V})(20\text{A})}{2} \sin(-45^\circ - 15^\circ)$$


$$Q = -866 \text{ VAR} \quad (B \text{ to } A)$$

(b) $v = 100 \cos(\omega t - 45^\circ) \text{ V}$, $i = 20 \cos(\omega t + 165^\circ) \text{ A}$

$$P = \frac{(100\text{V})(20\text{A})}{2} \cos(-45^\circ + 165^\circ) = -866 \text{ W} \quad (B \text{ to } A)$$

$$Q = \frac{(100\text{V})(20\text{A})}{2} \sin(-45^\circ - 165^\circ) = 500 \text{ VAR} \quad (A \text{ to } B)$$

(4)

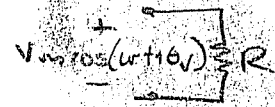CIRCUITS IIRMS Values and Power Calculations

Use $V_{rms}(V_{eff})$ and $I_{rms}(I_{eff})$ instead of V_m and I_m from before for

$$V_{eff} = \frac{V_m}{\sqrt{2}} \quad , \quad I_{eff} = \frac{I_m}{\sqrt{2}}$$

$$P = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) = \frac{V_m I_m}{\sqrt{2} \sqrt{2}} \cos(\theta_v - \theta_i)$$

$$\boxed{P = V_{eff} I_{eff} \cos(\theta_v - \theta_i)}$$


Similarly

$$\boxed{Q = V_{eff} I_{eff} \sin(\theta_v - \theta_i)}$$

Complex Power

Complex power = (S) sum of the real power and the complex power

$$S = P + jQ \quad \text{Units Volt-Amps (VA)}$$

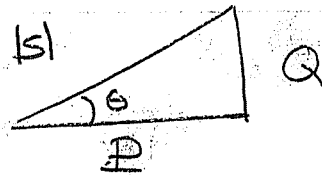Power Triangle

$$|S| = \sqrt{P^2 + Q^2} \Rightarrow \text{Apparent Power}$$

$$\tan \theta = \frac{Q}{P} = \frac{(V_m I_m / 2) \sin(\theta_v - \theta_i)}{(V_m I_m / 2) \cos(\theta_v - \theta_i)} = \tan(\theta_v - \theta_i)$$

5

CIRCUITS II

$$S = P + jQ = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i) + j \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

$$= \frac{V_m I_m}{2} (\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i))$$

$$S = \frac{1}{2} V_m I_m \angle (\theta_v - \theta_i)$$

For rms values

$$S = V_{\text{eff}} I_{\text{eff}} \angle (\theta_v - \theta_i)$$

$$S = V_{\text{eff}} I_{\text{eff}} e^{j(\theta_v - \theta_i)}$$

$$= \underbrace{V_{\text{eff}} e^{j\theta_v}}_{V_{\text{eff}}} \underbrace{I_{\text{eff}} e^{-j\theta_i}}_{I_{\text{eff}}^*}$$

due to minus sign

Note: $\cos(-\theta) = \cos \theta$ $\sin(-\theta) = -\sin \theta$

$$S = V_{\text{eff}} I_{\text{eff}}^*$$

Could do the same for I_m and V_m

$$S = \frac{1}{2} V_m I_m e^{j(\theta_v - \theta_i)}$$

$$= \frac{1}{2} \underbrace{(V_m e^{j\theta_v})}_{V} \underbrace{(I_m e^{-j\theta_i})}_{I^*}$$

$$S = \frac{1}{2} V I^*$$

6

CIRCUITS II

Alternate Forms of Complex Power From Phasors

$$V_{eff} = Z I_{eff}$$

$$S = \bar{V}_{eff} I_{eff}^*$$

$$= Z \underbrace{I_{eff} I_{eff}^*}_{|I_{eff}|^2}$$

$Z = (R + jX)$ reactance for inductor or capacitor

$$S = |I_{eff}|^2 (R + jX)$$

$$= \underbrace{|I_{eff}|^2 R}_P + j \underbrace{|I_{eff}|^2 X}_Q$$

$$P = |I_{eff}|^2 R = \frac{1}{2} I_m^2 R$$
$$Q = |I_{eff}|^2 X = \frac{1}{2} I_m^2 X$$


Could also use voltages

$$P = \frac{|V_{eff}|^2}{R}$$

$$Q = \frac{|V_{eff}|^2}{X}$$

*** Example 10.5

①
Example 10.5

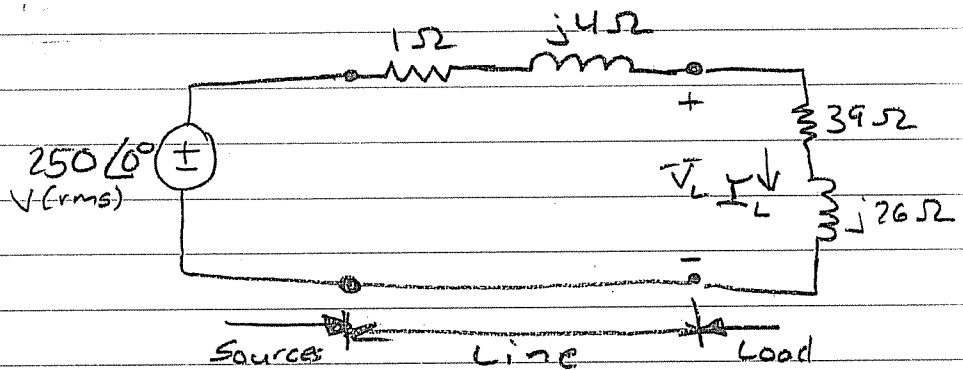

(a) Find V_L & I_L

$$I_L = \frac{250 \angle 0^\circ}{40 \Omega + j30 \Omega - j22} = \frac{250 \angle 0^\circ}{50 \angle 36.87^\circ} = \boxed{5 \angle -36.87^\circ \text{ A (rms)}}$$

$$V_L = (I_L)(39 + j26) = (5 \angle -36.87^\circ \text{ A})(46.81 \angle 33.69^\circ \Omega)$$

$$\boxed{V_L = 234.36 \angle -3.18^\circ \text{ V (rms)}}$$

(b) Find the average and reactive power delivered to the load

$$P = V_L I_L^*$$

$$I_L = 5 \angle -36.87^\circ = 4 - j3 \text{ A (rms)}$$

$$I_L^* = 4 + j3 = 5 \angle 36.87^\circ \text{ A (rms)}$$

$$S = [(234.36) \angle -3.18^\circ] [5 \angle 36.87^\circ]$$

$$S = 1171.8 \angle 33.7^\circ \text{ VA}$$

$$\boxed{S = 975 + j650 \text{ VA}}$$

$$\boxed{P = 975 \text{ W}}$$

$$\boxed{Q = 650 \text{ VAR}}$$

②

Example 10.5

Calculate the average and reactive power delivered to the ~~load~~.

$$(c) \quad P = |I_{eff}|^2 R \\ = (5)^2 (1 \Omega) = \underline{25 \text{ W}}$$

$$Q = |I_{eff}|^2 X \\ = (5)^2 (4) = \underline{100 \text{ VAR}}$$

$$\boxed{S = 25 + j100 \text{ VA}}$$

(d) Calculate the average and reactive power delivered by the source.
delivered

$$S = - (975 + j650 + 25 + j100)$$

$$\boxed{S = - (1000 + j750) \text{ VA}}$$