

Chapter 13: Laplace Transform in Circuit Analysis

Circuit Elements in the s Domain


$f(t) \Rightarrow$ time domain $v(t), i(t)$
 $F(s) \Rightarrow$ s-Domain $V(s), I(s)$
 $V = \mathcal{L}\{v\}, I = \mathcal{L}\{i\}$

Steps


- 1) Write the time-domain equation relating voltage to current for the element
 \Rightarrow s-domain current to voltage relation
- 2) Construct a circuit model that satisfies the s-domain current to voltage relation

Note: voltage in time-domain \Rightarrow volts, s-domain, volt-sec

Resistor in the s Domain

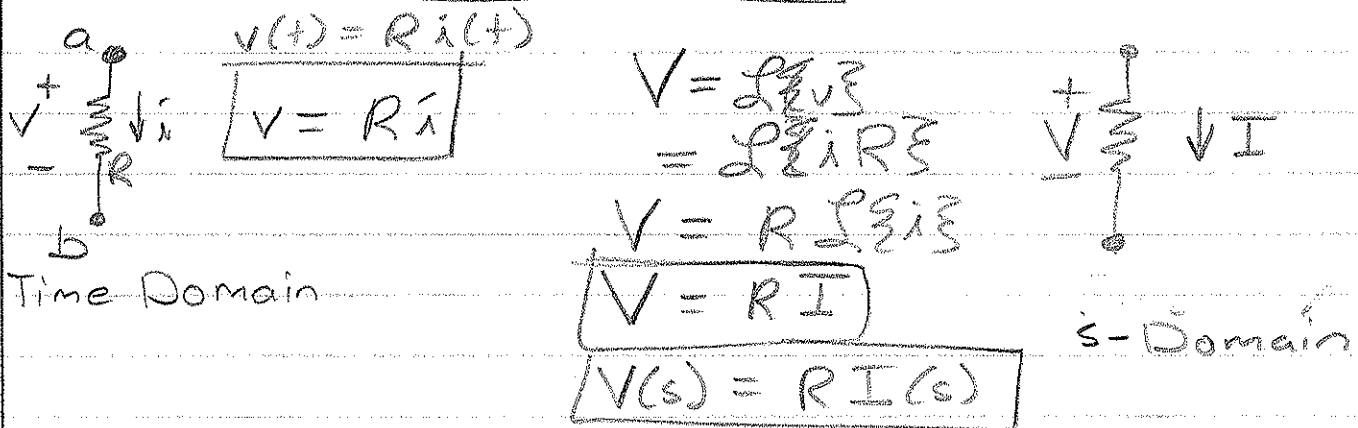

Inductor in the s Domain

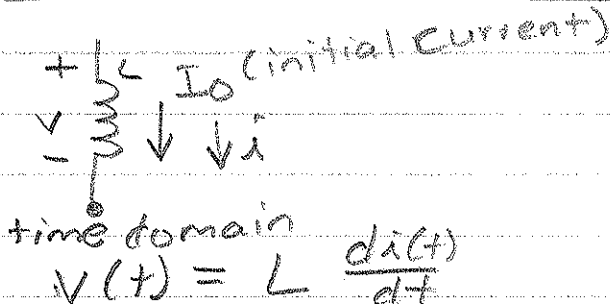

$V(s) = L [s I(s) - i(0^-)]$


$V(s) = s L I(s) - L I_0$ or $V = s L I - L I_0$

29


CIRCUITS II

Circuit Model

Series

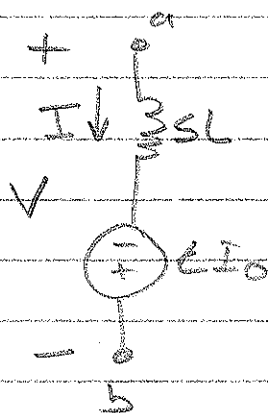


Parallel Model

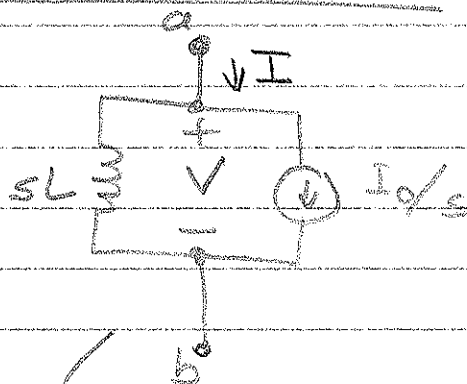

$$I = \frac{V + LI_0}{sL} = \frac{V}{sL} + \frac{I_0}{s}$$

Capacitor in the s Domain

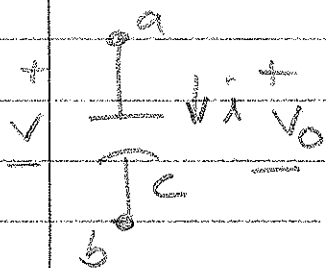

$$i = C \frac{dv}{dt}$$

$$I = C [sV - v(0^-)]$$

$$I = sCV - v(0^-)$$

$$V = \frac{1}{C} \int_{0^-}^+ i d\tau + V_0$$

$$= \frac{1}{C} \left[\frac{I(s)}{s} \right] + \frac{V_0}{s}$$

$$V = \frac{I}{sC} + \frac{V_0}{s}$$

30

CIRCUITS II

Circuit Analysis in the s Domain

$$V = ZI \quad (\text{Assuming no initial energy is stored in the inductor or capacitor})$$

$Z \Rightarrow$ s domain impedance

Resistor $\Rightarrow R$ ohms

Inductor $\Rightarrow sL$ ohms

Capacitor $\Rightarrow 1/sC$ ohms


Rules for s-domain impedances are the same as for the frequency domain impedances

- Series to parallel
- Δ - Y transformation
- KVL, KCL

Drill Exercise 13.1

①

Drill Exercise 13.1

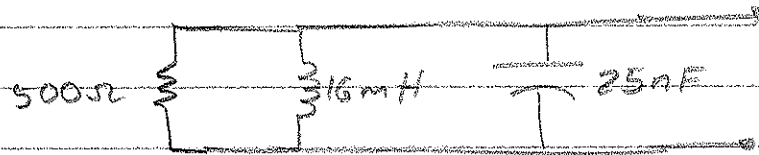

(a) Express the admittance of this parallel combination as a rational function of s

$$Y = \frac{1}{Z} \quad Y_{eq} = \frac{1}{Z_{eq}}$$

$$Y = \frac{1}{R} + \frac{1}{sL} + sC$$

$$= C \left[\frac{1}{s} \left(s^2 + \frac{1}{RC} s + \frac{1}{LC} \right) \right]$$

$$Y = \frac{C \left[s^2 + \left(\frac{1}{RC} \right) s + \left(\frac{1}{LC} \right) \right]}{s}$$

$$\frac{1}{RC} = \frac{1}{(500)(25 \times 10^{-9})} = 80,000$$


$$\frac{1}{LC} = \frac{1}{(16 \times 10^{-3})(25 \times 10^{-9})} = 25 \times 10^8$$

$$Y = \frac{25 \times 10^{-9} (s^2 + 80,000s + 25 \times 10^8)}{s}$$

31

CIRCUITS II

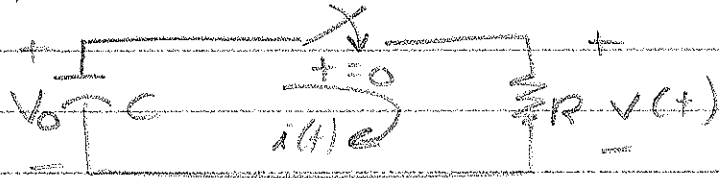Circuit Applications of the Laplace Transform
Natural Response of an RC Circuit



KVL

$$-V_c(t) + v(t) = 0$$

$$-\left(\frac{1}{C} \int_0^t i(\tau) d\tau + V_0\right) + i(t)R = 0$$

s-Domain

$$-\left(\frac{-I(s)}{sC} + \frac{V_0}{s}\right) + I(s)R = 0$$

$$I(s) \left(\frac{1}{sC} + R\right) = \frac{V_0}{s}$$

$$I(s) (1 + sRC) = V_0 C$$

$$I(s) = \frac{V_0 C}{(1 + sRC)} = \frac{V_0 C}{RC \left(\frac{1}{RC} + s\right)}$$



$$I(s) = \frac{V_0/R}{(s + 1/RC)}$$

$$i(t) = \frac{V_0}{R} e^{-t/RC} u(t)$$

$$v = Ri = V_0 e^{-t/RC} u(t)$$

Could also use the s-domain equivalent

Capacitor

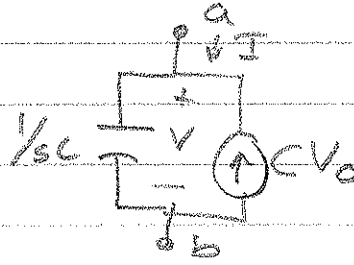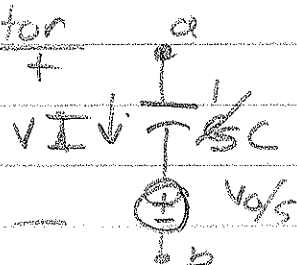


$$\frac{1}{sC} I(s) - \frac{V_0}{s} + RI = 0$$

$$V = \frac{I}{sC} + \frac{V_0}{s}$$


Drill Exercise 13.4

①

Drill Exercise 13.4

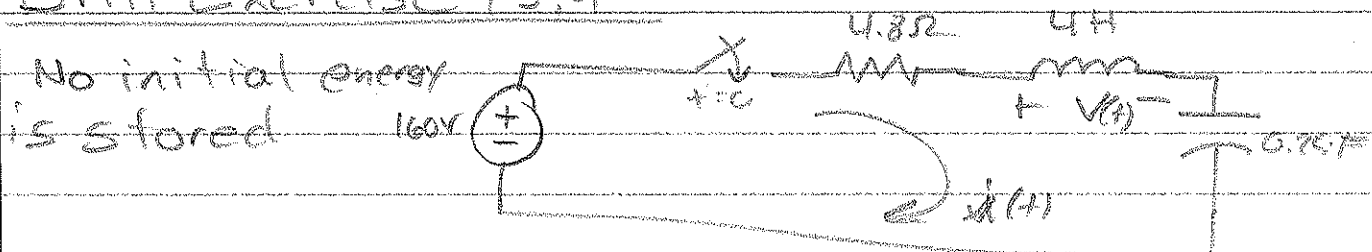

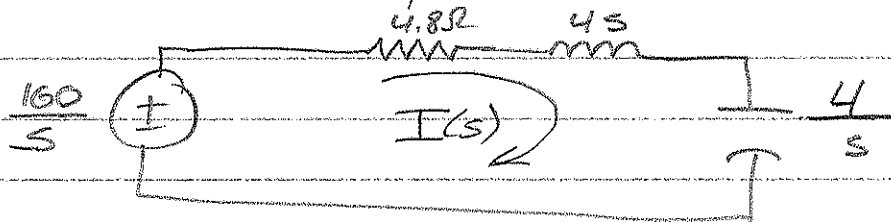(a) Find the s -domain expression for I
 s -domain



$$\frac{160}{s} = 4.8 I(s) + 4s I(s) + \frac{4}{s} I(s)$$

$$160 = 4.8s I(s) + 4s^2 I(s) + 4 I(s)$$

$$I(s) = \frac{160}{4s^2 + 4.8s + 4}$$

$$I(s) = \frac{40}{s^2 + 1.2s + 1}$$

(b) Find $i(t)$

$$s = \frac{-1.2 \pm \sqrt{(1.2)^2 - (4)(1)}}{2} = -0.6 \pm j0.8$$

$$\frac{40}{s^2 + 1.2s + 1} = \frac{K}{s + 0.6 - j0.8} + \frac{K^*}{s + 0.6 + j0.8}$$

$$K = \frac{40}{(s + 0.6 - j0.8)(s + 0.6 + j0.8)} \Big|_{s = -0.6 + j0.8} = \frac{40}{j1.6}$$

$$K = -j25 = 25 \angle -90^\circ \quad K^* = 25 \angle 90^\circ$$

$$i(t) = 2(25) e^{-0.6t} \cos(0.8t - 90^\circ) \text{ uA} \quad \text{A}$$

$$i(t) = 50 e^{-0.6t} \sin(0.8t) \text{ uA} \quad \text{A}$$

②

Drill Exercise 13.4

(c) Find $V(s)$

$$V(s) = Z I(s)$$

$$V(s) = \frac{(4s)(40)}{s^2 + 1.2s + 1}$$

$$V(s) = \frac{160s}{s^2 + 1.2s + 1}$$

(d) Find $v(t)$

$$\frac{160s}{(s+0.6-j0.8)(s+0.6+j0.8)} = \frac{K}{s+0.6-j0.8} + \frac{K^*}{s+0.6+j0.8}$$

$$K = \frac{160s}{\cancel{(s+0.6-j0.8)}(s+0.6+j0.8)} \Big|_{s=0.6+j0.8}$$

$$= \frac{160(-0.6+j0.8)}{j1.6} = \frac{-160(-j0.6-0.8)}{1.6}$$

$$K = 80 + j60 = 100 \angle 36.87^\circ$$


$$v(t) = 2(100) e^{-0.6t} \cos(0.8t + 36.87^\circ) u(t) \text{ V}$$

$$v(t) = [200 e^{-0.6t} \cos(0.8t + 36.87^\circ)] u(t) \text{ V}$$


32

CIRCUITS II

Multiple Mesh Circuit

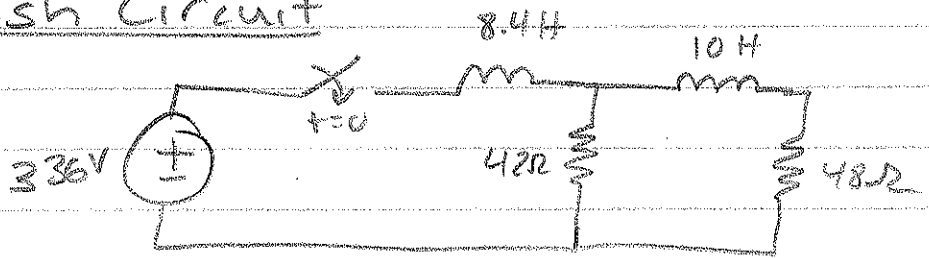

S-Domain

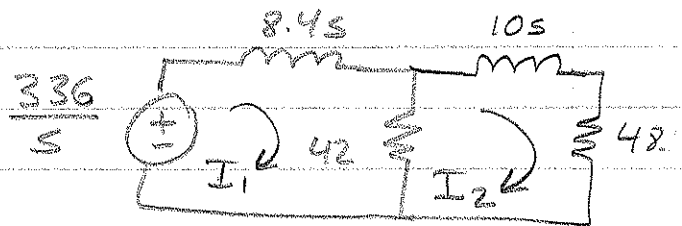

Mesh Current

$$-\frac{336}{s} + 8.4sI_1 + 42(I_1 - I_2) = 0$$

$$10sI_2 + 48I_2 + 42(I_2 - I_1) = 0$$

$$(42 + 8.4s)I_1 - 42I_2 = \frac{336}{s}$$

$$-42I_1 + (90 + 10s)I_2 = 0$$

Cramer's Method

$$\Delta = \begin{vmatrix} 42 + 8.4s & -42 \\ -42 & 90 + 10s \end{vmatrix}$$

$$= (42 + 8.4s)(90 + 10s) - (-42)(-42)$$

$$= 3780 + 1176s + 84s^2 - 1764$$

$$= 84[s^2 + 14s + 24]$$

$$\Delta = 84(s+2)(s+12)$$

$$N_1 = \begin{vmatrix} 336/s & -42 \\ 0 & 90 + 10s \end{vmatrix} = \frac{336}{s}(90 + 10s)$$

$$N_1 = \frac{3360(s+9)}{s}$$

33

CIRCUITS II

$$N_2 = \begin{vmatrix} 42 + 8.4s & 336/s \\ -42 & 0 \end{vmatrix} = \frac{14,112}{s}$$

$$I_1 = \frac{N_1}{\Delta} = \frac{3360(s+9)}{s} \left(\frac{1}{84(s+2)(s+12)} \right)$$

$$I_1 = \frac{40(s+9)}{s(s+2)(s+12)}$$

$$I_2 = \frac{N_2}{\Delta} = \frac{14,112}{s} \left(\frac{1}{84(s+2)(s+12)} \right)$$

$$I_2 = \frac{168}{s(s+2)(s+12)}$$

34

CIRCUITS II



The Transfer Function

Transfer Function $H(s) = \frac{Y(s)}{X(s)}$ (Assume all initial conditions are zero)

$H(s) \Rightarrow$ Transfer Function

$Y(s) \Rightarrow$ Laplace Transform of the output (response)

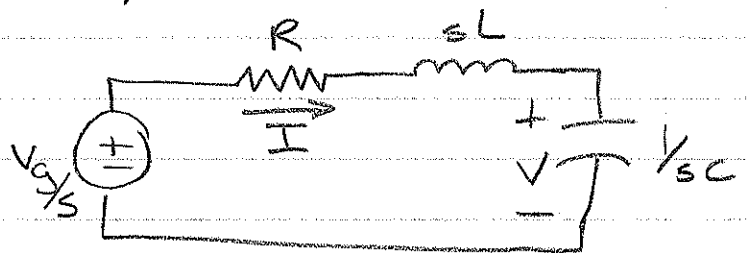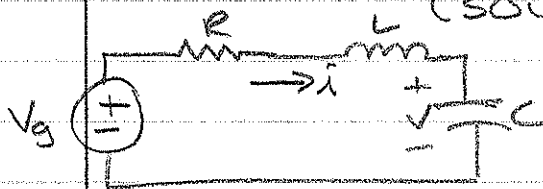$X(s) \Rightarrow$ Laplace Transform of the input (source)



Transfer Function for the current

$$I(s) = \frac{V_g/s}{R + sL + 1/sC}$$

$$V_g(s) = \frac{V_g}{s}$$

$$H(s) = \frac{I(s)}{V_g(s)} = \frac{(V_g/s)}{(V_g/s)(R + sL + 1/sC)} = \frac{1}{R + sL + 1/sC} = \frac{sC}{s^2LC + RCs + 1}$$

Transfer Function for V

$$V(s) = I \left(\frac{1}{sC} \right) = \frac{V_g/s^2C}{R + sL + 1/sC}$$


$$H(s) = \frac{V(s)}{V_g(s)} = \frac{(V_g/s)(1/sC)}{(V_g/s)(R + sL + 1/sC)} = \frac{(1/sC)}{(1/sC)(s^2LC + RCs + 1)}$$

$$H(s) = \frac{1}{s^2LC + RCs + 1}$$


Drill Exercise 13.9

①

Drill Exercise 13.9

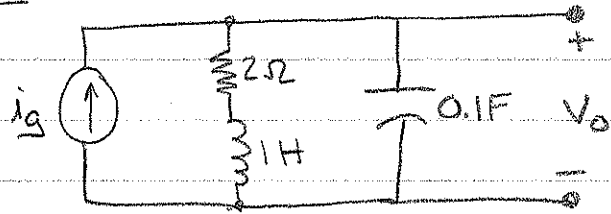

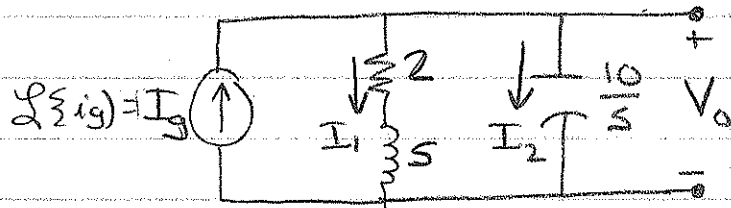(a) Derive the numerical expression for the transfer function V_o/I_g



$$I_g = I_1 + I_2$$

$$I_g = \frac{V_o}{s+2} + \frac{V_o}{10/s}$$

$$V_o \left(\frac{s}{10} + \frac{1}{s+2} \right) = I_g$$

$$H(s) = \frac{V_o}{I_g} = \frac{1}{\left(\frac{s}{10} + \frac{1}{s+2} \right)} = \frac{10(s+2)}{s(s+2) + 10}$$

$$H(s) = \frac{10(s+2)}{s^2 + 2s + 10}$$


(b) Find the numerical value of each pole and the zero of $H(s)$

zeros \Rightarrow value of s that makes $H(s) = 0$
 $= -2$


poles \Rightarrow value of s that makes $H(s) \rightarrow \infty$

$$s = \frac{-2 \pm \sqrt{4 - 40}}{2} = -1 \pm j3$$


Alternating Current

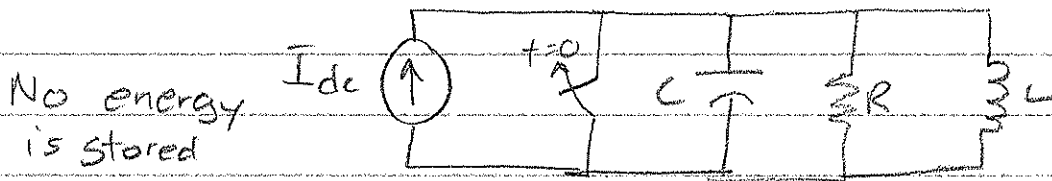


s-domain

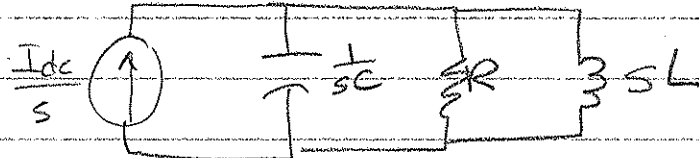

Alternating Current

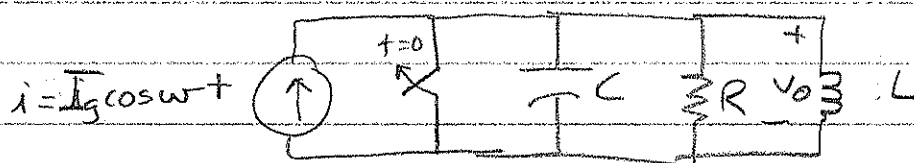

s-Domain

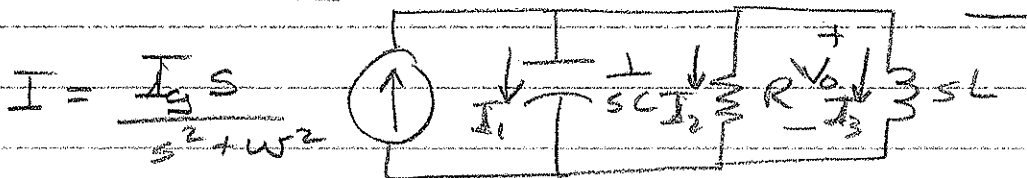

$$I = I_1 + I_2 + I_3$$

$$\frac{I_g s}{s^2 + \omega^2} = \frac{V_o}{1/sC} + \frac{V_o}{R} + \frac{V_o}{sL}$$

Simplify & take the inverse Laplace Transform

Two terms \Rightarrow transient + steady-state

(13.7) Transfer Function in Steady-state Sinusoidal Response

Can use the transfer function to get the ^{steady-state} sinusoidal response of a circuit

Given

Source $x(t) = A \cos(\omega t + \phi)$


$H(s)$

Evaluate $H(s)$ at $j\omega$

$$H(j\omega) = |H(j\omega)| \angle \theta(\omega)^\circ$$

$$y_{ss}(t) = A / |H(j\omega)| \cos[\omega t + \phi + \theta(\omega)]$$

Example 13.4

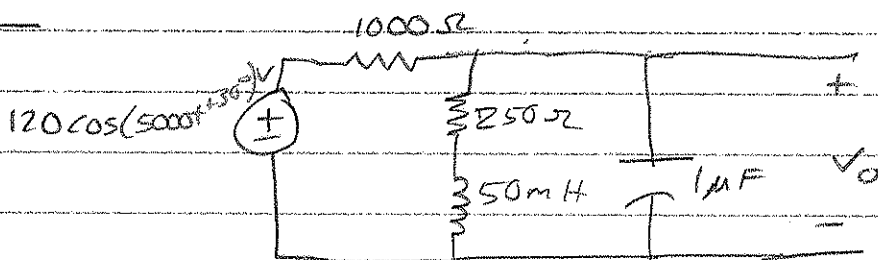

Transfer

Function for $v_o \Rightarrow H(s) = \frac{1000(s+5000)}{s^2 + 6000s + 25 \times 10^6}$

Find $v_o(t)$ (steady-state)

$$\begin{aligned}
 H(j\omega) &= H(j5000) = \frac{1000(j5000 + 5000)}{(j5000)^2 + (6000)(j5000) + 25 \times 10^6} \\
 &= \frac{1+j1}{j6} = \frac{1}{6} - j\frac{1}{6} = \frac{\sqrt{2}}{6} \angle -45^\circ
 \end{aligned}$$

$$v_{o,ss}(t) = (120) \left(\frac{\sqrt{2}}{6} \right) \cos(5000t + 30^\circ + (-45^\circ)) \text{ V}$$

$$v_{o,ss}(t) = 20\sqrt{2} \cos(5000t - 15^\circ) \text{ V}$$