


Chapter 14: Frequency Selective Circuits

Sinusoidal Sources \Rightarrow Frequency was held constant


Frequency Response: Analysis of the effect of varying the source frequency

In circuit elements, varying the frequency will affect the impedance of inductors and capacitors.

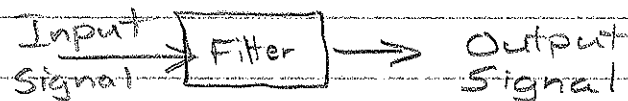Frequency Selective Circuits (Filters) \Rightarrow circuits that pass to output only input signals within a certain frequency range



Filters weaken or lessen the effect (attenuate) of signals with frequencies outside a frequency band
- Example (Graphic equalizer)

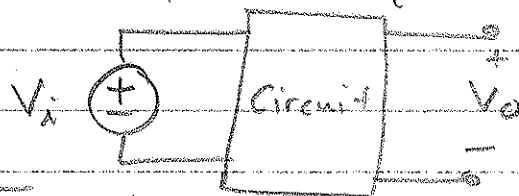Transfer Function

From before, Fixed-Frequency sources
Replace with a varying-Frequency source

$$H(s) = \frac{V_o(s)}{V_i(s)}$$

Frequency Bands


- Pass band => band of frequencies where signals from the input are passed to the output

Inputs outside this band are attenuated


- Stop Band => Frequencies not in the pass band

Cutoff Frequency =>

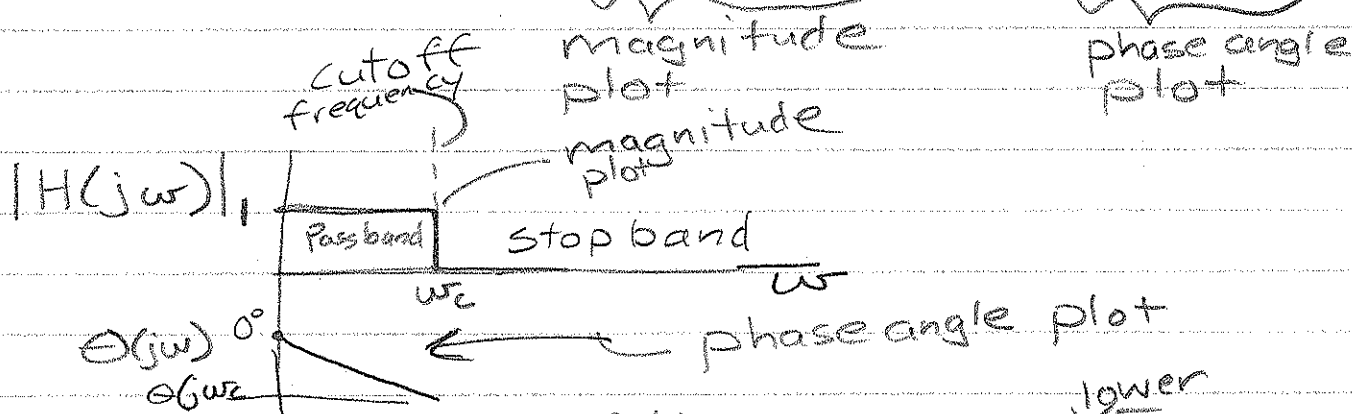Frequency Response Plot - shows how a circuit's transfer function changes as the source frequency changes => shows both magnitude and phase




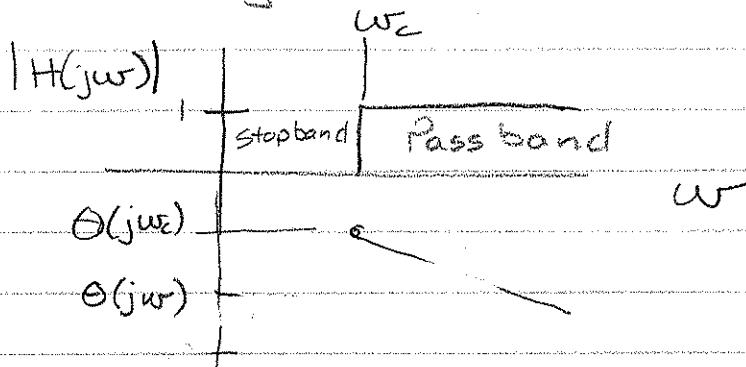Ideal low-pass filter => passes ^{lower} Frequency signals than the cutoff frequency




Ideal High-pass filter => passes signals at a higher frequency

CIRCUITS II

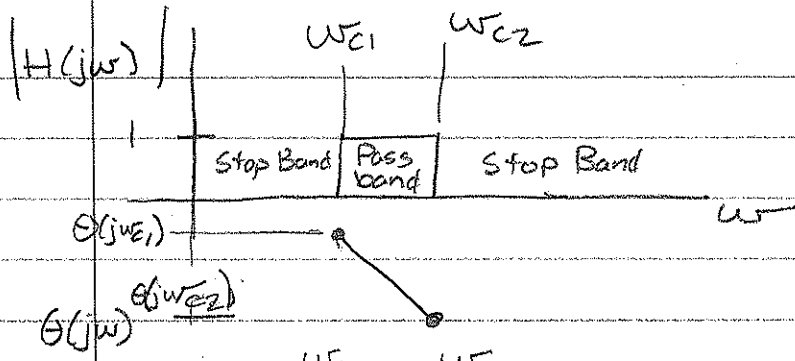

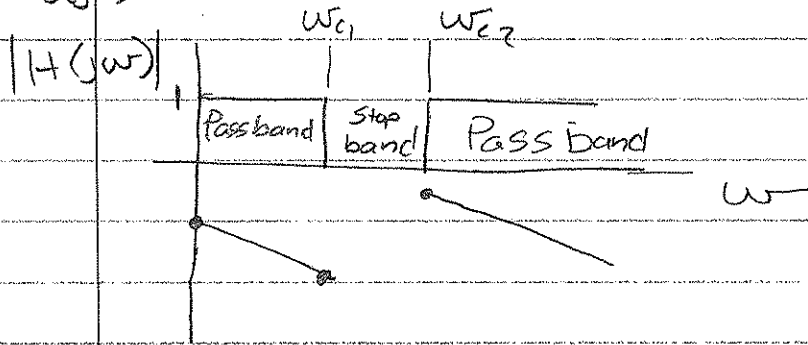Ideal Band-pass filter
=> passes signals within
a frequency band



Ideal Band-reject
filter => rejects
signals within a
frequency band


Low-Pass Filters

Series RL Circuit (Qualitative Analysis)

Impedances

Inductor $\Rightarrow Z = j\omega L$


Resistor $\Rightarrow Z = R$

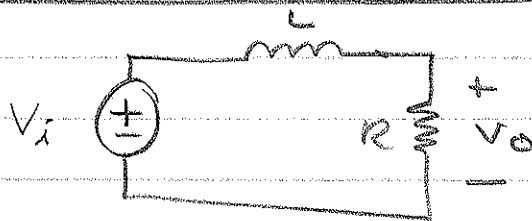

Low Frequencies $\Rightarrow \omega L \ll R$

If the inductor impedance is much lower than the resistor impedance, the inductor "effectively" acts as a short circuit

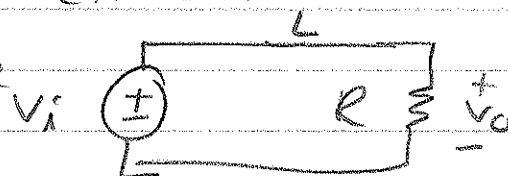\Rightarrow output voltage = input voltage




High Frequencies $\Rightarrow \omega L \gg R$


Inductor effectively acts as an open circuit

Magnitude of the output voltage = 0

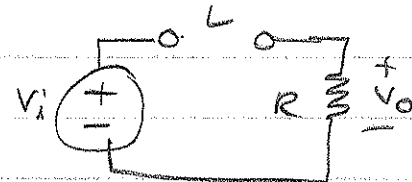phase angle for ^{the} output ^{voltage} lags the input by 90°



Frequency Response Plot

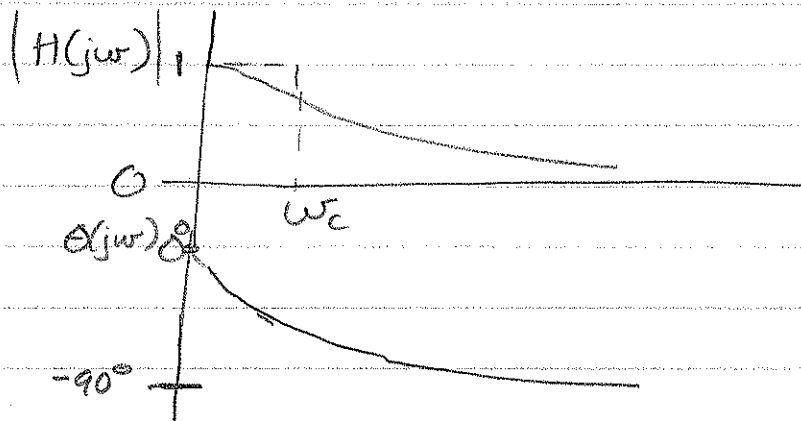

40

CIRCUITS II

Cutoff Frequency

In practice, the cutoff frequency is when the transfer function magnitude is decreased by $1/\sqrt{2}$

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} H_{\max}$$

where: H_{\max} is the maximum magnitude of the transfer function

Why $1/\sqrt{2}$?

Let V_L be the voltage drop across a load
Average power delivered to the load

$$P = \frac{1}{2} \frac{V_L^2}{R}$$

Maximum Power \Rightarrow when V_L is max

$$P_{\max} = \frac{1}{2} \frac{V_{L\max}^2}{R} \quad V_{L\max} = H_{\max} |V_i|$$

$$|V_L(j\omega_c)| = |H(j\omega_c)| |V_i|$$

$$\frac{1}{\sqrt{2}} H_{\max}$$

$$= \frac{1}{\sqrt{2}} H_{\max} |V_i|$$


$$= \frac{1}{\sqrt{2}} V_{L\max}$$

$$P(j\omega_c) = \frac{1}{2} \left(\frac{1}{\sqrt{2}} V_{L\max} \right)^2 \frac{1}{R}$$

$$= \frac{1}{2} \left[\frac{1}{2} \frac{V_{L\max}^2}{R} \right]$$

$$\left[P(j\omega_c) = \frac{1}{2} P_{\max} \right] \quad \omega_c \Rightarrow \text{half-power frequency}$$

(41)

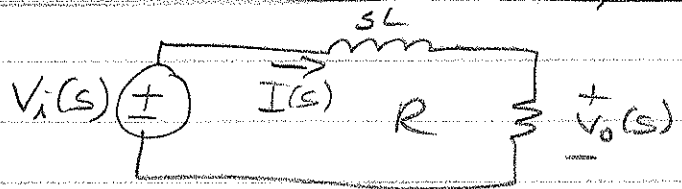CIRCUITS IISeries RL Circuit - Quantitative Analysis

$$-V_i + I sL + IR = 0$$

$$I = \frac{V_i}{sL + R}$$

$$V_o = IR = \frac{V_i R}{sL + R}$$

$$V_o = V_i \left(\frac{R/L}{s + R/L} \right)$$

$$H(s) = \frac{R/L}{s + R/L}$$

For the frequency response $\Rightarrow s = j\omega$

$$H(j\omega) = \frac{R/L}{j\omega + R/L}$$

Convert to phasor notation

ASIA.

$$|H(j\omega)| = \frac{R/L}{\sqrt{\omega^2 + (R/L)^2}} \quad (\text{magnitude of } H(j\omega))$$

$$\theta(j\omega) = -\tan^{-1}\left(\frac{\omega L}{R}\right) \quad (\text{phase angle of } H(j\omega))$$

Cutoff Frequency $|H(j\omega_c)| = \frac{1}{\sqrt{2}} H_{\max}$


$$H_{\max} = |H(j0)| = 1$$

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}}(1) = \frac{R}{\sqrt{\omega_c^2 + (R/L)^2}}$$

$$\omega_c = R/L$$

Low-Pass FiltersSeries RC Circuit

$$Z_C = \frac{-j}{\omega C}$$

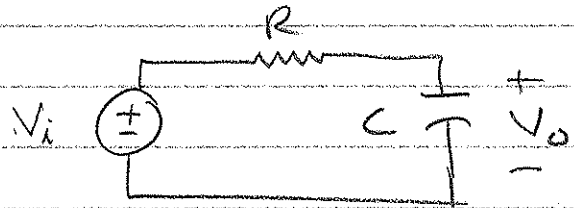

$$\omega = 0 \Rightarrow Z_C \Rightarrow \infty$$


$V_o = V_i$ (open circuit)

$$\omega = \infty \Rightarrow Z_C \Rightarrow 0$$

Short-circuit $V_o = 0$

Example 14.2

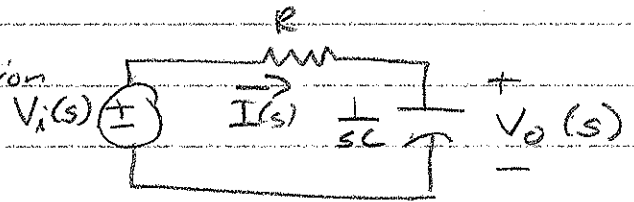(a) Find the transfer function for $V_o(s)$



KVL

$$-V_i + IR + \frac{I}{sC} = 0$$

$$I = \frac{V_i}{R + \frac{1}{sC}}$$

$$V_o = (I) \left(\frac{1}{sC} \right) = \frac{V_i}{\left(R + \frac{1}{sC} \right)} \left(\frac{1}{sC} \right) = \frac{V_i}{RCs + 1}$$

$$V_o = \frac{V_i (1/RC)}{s + 1/RC}$$

$$H(s) = \frac{1/RC}{s + 1/RC}$$

(b) Determine the cutoff frequency, ω_c

$$|H(j\omega)| = \frac{1/RC}{j\omega + 1/RC}$$

$$|H(j\omega)| = \frac{1/RC}{\sqrt{\omega^2 + \left(\frac{1}{RC}\right)^2}}$$

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} H_{\max}$$

Low Pass filter $H_{\max} = H(j0) = 1$

$$\frac{\frac{1}{RC}}{\sqrt{\omega_c^2 + (\frac{1}{RC})^2}} = \frac{1}{\sqrt{2}} \quad (1)$$

$$\boxed{\omega_c = \frac{1}{RC}}$$

(c) Choose values for R and C that will yield a cutoff frequency of 3 kHz

$$\omega_c = \frac{1}{RC}$$

$$(3000 \text{ Hz}) \left(\frac{2\pi \text{ rad/s}}{1 \text{ Hz}} \right) = \frac{1}{RC}$$

$$\frac{1}{RC} = 18849.56$$

Select a value for C \Rightarrow Calculate R

\Rightarrow less available capacitor values than for resistors or inductors

$$\underline{\text{Let } C = 1 \mu\text{F}}$$

$$\frac{1}{R(1 \times 10^{-6} \text{ F})} = 18,849.56$$

$$\boxed{R = 53.05 \Omega}$$

In general for RL or RC Circuits

$$\boxed{H(s) = \frac{\omega_c}{s + \omega_c}}$$

$$\underline{RL} \Rightarrow \omega_c = R/L$$

$$\underline{RC} \Rightarrow \omega_c = 1/RC$$

44

CIRCUITS II


High-Pass Filters

=> Attenuates Lower frequency input signals

Series RC Circuit

$$\omega = 0, V_o = 0$$

$$\omega = \infty, V_o = V_i$$

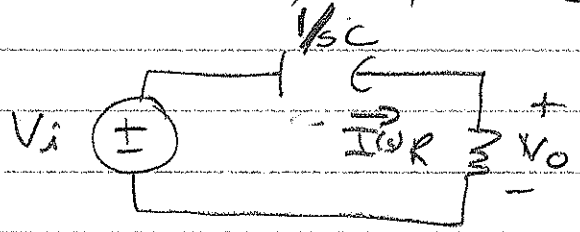

Transfer Function

$$-V_i + I\left(\frac{1}{sC}\right) + IR = 0$$

$$I = \frac{V_i}{R + \frac{1}{sC}}$$


$$V_o = IR = \frac{R V_i}{R + \frac{1}{sC}} = \frac{R s V_i}{R s + \frac{1}{C}} = \frac{s V_i}{s + \frac{1}{RC}}$$

$$H(s) = \frac{s}{s + 1/RC}$$

$$H(j\omega) = \frac{j\omega}{j\omega + 1/RC}$$

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + (1/RC)^2}}$$

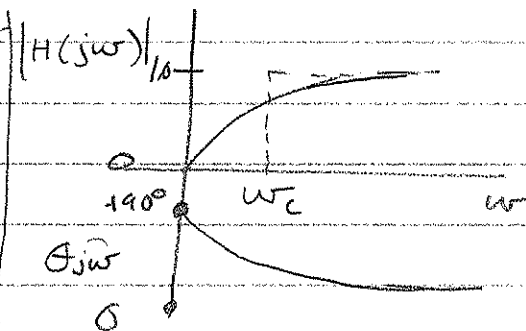
$$\theta(j\omega) = 90^\circ - \tan^{-1}(\omega RC)$$



Cutoff Frequency

$$\frac{1}{\sqrt{2}} = \frac{\omega_c}{\sqrt{\omega_c^2 + (1/RC)^2}}$$

$$\omega_c = 1/RC$$

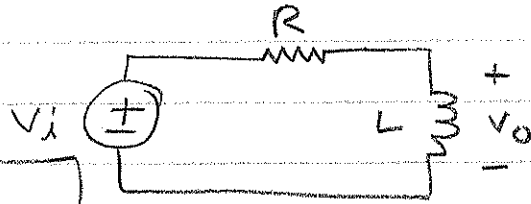CIRCUITS IISeries RL Circuit

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + (R/L)^2}}$$

$$|\theta(j\omega)| = 90^\circ - \tan^{-1}\left(\frac{\omega L}{R}\right)$$

Bandpass Filters

=> Pass Voltages within a frequency band

Parameters

Center Frequency (ω_0) => Frequency where the circuit's transfer function is purely real ($|H(j\omega)|$ is maximum)

- Also called the resonant frequency

Bandwidth (β) => Width of the pass band



Quality Factor (Q) ratio of the center frequency to the bandwidth

$$Q = \frac{\omega_0}{\beta}$$

Series RLC Circuit

$\omega = 0 \Rightarrow V_o = 0$


$\omega = \infty \Rightarrow V_o = 0$

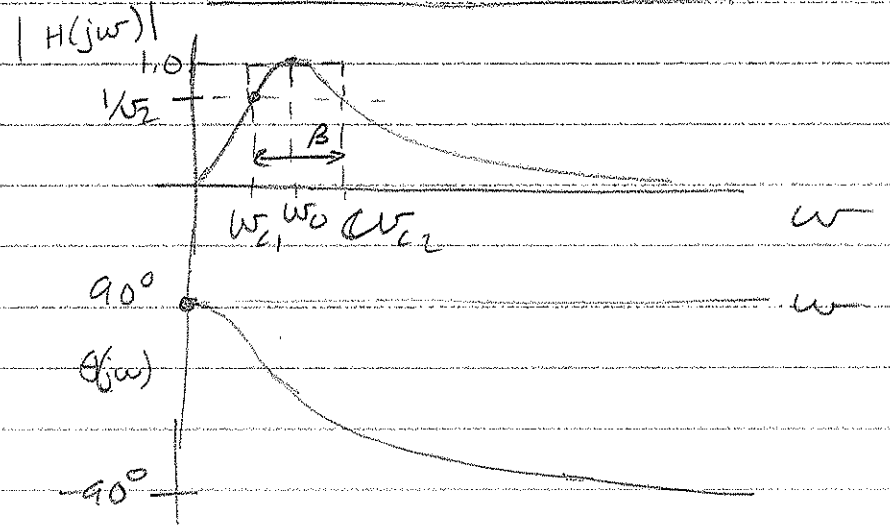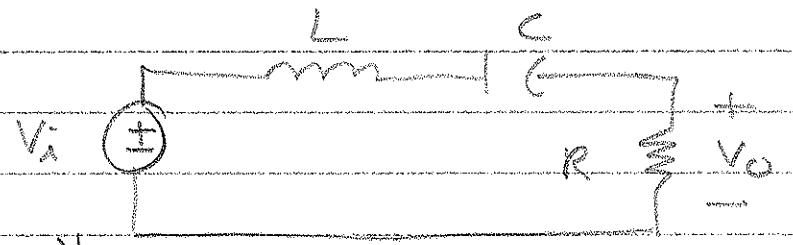

(47)

CIRCUITS II

$$H(s) = \frac{(R/L)s}{s^2 + (R/L)s + 1/LC}$$

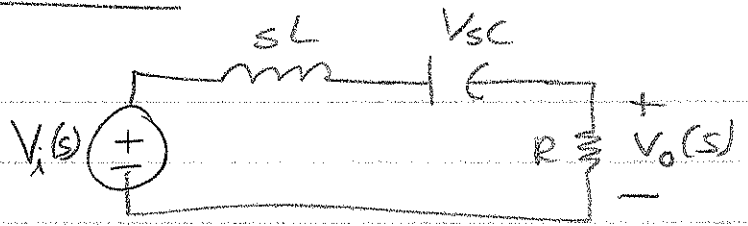Substitute $s = j\omega$

$$|H(j\omega)| = \frac{\omega(R/L)}{\sqrt{(\frac{1}{LC} - \omega^2)^2 + (\omega R/L)^2}}$$

$$\theta(j\omega) = 90^\circ - \tan^{-1}\left(\frac{\omega(R/L)}{\frac{1}{LC} - \omega^2}\right)$$

Center Frequency, ω_0

$$Z_C = Z_L = 0$$

$$j\omega_0 L - \frac{j}{\omega_0 C} = 0$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

 ω_{c1} & ω_{c2}

$$H_{max} = |H(j\omega_0)| = \frac{\omega_0(R/L)}{\sqrt{(\frac{1}{LC} - \omega_0^2)^2 + (\omega_0 R/L)^2}}$$

Substitute $\omega_0 = \sqrt{1/LC}$

$$H_{max} = 1$$

$$\frac{1}{\sqrt{2}} (1) = \frac{\omega_c(R/L)}{\sqrt{(\frac{1}{LC} - \omega_c^2)^2 + (\omega_c R/L)^2}}$$

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{(\omega_c \frac{L}{R} - \frac{1}{\omega_c RC})^2 + 1}}$$

CIRCUITS II

$$\left(\omega_c \frac{L}{R} - \frac{1}{\omega_c RC} \right)^2 + 1 = 2$$

$$\pm 1$$

$$\pm 1 = \omega_c \frac{L}{R} - \frac{1}{\omega_c RC}$$

$$\omega_c^2 L \pm \omega_c R - \frac{1}{C} = 0$$

Quadratic Formula \Rightarrow Four answers, only two are positive

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

Bandwidth β

$$\beta = \omega_{c2} - \omega_{c1} = \frac{R}{L}$$

Quality Factor, Q

$$Q = \frac{\omega_0}{\beta} = \frac{\sqrt{1/LC}}{R/L} = \sqrt{\frac{L}{CR^2}}$$

Alternative Forms for Cutoff Frequencies

$$\omega_{c1} = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$

$$\omega_{c2} = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$


$$\omega_{c1} = \omega_0 \left[-\frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right]$$

$$\omega_{c2} = \omega_0 \left[\frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right]$$

①

Problem 14.10High-Pass filter

$f_c = 800 \text{ Hz}$


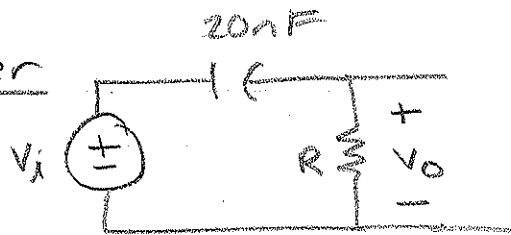


(a) Specify R

$$\frac{1}{RC} = \omega_c = (2\pi)(800)$$

$$\frac{1}{R(20 \times 10^{-9})} = (2\pi)(800)$$

$$R = 9.95 \text{ k}\Omega$$

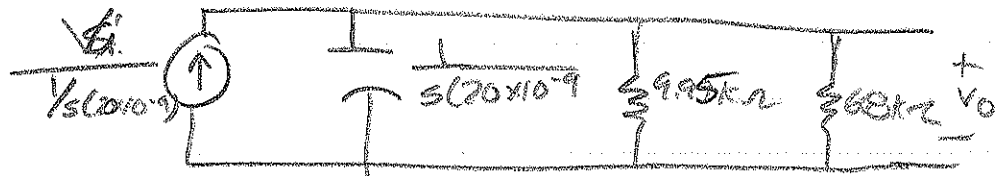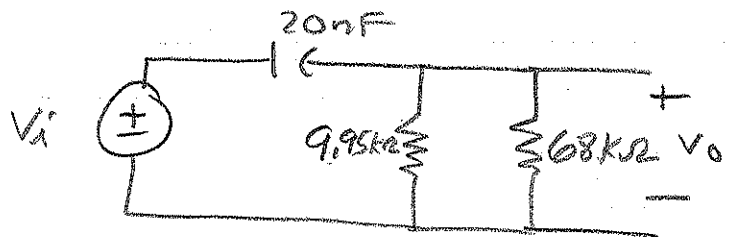(b) Find ω_c 

$$\frac{V_o}{s(20 \times 10^{-9})} + \frac{V_o}{9.95} + \frac{V_o}{68} = \frac{V_i (20 \times 10^{-9}) s}{s}$$

$$V_o = \frac{V_i (20 \times 10^{-9}) s}{(20 \times 10^{-9}) s + \frac{1}{9.95 \times 10^3} + \frac{1}{68 \times 10^3}}$$

$$H(s) = \frac{s}{s + \frac{1}{20 \times 10^{-9}} \left(\frac{1}{9.95 \times 10^3} + \frac{1}{68 \times 10^3} \right)}$$

$$H(j\omega) = \frac{j\omega}{j\omega + \frac{1}{20 \times 10^{-9}} \left(\frac{1}{9.95 \times 10^3} + \frac{1}{68 \times 10^3} \right)}$$

$$|H(j\omega)| = \frac{\omega}{\omega^2 + \left[\frac{1}{20 \times 10^{-9}} \left(\frac{1}{9.95 \times 10^3} + \frac{1}{68 \times 10^3} \right) \right]^2}$$

②

$$\omega_c = \frac{1}{20 \times 10^{-9}} \left(\frac{1}{9.95 \times 10^3} + \frac{1}{68 \times 10^3} \right)$$

$$\omega_c = 5760 \text{ rad/s}$$

$$f_c = \frac{5760}{2\pi} = 917 \text{ Hz}$$

What if

$$H(s) = \frac{s}{s(4) + 10}$$

$$H(s) = \frac{s/4}{s + \frac{10}{4}}$$

$$H(j\omega) = \frac{1}{4} \left[\frac{j\omega}{j\omega + \frac{10}{4}} \right]$$

$$|H(j\omega)| = \frac{1}{4} \left[\frac{\omega}{\sqrt{\omega^2 + \left(\frac{10}{4}\right)^2}} \right]$$

Max value = 1

$$H_{\max} = \frac{1}{4}$$


$$\omega_c = \frac{10}{4}$$

$$H_{\max} \ll 1$$


Bandreject Filters

Series RLC Circuit

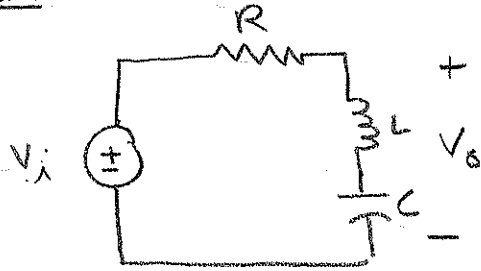$\omega = 0 \Rightarrow V_o = V_i$
 $\omega = \infty \Rightarrow V_o = V_i$



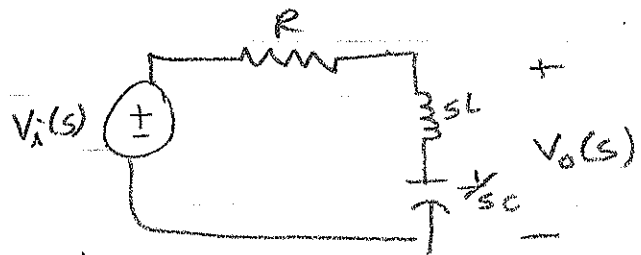
$$H(s) = \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$



$$|H(j\omega)| = \frac{|\frac{1}{LC} - \omega^2|}{\sqrt{(\frac{1}{LC} - \omega^2)^2 + (\frac{\omega R}{L})^2}}$$

$$\Theta(j\omega) = -\tan^{-1}\left(\frac{\omega R/L}{\frac{1}{LC} - \omega^2}\right)$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

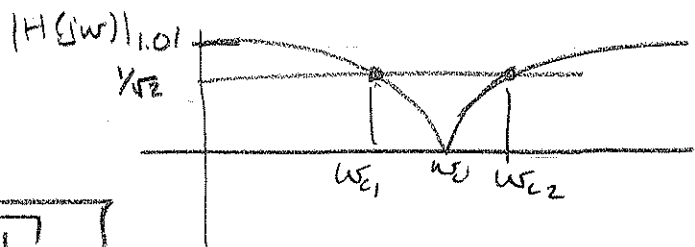

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\beta = \frac{R}{L}$$

$$Q = \sqrt{\frac{L}{R^2 C}}$$

Bode Diagrams

- Efficient method used for generating and plotting amplitude and phase data.

Start with $H(s)$

$$H(s) = \frac{K (s + z_1)}{s (s + p_1)}$$

zeros
constants
poles

$$H(j\omega) = \frac{K(j\omega + z_1)}{j\omega(j\omega + p_1)}$$

Factor out zeros and poles

$$H(j\omega) = \frac{K z_1 (1 + j\omega/z_1)}{p_1 (j\omega) (1 + j\omega/p_1)}$$

(standard form)

$$\text{Let } K_0 = \frac{K z_1}{p_1}$$

$$H(j\omega) = \frac{K_0 (1 + j\omega/z_1)}{(j\omega) (1 + j\omega/p_1)}$$

$$= \frac{K_0 |1 + j\omega/z_1| \angle \psi_1}{(|\omega| \angle 90^\circ) (|1 + j\omega/p_1| \angle \beta_1)}$$

$$= \frac{K_0 |1 + j\omega/z_1|}{(|\omega|) (|1 + j\omega/p_1|)} \angle (\psi_1 - 90^\circ - \beta_1)$$

51

CIRCUITS II

$$|H(j\omega)| = \frac{K_0 |1 + j\omega/z_1|}{|\omega| |1 + j\omega/p_1|}$$
$$\theta(\omega) = \psi_1 - 90^\circ - \beta_1$$

$$\tan \psi_1 = \frac{\omega/z_1}{1} \Rightarrow \psi_1 = \tan^{-1}(\omega/z_1)$$
$$\tan \beta_1 = \frac{\omega/p_1}{1} \Rightarrow \beta_1 = \tan^{-1}(\omega/p_1)$$

Straight Line Plots

Express the amplitude of $H(j\omega)$ in terms of a logarithmic value: the decibel (dB)

$$A_{dB} = 20 \log_{10} |H(j\omega)|$$

$$A_{dB} = 20 \log_{10} \left(\frac{K_0 |1 + j\omega/z_1|}{\omega |1 + j\omega/p_1|} \right)$$
$$= 20 \log_{10}(K_0) + 20 \log_{10} |1 + j\omega/z_1|$$
$$- 20 \log_{10}(\omega) - 20 \log_{10} |1 + j\omega/p_1|$$

- Plot each term separately, and add graphically to get A_{dB}
- Approximate as straight lines

52

CIRCUITS II

$$20 \log_{10}(K_0) = \text{constant}$$


$$20 \log_{10} |1 + j\omega/z_1|$$

Small values of ω


$$\text{As } \omega \rightarrow 0, \quad 20 \log_{10} |1 + \frac{j\omega}{z_1}| \rightarrow 0$$

Large values of ω
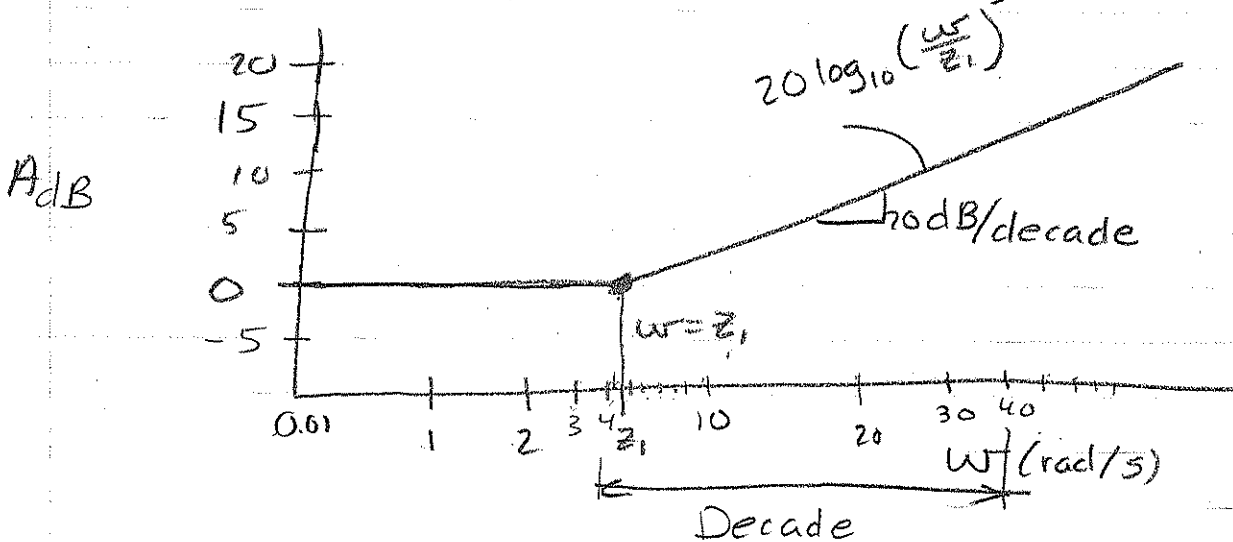
$$\text{As } \omega \rightarrow \infty, \quad 20 \log_{10} (\omega/z_1)$$



$$-20 \log_{10}(\omega)$$

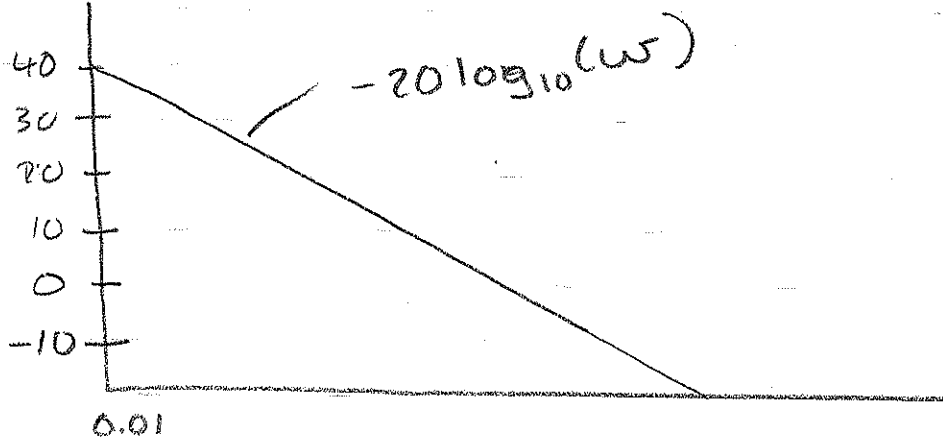

$$-20 \log_{10} |1 + j\omega/P_1|$$

