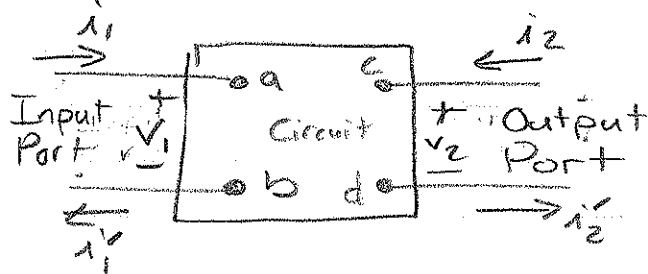


### Chapter 18: Two-Port Circuits

- Previously, focused on the behavior of a circuit at a single pair of terminals
- Also can look at two pairs of terminals  
Each pair of terminals  $\Rightarrow$  port
- Signal fed into a pair of terminals (Input Port) and is then extracted from a second pair of terminals (Output Port)
- Can also be more than two ports




Two-port building block

### Restrictions

- 1) No energy can be stored in the circuit
- 2) No independent sources with the circuit (can be dependent sources)
- 3) Current into the port must equal the current out of the port  

$$i_1 = i_1' \quad , \quad i_2 = i_2'$$
- 4) All <sup>external</sup> connections must be made to either the input or output ports (no connections between ports) (e.g.  $a-c$ ,  $b-c$ ,  $a-d$ )

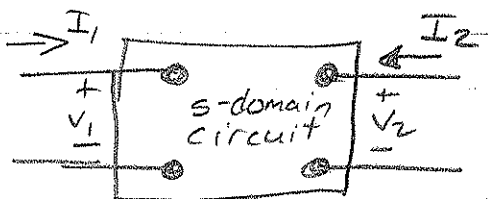CIRCUITS IITerminal Equations

- Four terminal variables  $\Rightarrow I_1, V_1, I_2, V_2$   
 $\Rightarrow$  Two are independent
- If we know two variables, can solve for the other two using two simultaneous equations.

Six Different Ways

$$\begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} I_2 \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 \end{aligned}$$

$I_1, I_2$  known

$$\begin{aligned} I_1 &= Y_{11} V_1 + Y_{12} V_2 \\ I_2 &= Y_{21} V_1 + Y_{22} V_2 \end{aligned}$$

$V_1, V_2$  known

$$\begin{aligned} V_1 &= a_{11} V_2 - a_{12} I_2 \\ I_1 &= a_{21} V_2 - a_{22} I_2 \end{aligned}$$

$V_2, I_2$  known

$$\begin{aligned} V_2 &= b_{11} V_1 - b_{12} I_1 \\ I_2 &= b_{21} V_1 - b_{22} I_1 \end{aligned}$$

$V_1, I_1$  known

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$

$I_1, V_2$  known

$$\begin{aligned} I_1 &= g_{11} V_1 + g_{12} I_2 \\ V_2 &= g_{21} V_1 + g_{22} I_2 \end{aligned}$$

$V_1, I_2$  known

78

## CIRCUITS II

Coefficients on the right-hand side  
=> parameters of the two-port  
circuit

z parameters, a parameters, b parameters,  
h parameters, and g parameters

### Two-port Parameters

Can be determined by computation or  
measurement

### z parameters

Two port equations

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

$$I_2 = 0$$

$z_{11} = \frac{V_1}{I_1} \Big _{I_2=0}$
$z_{21} = \frac{V_2}{I_1} \Big _{I_2=0}$
$z_{12} = \frac{V_1}{I_2} \Big _{I_1=0}$
$z_{22} = \frac{V_2}{I_2} \Big _{I_1=0}$

$I_1=0$

$z_{11}$  => impedance seen looking into port 1  
when port 2 is open

$z_{12}$  => transfer impedance => ratio of port 1  
voltage to port 2 current when port  
1 is open

CIRCUITS II


$z_{21} \Rightarrow$  transfer impedance  $\Rightarrow$  ratio of port 2 voltage to port 1 current when port 2 is open

$z_{22} \Rightarrow$  impedance seen looking into port 2 when port 1 is open



①

CIRCUITS IIExample 18.1

Determine:

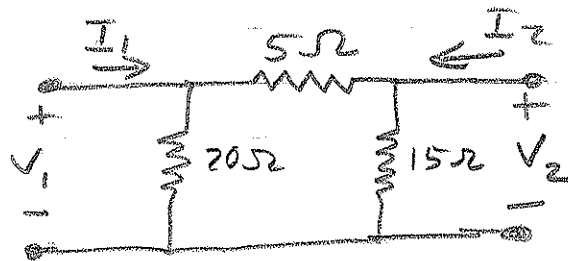The  $z$ -parameter

$z_{11} \Rightarrow$  resistance seen looking into port 1 when port 2 is open,  $z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$

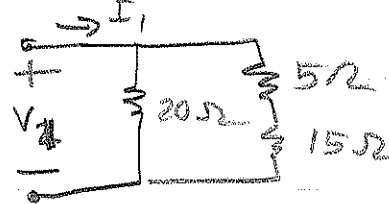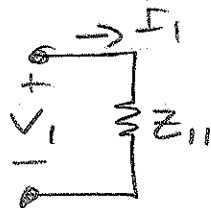

$$z_{11} = \left( \frac{1}{20\Omega} + \frac{1}{5\Omega + 15\Omega} \right)^{-1}$$

$$z_{11} = \left( \frac{1}{20\Omega} + \frac{1}{20\Omega} \right)^{-1} = \left( \frac{20 + 20}{(20)(20)} \right)^{-1}$$

$$= \frac{(20)(20)}{20 + 20} = \boxed{10\Omega}$$

$$z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = \left( \frac{1}{15\Omega} + \frac{1}{20\Omega + 5\Omega} \right)^{-1}$$

$$= \left( \frac{25 + 15}{(15)(25)} \right)^{-1} = \frac{(15)(25)}{25 + 15}$$

$$\boxed{z_{22} = 9.375\Omega}$$


$$z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

terms of a single variable  
Need  $V_2$  &  $I_1$  when  $I_2=0$

$$I_1 \Big|_{I_2=0} = \frac{V_1}{z_{11}} = \frac{V_1}{10}$$

Current Divider Circuit
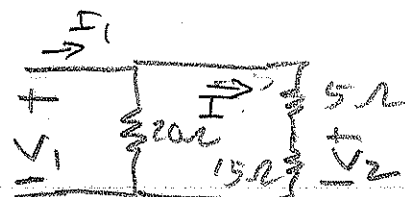
$$I = \frac{20\Omega}{(15\Omega + 5\Omega) + 20\Omega} = 0.5 I_1$$



②

## CIRCUITS II

$$V_2 = (15\Omega)I = 7.5I_1$$

$$V_2 = 7.5 \left( \frac{V_1}{10} \right) = 0.75 V_1 \quad \text{When } I_2 = 0$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = \frac{0.75 V_1}{V_1/10} = \boxed{7.5\Omega}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

Find  $V_1$  &  $I_2$  in terms of  $V_2$  when  $I_1 = 0$


$$I_2 = \frac{V_2}{Z_{22}} = \frac{V_2}{9.375}$$

$$I = \frac{15\Omega}{(15\Omega + 5\Omega + 20\Omega)} I_2$$

$$I = 0.375 I_2$$

$$V_1 = 20I = 7.5I_2 = 7.5 \left( \frac{V_2}{9.375} \right) = 0.8 V_2$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = \frac{0.8 V_2}{V_2/9.375} = 7.5\Omega$$

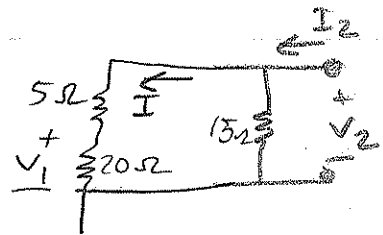

Parameter Conversion

Use matrix Form

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Cramer's Method

$$V_1 = \frac{\begin{vmatrix} I_1 & Y_{12} \\ I_2 & Y_{22} \end{vmatrix}}{\begin{vmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{vmatrix}}} = \frac{Y_{22} I_1 - Y_{12} I_2}{\Delta Y}$$

$$V_1 = \underbrace{\frac{Y_{22}}{\Delta Y}}_{Z_{11}} I_1 - \underbrace{\frac{Y_{12}}{\Delta Y}}_{Z_{12}} I_2$$

$$V_2 = \frac{\begin{vmatrix} Y_{11} & I_1 \\ Y_{21} & I_2 \end{vmatrix}}{\begin{vmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{vmatrix}}} = \frac{Y_{11} I_2 - Y_{21} I_1}{\Delta Y}$$

$$V_2 = \underbrace{\frac{-Y_{21}}{\Delta Y}}_{Z_{21}} I_1 + \underbrace{\frac{Y_{11}}{\Delta Y}}_{Z_{22}} I_2$$

$$\boxed{Z_{11} = \frac{Y_{22}}{\Delta Y}, Z_{12} = \frac{-Y_{12}}{\Delta Y}, Z_{21} = \frac{-Y_{21}}{\Delta Y}, Z_{22} = \frac{Y_{11}}{\Delta Y}}$$

Parameter Conversion Table  $\Rightarrow$  Table 18.1