


①

## CIRCUITS II
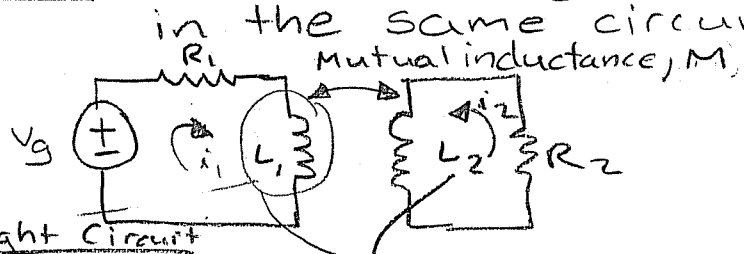
### Mutual Inductance (6.4)

- Two circuits are linked by a magnetic field
- Voltage in
- Induced voltage in one circuit is related by the current in the other circuit through mutual inductance

- Self-Inductance - relates voltage to current in the same circuit



Left Circuit

Right Circuit

Induced voltages  $L_1 \frac{di_1}{dt}, M \frac{di_2}{dt}$


$L_2 \frac{di_2}{dt}, M \frac{di_1}{dt}$  self inductance

### Dot Convention for Mutual Inductance

- Provides information on polarities
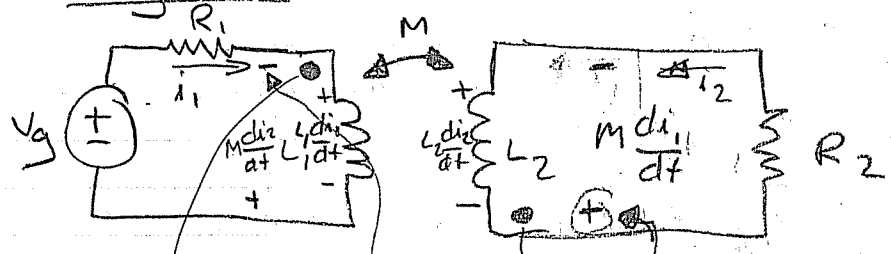
#### Rules

- When the reference direction for the current enters the dotted terminal of the coil, the polarity of the voltage of the other coil is positive at the dotted terminal
- When the reference direction for the current leaves the dotted terminal of the coil, the polarity of the voltage of the other coil is negative at the dotted terminal.



current enters dotted terminal

current leaves dotted terminal

2


## CIRCUITS II

### Mesh Current Method

$$-v_g + i_1 R_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} = 0 \quad (\text{Left Mesh})$$

$$i_2 R_2 + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} = 0 \quad (\text{Right Mesh})$$

### Determining Dot Markings

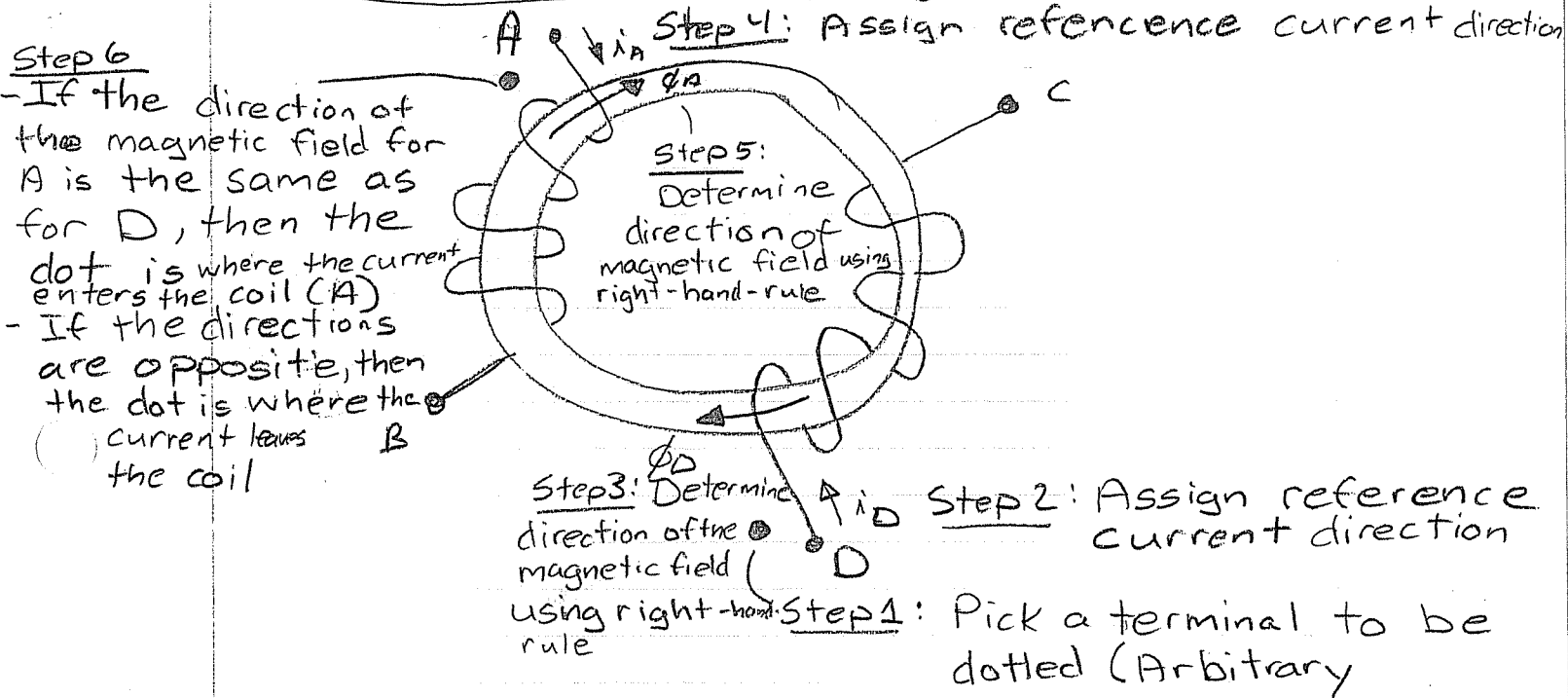

### Self Inductance

Faraday's Law

$$v = \frac{d\lambda}{dt}$$

$\lambda$  = flux linkage measured in weber-turns

$$\lambda = N\phi$$

$N$  = number of turns linked by the field

$\phi$  = magnetic flux

$$\phi = \mathcal{P} Ni$$

$\mathcal{P}$  = permeance of the space occupied by flux (magnetic properties)

3


### CIRCUITS II

$N$  = number of turns in the coil

$$v = \frac{d\lambda}{dt} = \frac{d(N\phi)}{dt} = N \frac{d\phi}{dt} = N \frac{d}{dt} (\mathcal{P} N i)$$

$$v = \underbrace{N^2 \mathcal{P}}_L \frac{di}{dt} \Rightarrow v = L \frac{di}{dt}$$

### Mutual Inductance

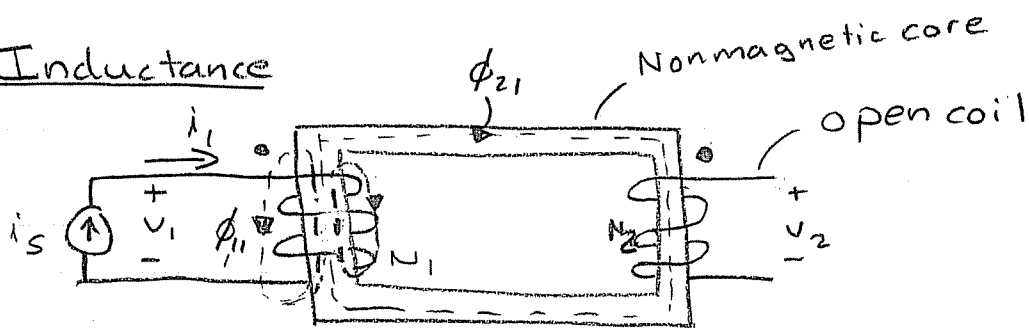

Total flux in coil 1,  $\phi_1$

$$\phi_1 = \phi_{11} + \phi_{21}$$

$\phi_{11}$  = produced by  $i_1$  in coil 1 that links  $N_1$

$$\phi_{11} = \mathcal{P}_{11} N_1 i_1$$

$\phi_{21}$  = produced by  $i_1$  in coil 1, but links  $N_2$

$$\phi_{11} = \mathcal{P}_{11} N_1 i_1$$

$$\phi_{21} = \mathcal{P}_{21} N_1 i_1$$

$$\mathcal{P}_1 = \mathcal{P}_{11} + \mathcal{P}_{21}$$

$$v_1 = \frac{d\lambda_1}{dt} = \frac{d(N_1 \phi_1)}{dt} = N_1 \frac{d}{dt} (\phi_{11} + \phi_{21})$$

$$= N_1 \frac{d}{dt} (N_1 \mathcal{P}_{11} i_1 + N_1 \mathcal{P}_{21} i_1) = \underbrace{N_1^2 \mathcal{P}_1}_{L_1} \frac{di_1}{dt} = \boxed{L_1 \frac{di_1}{dt}}$$

$$v_2 = \frac{d\lambda_2}{dt} = \frac{d(N_2 \phi_{21})}{dt} = N_2 \frac{d}{dt} (\mathcal{P}_{21} i_1)$$

$$v_2 = \underbrace{N_2 N_1 \mathcal{P}_{21}}_{M_{21}} \frac{di_1}{dt}$$

$$M_{21} = N_2 N_1 \mathcal{P}_{21}$$

Similarly

$$M_{12} = N_1 N_2 \mathcal{P}_{12}$$

For nonmagnetic cores

$$\mathcal{P}_{12} = \mathcal{P}_{21} \Rightarrow \boxed{M_{12} = M_{21}}$$

④

## CIRCUITS II

$$L_1 = N_1^2 \mathcal{P}_1 = N_1^2 (\mathcal{P}_{11} + \mathcal{P}_{21})$$

$$L_2 = N_2^2 \mathcal{P}_2 = N_2^2 (\mathcal{P}_{22} + \mathcal{P}_{12})$$

$$L_1 L_2 = N_1^2 N_2^2 (\mathcal{P}_{11} + \mathcal{P}_{21})(\mathcal{P}_{22} + \mathcal{P}_{12})$$

$$= M^2 \underbrace{\left(1 + \frac{\mathcal{P}_{11}}{\mathcal{P}_{12}}\right) \left(1 + \frac{\mathcal{P}_{22}}{\mathcal{P}_{12}}\right)}_{1/k^2}$$

$1/k^2$

$k \Rightarrow$  coefficient of coupling

$$M^2 = k^2 L_1 L_2$$

$$\boxed{M = k \sqrt{L_1 L_2}}$$

$$0 \leq k \leq 1$$

## Energy

$$w(t) = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 \pm M i_1 i_2$$

If both currents enter the polarity marked terminals,  $\Rightarrow + M i_1 i_2$


If one enters while the other leaves,  $\Rightarrow - M i_1 i_2$

If both leaving  $\Rightarrow + M i_1 i_2$

Example 6.6  
Drill Exercise 6.8

①

Example 6.6

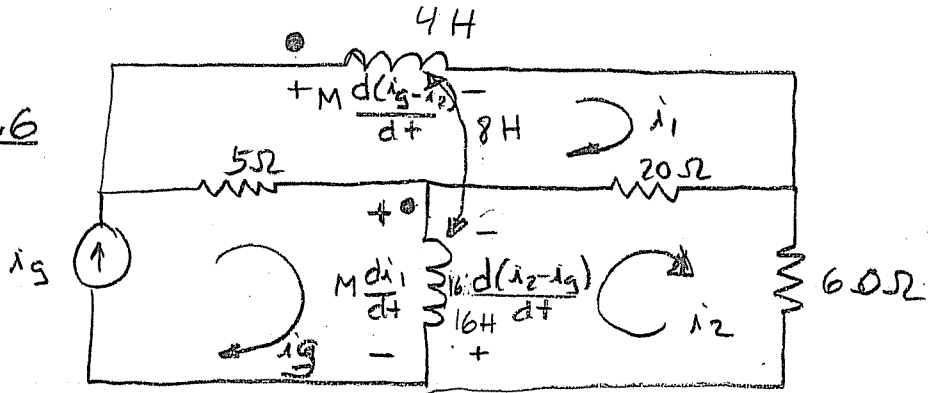

(a) Write a set of Mesh-Current Equations that describe the circuit in terms of  $i_1$  &  $i_2$



Mesh 1

$$(4H) \frac{di_1}{dt} + (8H) \frac{d(i_1 - i_2)}{dt} + (20\Omega)(i_1 - i_2) + (5\Omega)(i_1 - i_g) = 0$$

Mesh 2

$$(20\Omega)(i_2 - i_1) + (60\Omega)(i_2) + (16H) \frac{d(i_2 - i_g)}{dt} - (8H) \frac{di_1}{dt} = 0$$

(b) Verify that if there is no energy stored in the circuit at  $t=0$  and if  $i_g = 16 - 16e^{-5t}$  A, that the solutions for  $i_1$  &  $i_2$  are

$$i_1 = 4 + 64e^{-5t} - 68e^{-4t} \text{ A}$$

$$i_2 = 1 - 52e^{-5t} + 51e^{-4t} \text{ A}$$

No energy at  $t=0 \Rightarrow i=0$

$$i_1(0) = (4 + 64 - 68) \text{ A} = 0$$

$$i_2(0) = (1 - 52 + 51) \text{ A} = 0$$


@  $t = \infty \Rightarrow$  voltage in the inductor = 0

$$i_g = 16 \text{ A}, i_1 = 4 \text{ A}, i_2 = 1 \text{ A}$$

②

Example 6.6

Use KVL + KCL ✓

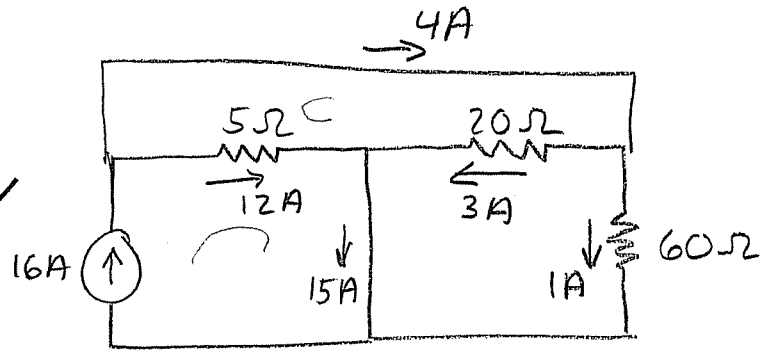

①

Drill Exercise 6.8

Two coupled coils wound around a nonmagnetic core

$$L_1 = 288 \text{ mH}, \quad M = 90 \text{ mH}$$

$$K = 0.75 \quad P_{11} = P_{22}$$

(a) Find  $L_2$  and  $N_1/N_2$  (turns ratio)

$$M = K\sqrt{L_1 L_2}$$

$$L_2 = \frac{1}{L_1} \left( \frac{M}{K} \right)^2 = \frac{1}{288 \times 10^{-3}} \left( \frac{90 \times 10^{-3}}{0.75} \right)^2$$

$$L_2 = 0.05 \text{ H} = \boxed{50 \text{ mH}}$$

$$L_1 = N_1^2 \bar{P}_1$$

$$L_2 = N_2^2 \bar{P}_2$$

$$\frac{L_1}{L_2} = \left( \frac{N_1^2}{N_2^2} \right) \frac{\bar{P}_1}{\bar{P}_2} = \left( \frac{N_1^2}{N_2^2} \right) \left( \frac{\bar{P}_{11} + \bar{P}_{12}}{\bar{P}_{22} + \bar{P}_{21}} \right)$$

$$\bar{P}_{12} = \bar{P}_{21} \text{ (non magnetic)}$$

$$\bar{P}_{11} = \bar{P}_{22} \text{ (given)}$$

$$\frac{N_1}{N_2} = \sqrt{\frac{L_1}{L_2}} = \sqrt{\frac{288 \text{ mH}}{50 \text{ mH}}} = \boxed{2.4}$$

(b) if  $N_1 = 1200$ , what is  $\bar{P}_1 + \bar{P}_2$ 

$$\bar{P}_1 = \frac{L_1}{N_1^2} = \frac{288 \times 10^{-3} \text{ H}}{(1200)^2} = \boxed{2 \times 10^{-7} \text{ Wb/A}}$$

$$N_2 = \frac{N_1}{2.4} = \frac{1200}{2.4} = 500$$


$$\bar{P}_2 = \frac{L_2}{N_2^2} = \frac{50 \times 10^{-3} \text{ H}}{(500)^2} = \boxed{2 \times 10^{-7} \text{ Wb/A}}$$

5

# CIRCUITS II
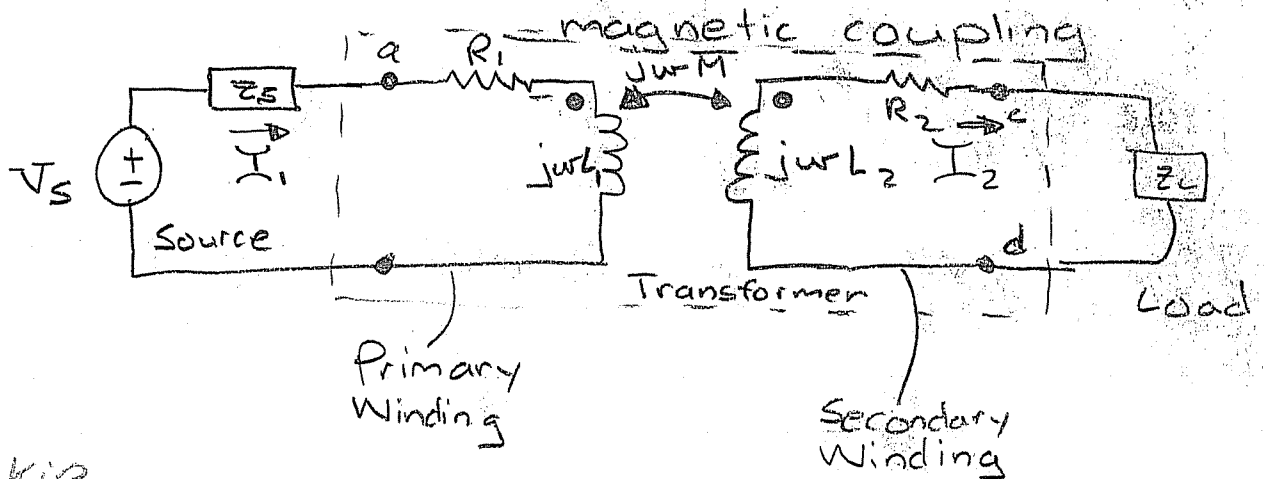
## Transformers (Sinusoidal Steady-State)

Simple Transformer - Two coils wound around a single core to ensure



SKIP  
Mesh-Current

$$-V_s = I_1 (Z_s + R_1 + j\omega L_1) - I_2 (j\omega M)$$

$$I_2 (R_2 + j\omega L_2 + Z_L) - j\omega M I_1 = 0$$

Let  $Z_{11} = Z_s + R_1 + j\omega L_1$   
 $Z_{22} = R_2 + j\omega L_2 + Z_L$

ASA

$$I_1 = \frac{Z_{22}}{Z_{11} Z_{22} + \omega^2 M^2} V_s$$

$$I_2 = \frac{j\omega M}{Z_{11} Z_{22} + \omega^2 M^2} V_s = \frac{j\omega M}{Z_{22}} I_1$$

\* Impedance of the Voltage Source,  $Z_{int}$

$$Z_{int} = \frac{V_s}{I_1} = \frac{Z_{11} Z_{22} + \omega^2 M^2}{Z_{22}} = \boxed{Z_{11} + \frac{\omega^2 M^2}{Z_{22}} Z_{int}}$$

Impedance at the source terminals a + e

$$* Z_{ab} = Z_{int} - Z_s = \frac{Z_{11} Z_{22} + \omega^2 M^2}{Z_{22}} - Z_s = Z_s + R_1 + j\omega L_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$

$$\boxed{Z_{ab} = j\omega L_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}}$$

6

CIRCUITS II

\* Reflected Impedance,  $Z_r$

Defined as  $\frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$

Let the load impedance,  $Z_L = R_L + jX_L$

$$Z_r = \frac{\omega^2 M^2}{R_2 + R_L + j(\omega L_2 + X_L)} \quad \text{--- conjugate}$$

$$Z_r = \frac{\omega^2 M^2}{|Z_{22}|^2} [(R_2 + R_L) - j(\omega L_2 + X_L)]$$

Note:  $Z_{22} = R_2 + R_L + j(\omega L_2 + X_L)$


$$\therefore |Z_{22}|^2 = [(R_2 + R_L) + j(\omega L_2 + X_L)] [(R_2 + R_L) - j(\omega L_2 + X_L)]$$

Start

Ideal Transformer

- $k = 1$
- $L_1 = L_2 = \infty$  (magnetic coupling)
- Coil losses are negligible

Voltage and Current Ratios

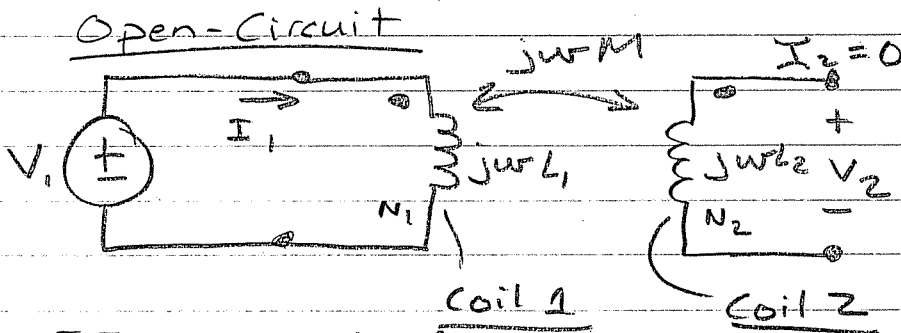

Coil 2  $V_2 = j\omega M I_1$

coil 1  $I_1 = \frac{V_1}{j\omega L_1}$

Substituting

$$V_2 = \frac{M}{L_1} V_1$$

7

CIRCUITS II

Ideal Transformer

$k=1 \quad M = \sqrt{L_1 L_2}$


$V_2 = \frac{\sqrt{L_1 L_2}}{L_1} V_1 \Rightarrow V_2 = \sqrt{\frac{L_2}{L_1}} V_1$

$L_1 = N_1^2 P$

$V_2 = \sqrt{\frac{N_2^2 j\omega}{N_1^2 j\omega}} V_1 \Rightarrow V_2 = \frac{N_2}{N_1} V_1$

$\frac{V_1}{N_1} = \frac{V_2}{N_2}$

Short Circuit

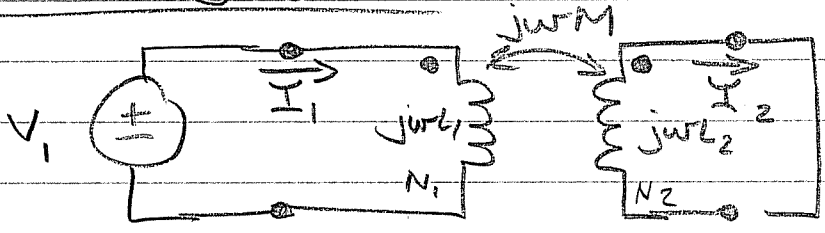


KVL (coil 2)

$0 = -j\omega M I_1 + j\omega L_2 I_2$

$\frac{I_1}{I_2} = \frac{L_2}{M} = \frac{L_2}{\sqrt{L_1 L_2}} = \sqrt{\frac{L_2}{L_1}} = \frac{N_2}{N_1}$

$I_1 N_1 = I_2 N_2$

Symbol for an Ideal Transformer

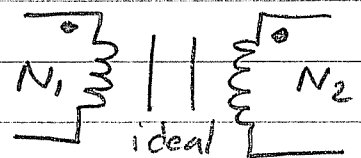



8

## CIRCUITS II

### Polarity of the Voltage and Current Ratios Rules

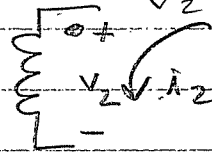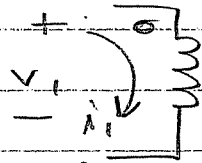- 1) If  $v_1$  &  $v_2$  are <sup>both</sup> positive or negative at the dotted terminal, use a <sup>plus</sup> (+) sign.  $\frac{v_1}{N_1} = \frac{v_2}{N_2}$ . If not, use a negative sign.
- 2) If  $i_1$  &  $i_2$  are both directed in or out of the dotted terminals, use a minus sign. If not, use a plus sign.

$i_1 \Rightarrow$  into dotted terminal       $i_2 \Rightarrow$  into dotted terminal  
 $v_1 \Rightarrow$  + at dotted terminal       $v_2 \Rightarrow$  + at dotted terminal



$$\frac{v_1}{N_1} = \frac{v_2}{N_2}$$

$$N_1 i_1 = -N_2 i_2$$


### Turns ratio

$$a = \frac{N_2}{N_1}$$

where  $a =$  turns ratio


①

Example 9.14

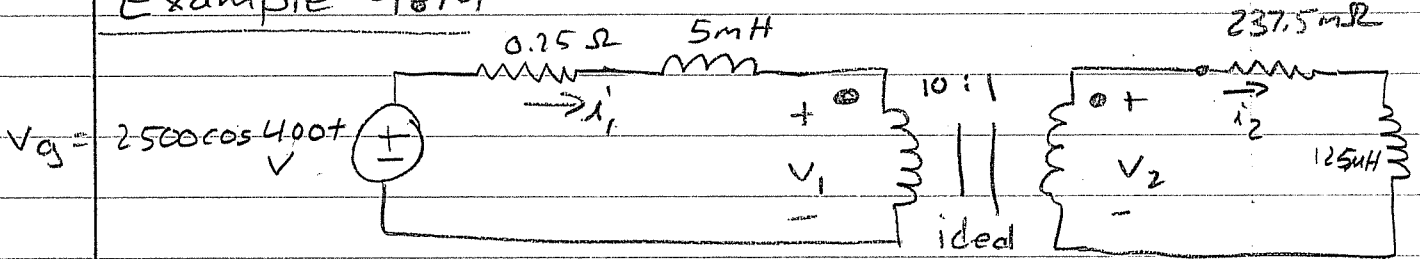

Find:  $i_1, v_1, v_2, i_2$

$$V_g = 2500 \angle 0^\circ \text{ V}$$

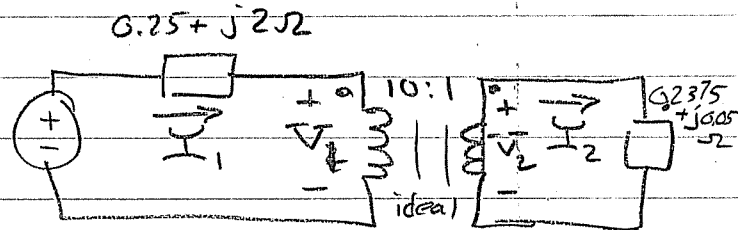

Ideal Transformer

$$\frac{V_1}{N_1} = \frac{V_2}{N_2}$$

$$V_1 = \frac{N_1}{N_2} V_2$$

$$\boxed{V_1 = 10 V_2}$$

$$N_1 i_1 = N_2 i_2$$

$$I_2 = \frac{N_1}{N_2} I_1 \Rightarrow$$

$$\boxed{I_2 = 10 I_1}$$

KVL Left Circuit

$$-2500 \angle 0^\circ + (0.25 + j2) I_1 + V_1 = 0 \quad \text{①}$$

Right Circuit

$$-V_2 + (0.2375 + j0.05) I_2 = 0$$

$$V_2 = (0.2375 + j0.05) I_2 = (0.2375 + j0.05) (10 I_1)$$

$$\left(\frac{V_1}{10}\right) = 10 I_1 (0.2375 + j0.05)$$

$$V_1 = 100 I_1 (0.2375 + j0.05)$$

②

Example 9.14

Substitute into ①

$$2500 \angle 0^\circ = (0.25 + j2) \mathcal{I}_1 + (23.75 + j5) \mathcal{I}_1$$

$$2500 \angle 0^\circ = (24 + j7) \mathcal{I}_1$$

$$Z_m \cos \phi = 24$$

$$Z_m \sin \phi = 7$$

$$2500 \angle 0^\circ = 25 \angle 16.26^\circ \mathcal{I}_1$$

$$\tan \phi = \frac{7}{24}$$

$$\phi = 16.26^\circ$$

$$Z_m = \frac{24}{\cos 16.26^\circ} = 25$$

$$\mathcal{I}_1 = \frac{2500 \angle 0^\circ}{25 \angle 16.26^\circ}$$

$$\boxed{\mathcal{I}_1 = 100 \angle -16.26^\circ \text{ A}}$$

$$\boxed{i_1 = 100 \cos(400t - 16.26^\circ) \text{ A}}$$

$$\mathcal{I}_2 = 10 \mathcal{I}_1 = 1000 \angle -16.26^\circ \text{ A}$$

$$\boxed{i_2 = 1000 \cos(400t - 16.26^\circ) \text{ A}}$$

$$\mathcal{V}_1 = 100(0.2375 + j0.05) \mathcal{I}_1$$

$$\mathcal{V}_1 = (23.75 + j5)(100 \angle -16.26^\circ)$$

$$= (24.27 \angle 11.89^\circ)(100 \angle -16.26^\circ)$$

$$\boxed{\mathcal{V}_1 = 2427 \angle -4.37^\circ \text{ V}} \Rightarrow \boxed{v_1 = 2427 \cos(400t - 4.37^\circ) \text{ V}}$$

$$\mathcal{V}_2 = \frac{1}{10} \mathcal{V}_1 = 242.7 \angle -4.37^\circ$$

$$\boxed{v_2 = 242.7 \cos(400t - 4.37^\circ) \text{ V}}$$