
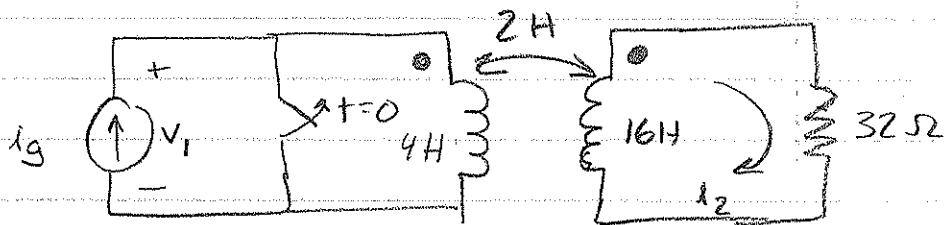


CIRCUITS II
Exam 1 Review

Problem 6-36

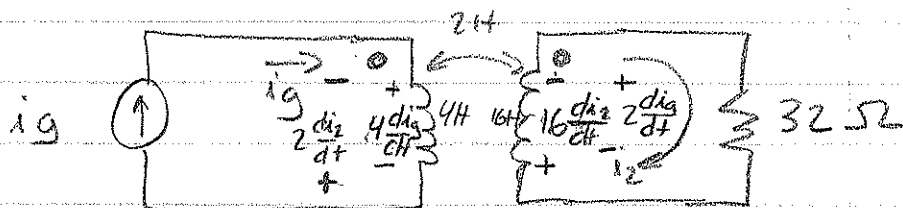

(a) Derive the differential Equation that governs the behavior of i_2



KVL (Right Circuit)

$$\boxed{16 \frac{di_2}{dt} - 2 \frac{di_g}{dt} + 32 i_2 = 0}$$

(b) Show if $i_g = 8 - 8e^{-t}$ A $t \geq 0$, then $i_2 = e^{-t} - e^{-2t}$ A satisfies the equation derived in (a)

$$\begin{aligned} & 16 \frac{d}{dt} (e^{-t} - e^{-2t}) - 2 \frac{d}{dt} (8 - 8e^{-t}) + 32(e^{-t} - e^{-2t}) \\ &= 16(-e^{-t} + 2e^{-2t}) - 2(8e^{-t}) + 32(e^{-t} - e^{-2t}) \\ &= -16e^{-t} + 32e^{-2t} - 16e^{-t} + 32e^{-t} - 32e^{-2t} = 0 \end{aligned}$$

(c) Find an expression for v_1

KVL (Left Circuit)

$$-v_1 + 4 \frac{di_g}{dt} - 2 \frac{di_2}{dt} = 0$$

$$\boxed{v_1 = 4 \frac{di_g}{dt} - 2 \frac{di_2}{dt}}$$

②

Problem 6.36

$$v_1 = 4(8e^{-t}) - 2(-e^{-t} + 2e^{-2t})$$


$$v_1 = 34e^{-t} - 4e^{-2t} \text{ V}$$

(d) Find the initial value of v_1

$$v_1(0) = 34 - 4 = 30 \text{ V}$$

3

Problem 9.78

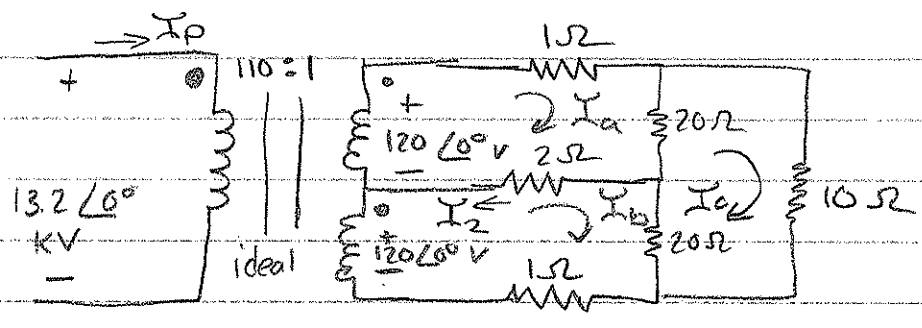

(a) Calculate the branch current in the 2Ω resistor

Mesh Current

Mesh (a)

$$-120 \angle 0^\circ + (1)I_a + (20)(I_a - I_c) + 2(I_a - I_b) = 0 \quad (1)$$

Mesh (b)

$$-120 \angle 0^\circ + 2(I_b - I_a) + 20(I_b - I_c) + 1(I_b) = 0 \quad (2)$$

Mesh (c)

$$20(I_c - I_a) + 10I_c + 20(I_c - I_b) = 0 \quad (3)$$

$$(1) \Rightarrow 23I_a - 2I_b - 20I_c = 120 \angle 0^\circ$$

$$(2) \Rightarrow -2I_a + 23I_b - 20I_c = 120 \angle 0^\circ$$

$$(3) \Rightarrow -20I_a - 20I_b + 50I_c = 0$$

Three Equations, 3 Unknowns


$$I_a = 24 \angle 0^\circ \text{ A}, \quad I_b = 24 \angle 0^\circ \text{ A}, \quad I_c = 19.2 \angle 0^\circ \text{ A}$$

$$I_2 = I_a - I_b = 24 \angle 0^\circ \text{ A} - 24 \angle 0^\circ \text{ A} = \boxed{0}$$

4

Problem 9.78

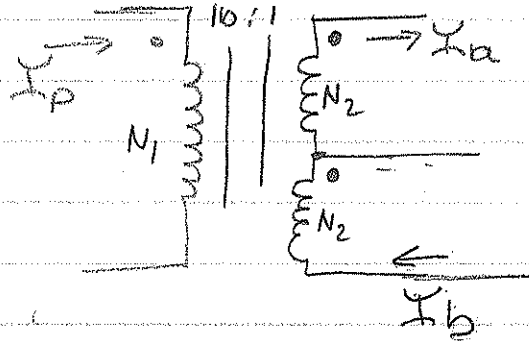(b) Calculate I_p , assuming $N_1 I_p = N_2 I_a + N_2 I_b$



$$N_1 I_p = N_2 I_a + N_2 I_b$$

$$I_p = \frac{N_2}{N_1} (I_a + I_b)$$


$$I_p = \frac{1}{110} (24 \angle 0^\circ + 24 \angle 0^\circ)$$

$$I_p = 0.436 \angle 0^\circ \text{ A}$$



5

Problem 10.12

$$i_g = 30 \cos 25,000t \text{ mA}$$

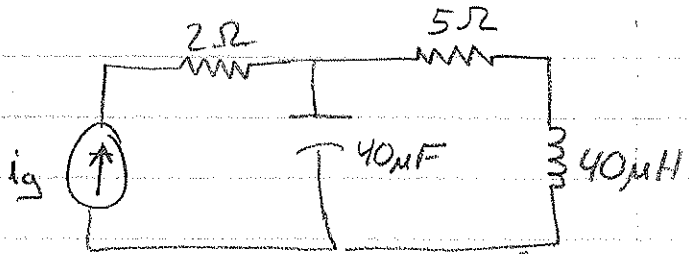
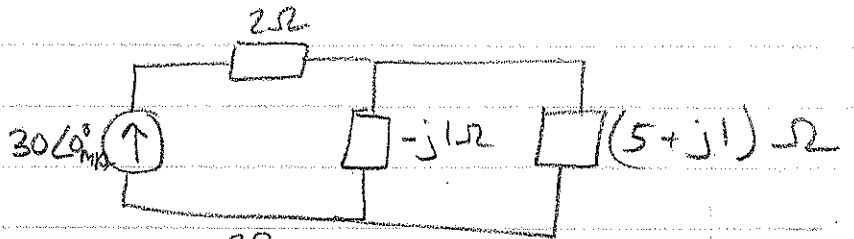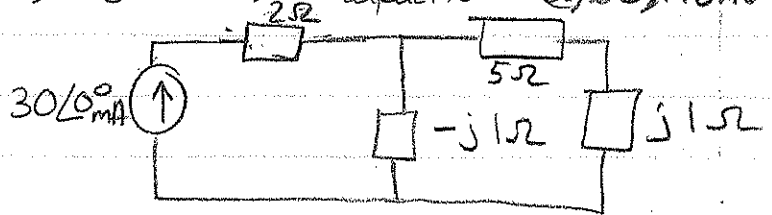
$$Z_{\text{inductor}} = j(25,000)(40 \times 10^{-6}) = j1 \Omega, \quad Z_{\text{capacitor}} = \left(\frac{-j}{25,000 \times 40 \times 10^{-6}} \right) = -j1 \Omega$$





$$Z_{\text{eq}} = \left(\frac{1}{-j1} + \frac{1}{5+j1} \right)^{-1}$$

$$= \left(j + \frac{5-j1}{26} \right)^{-1}$$

$$= \left(j + \frac{5}{26} - j\left(\frac{1}{26}\right) \right)^{-1} = \left(0.1923 + j0.9615 \right)^{-1}$$

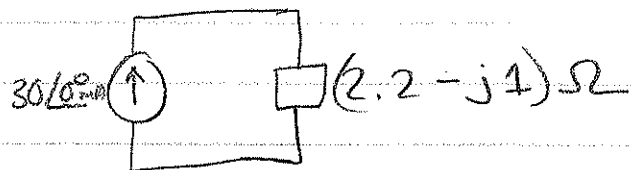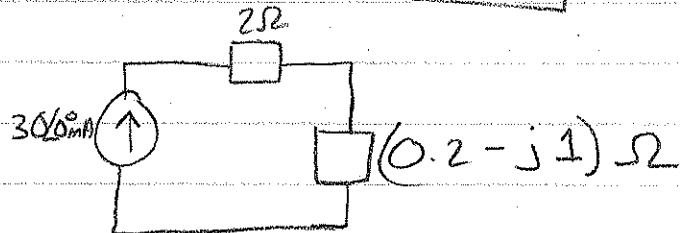
$$= \frac{0.1923 - j0.9615}{(0.1923^2 + 0.9615^2)} = (0.2 - j1) \Omega$$



Average Power \Rightarrow Real Power

$$P = \frac{1}{2} |I_m|^2 R$$

$$30 \angle 0^\circ \text{ mA}$$

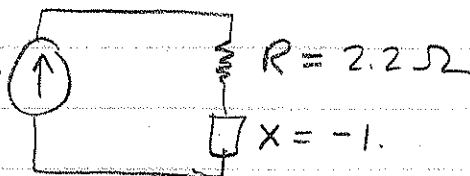


$$= \frac{1}{2} (30 \times 10^{-3} \text{ A})^2 (2.2 \Omega)$$

$$P = 9.9 \times 10^{-4} \text{ W} = \boxed{990 \mu\text{W}}$$

6

Problem 11.19

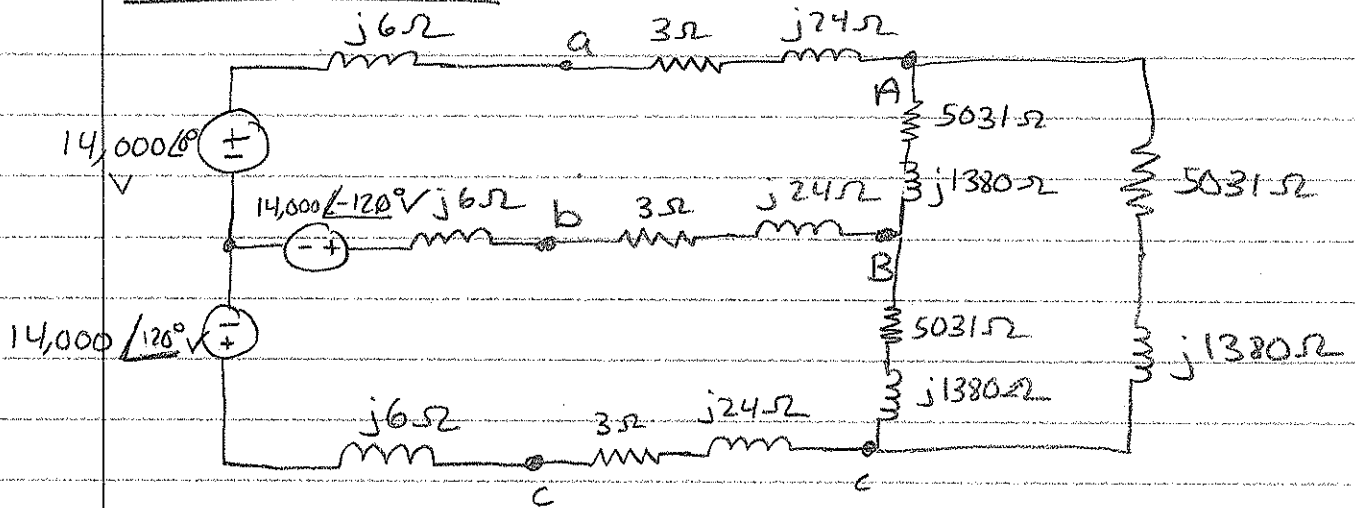


(a) Determine I_{aA} (rms)

Is it balanced? abc sequence, source impedances are equal
 Line " " " "
 Load " " " "
 ⇒ Yes

WYE-to-DELTA Circuit

$$Z_Y = \frac{Z_\Delta}{3} = \frac{5031\Omega + j1380\Omega}{3} = (1677 + j460)\Omega$$

a-phase equivalent

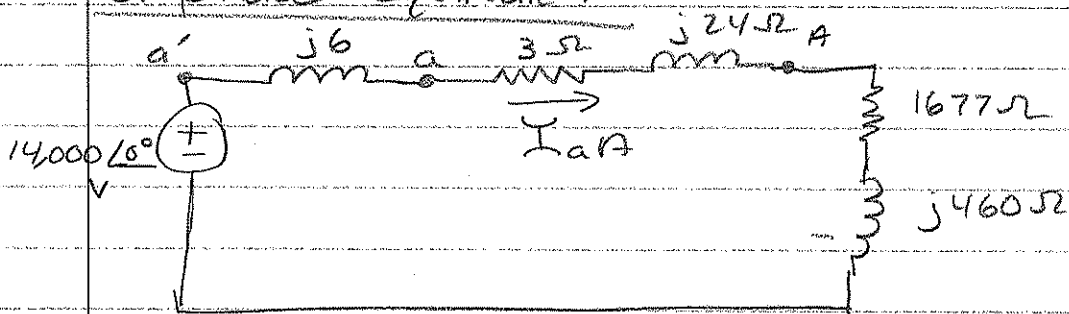

$$I_{aA} = \frac{14,000 \angle 0^\circ \text{ V}}{(j6)\Omega + (3 + j24)\Omega + (1677 + j460)\Omega}$$

$$I_{aA} = \frac{14,000 \angle 0^\circ \text{ V}}{1680 + j490 \Omega} = \boxed{8 \angle -16.26^\circ \text{ A}}$$

$$I_{bB} = 8 \angle -16.26 - 120^\circ = \boxed{8 \angle -136.26^\circ \text{ A}}$$

$$I_{cC} = 8 \angle -16.26 + 120^\circ = \boxed{8 \angle 103.74^\circ \text{ A}}$$

7

Problem 11.14

$$I_{CC} = \sqrt{3} \angle -30^\circ I_{CA}$$

$$I_{CA} = \frac{I_{CC}}{\sqrt{3} \angle -30^\circ} = \frac{8 \angle 103.74^\circ}{\sqrt{3} \angle -30^\circ} = 4.62 \angle 133.74^\circ \text{ A}$$

$$I_{CA} (\text{rms}) = \frac{4.62}{\sqrt{2}} \angle 133.74^\circ \text{ A} = \boxed{3.266 \angle 133.74^\circ \text{ A}}$$

(b) What percentage of the ^{average} power delivered by the three-phase source is dissipated in the three phase load

Source

$$S = -\frac{1}{2} V I_{aA}^* = -\frac{1}{2} (14,000 \angle 0^\circ \text{ V}) (8 \angle 16.26^\circ \text{ A})$$
$$= -(56,000 \angle 16.26^\circ) \text{ VA}$$

$$S = -(53,760 + j15,680) \text{ VA}$$

$$\boxed{P_{\text{del}} = 53.76 \text{ kW}}$$

Load

$$P_{\text{abs}} = \frac{1}{2} |I_{aA}|^2 R = \frac{1}{2} (8)^2 (1677) = 53664 \text{ W}$$

$$\boxed{P_{\text{abs}} = 53.66 \text{ kW}}$$

$$\boxed{\% = \frac{53.66 \text{ kW}}{53.76 \text{ kW}} \times 100\% = 99.8\%}$$

①

CIRCUITS II
EXAM 2 Review

Find the Laplace Transform of :

$$\begin{aligned} f(t) &= -20 e^{-5t} u(t-2) \\ &= -20 e^{-5[(t-2)+2]} u(t-2) \\ &= -20 e^{-5(t-2)} (e^{-10}) u(t-2) \end{aligned}$$

$$\mathcal{L}\{f(t-a)u(t-a)\} = e^{-as} F(s)$$

$$F(s) = \mathcal{L}\{f(t)\} = \mathcal{L}\{e^{-5t}\} = \frac{1}{s+5}$$

$$-20e^{-10} \mathcal{L}\{e^{-5(t-2)} u(t-2)\} = -20e^{-10} e^{-2s} \left(\frac{1}{s+5}\right)$$

$$= \boxed{\frac{(-9.08 \times 10^{-4}) e^{-2s}}{s+5}}$$

$$\mathcal{L}\left\{\frac{d}{dt} \cos \omega t\right\} \quad f(0^-) = 0$$

$$= sF(s) - f(0^-)$$

$$= s \left(\frac{s}{s^2 + \omega^2}\right) - 0 = \boxed{\frac{s^2}{s^2 + \omega^2}}$$

$$\mathcal{L}\{\sin(\omega t + \theta)\}$$

$$\sin(\omega t + \theta) = \sin \omega t \cos \theta + \sin \theta \cos \omega t$$

$$\cos \theta \mathcal{L}\{\sin \omega t\} + \sin \theta \mathcal{L}\{\cos \omega t\}$$

$$\frac{\omega \cos \theta}{s^2 + \omega^2} + \frac{s(\sin \theta)}{s^2 + \omega^2} = \boxed{\frac{\omega \cos \theta + s(\sin \theta)}{s^2 + \omega^2}}$$

2

$$F(s) = \frac{24s^2 + 10s + 5}{s(s^2 + 5s + 6)} = \frac{25s^2 + 10s + 5}{s(s+3)(s+2)}$$

$$\frac{25s^2 + 10s + 5}{s(s+3)(s+2)} = \frac{K_1}{s} + \frac{K_2}{s+3} + \frac{K_3}{s+2}$$

$$K_1 = \frac{25s^2 + 10s + 5}{\cancel{s}(s+3)(s+2)} \Big|_{s=0} = \frac{5}{5} = 1$$

$$K_2 = \frac{25s^2 + 10s + 5}{s\cancel{(s+3)}(s+2)} \Big|_{s=-3} = \frac{25(9) + 10(-3) + 5}{(-3)(-3+2)} = 66.67$$

$$K_3 = \frac{25s^2 + 10s + 5}{s(s+3)\cancel{(s+2)}} \Big|_{s=-2} = \frac{25(4) + 10(-2) + 5}{(-2)(-2+3)} = -42.5$$

$$F(s) = \frac{1}{s} + 66.67 \left(\frac{1}{s+3} \right) - 42.5 \left(\frac{1}{s+2} \right)$$

$$f(t) = \left[1 + 66.67 e^{-3t} - 42.5 e^{-2t} \right] u(t)$$

$$F(s) = \frac{6s + 1}{s^2 + 2s + 8} = \quad s = \frac{-2 \pm \sqrt{4 - 32}}{2} = -1 \pm j5.29$$

$$\frac{6s + 1}{s^2 + 2s + 8} = \frac{K}{(s+1-j5.29)} + \frac{K^*}{(s+1+j5.29)}$$

$$K = \frac{6s + 1}{\cancel{(s+1-j5.29)}(s+1+j5.29)} \Big|_{s=-1+j5.29}$$

$$= \frac{6(-1+j5.29)}{(j10.58)} = \frac{-j6 - 31.74}{-10.58}$$


$$K = -3 + j0.567 \Rightarrow 3.05 / 10.7^\circ$$

$$f(t) = 2(3.05) e^{-t} \cos(5.29t + 10.7^\circ)$$

3

Drill Exercise 8.7

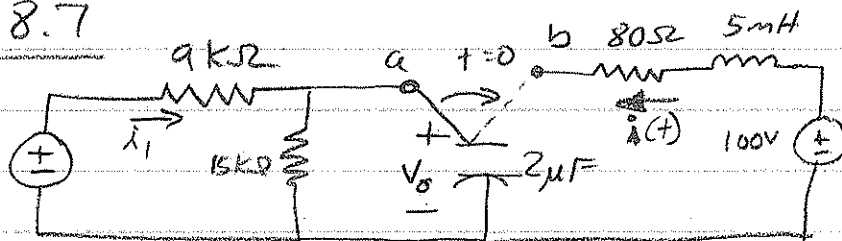Switch has been in position a for a long time



Find $i(t)$

No current in the capacitor

$$i_1 = \frac{80V}{9k\Omega + 15k\Omega} = 3.33 \text{ mA}$$


KVL

$$-80 + (9k\Omega)(3.33) + v_0 = 0$$

$$v_0 = 50V$$

S-Domain for $t \geq 0$

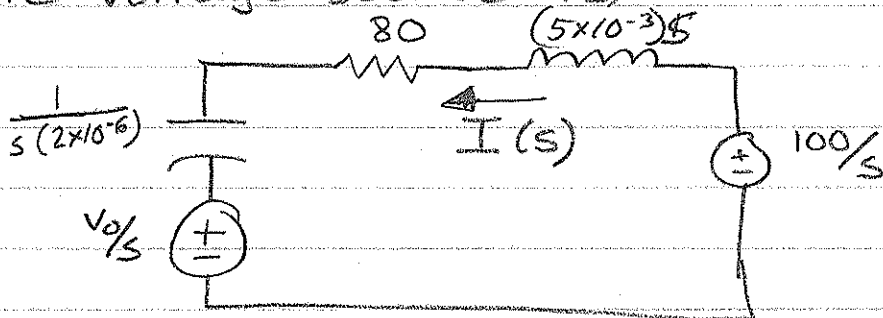Polarity of v_0 tells you what the polarity of the ^{equivalent} voltage source is.



KVL

$$\frac{50}{s} + \frac{5 \times 10^5}{s} I + 80I + (5 \times 10^{-3}) s I - \frac{100}{s} = 0$$

$$50 + 5 \times 10^5 I + 80sI + (5 \times 10^{-3}) s^2 I - 100 = 0$$

$$I (5 \times 10^{-3} s^2 + 80s + 5 \times 10^5) = +50$$

$$I = \frac{450}{(5 \times 10^{-3}) s^2 + 16000s + 100 \times 10^6}$$

$$s_{1,2} = \frac{-16000 \pm \sqrt{(16000)^2 - 4(100 \times 10^6)}}{2} = -8000 \pm j6000$$

④

$$\frac{+10000}{(s+8000-j6000)(s+8000+j6000)} = \frac{K}{s+8000-j6000} + \frac{K^*}{s+8000+j6000}$$

$$K = \frac{10,000}{(s+8000-j6000)(s+8000+j6000)} \Big|_{s=-8000+j6000}$$

$$K = \frac{10,000}{j12,000} = \frac{-j10,000}{12,000} = -j0.833$$

$$K = 0.833 \angle -90^\circ$$

$$i(t) = [2(0.833) e^{-8000t} \cos(6000t - 90^\circ)] u(t) \text{ A}$$

$$i(t) = [1.67 e^{-8000t} \sin(6000t)] u(t) \text{ A}$$

CIRCUITS II
REVIEW \Rightarrow EXAM 3

①

Drill Exercise 14.2

Given
Series \checkmark RL Low-Pass Filter with cutoff
frequency = 2 kHz, $R = 5 \text{ k}\Omega$

(a) Compute L
Standard Form

$$\omega_c = R/L$$

$$(2\pi)(2000 \text{ Hz}) = \frac{5000 \Omega}{L}$$

$$L = 0.4 \text{ H} = \boxed{400 \text{ mH}}$$

Find
(b) $|H(j\omega)|$ at 50 kHz

$$H(s) = \frac{\omega_c}{s + \omega_c}$$

$$H(j\omega) = \frac{\omega_c}{j\omega + \omega_c}$$

$$|H(j\omega)| = \frac{\omega_c}{\sqrt{\omega^2 + \omega_c^2}}$$

$$\omega_c = (2\pi)(2000 \text{ Hz}) = 12,566 \text{ rad/s}$$

$$|H(j\omega)| = \frac{12,566 \text{ rad/s}}{\sqrt{[(2\pi)(50,000 \text{ Hz})]^2 + (12,566 \text{ rad/s})^2}}$$

$$|H(j\omega)| = 0.04$$

(c) Find $\theta(j\omega)$ @ 50 kHz

$$\theta(j\omega) = -\tan^{-1}\left(\frac{\omega L}{R}\right)$$


$$= -\tan^{-1}\left(\frac{(2\pi)(50,000)(0.4 \text{ H})}{5000 \Omega}\right)$$

$$\theta(j\omega) = \boxed{-87.72^\circ}$$

(2)

CIRCUITS II EXAM 3 REVIEW

Drill Exercise 14.5


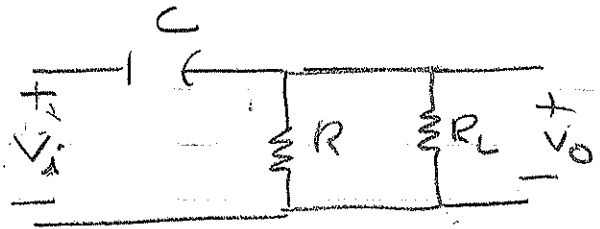


Derive the transfer function for V_o

$$\frac{1}{R_{eq}} = \frac{1}{R} + \frac{1}{R_L}$$

$$\frac{1}{R_{eq}} = \frac{R_L + R}{R R_L}$$

$$R_{eq} = \frac{R R_L}{R + R_L}$$

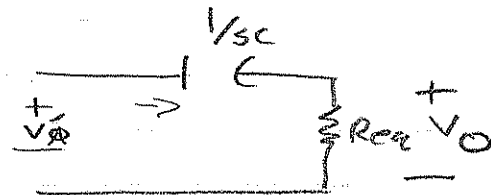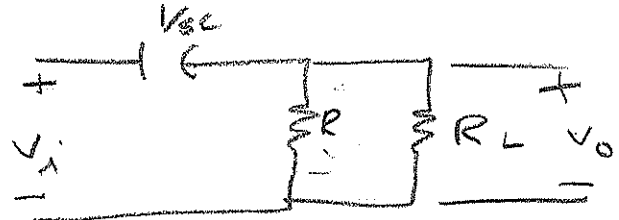

$$-V_i + \left(\frac{1}{sC} + \frac{R R_L}{R + R_L} \right) I = 0$$

$$I = \frac{V_i}{\left(\frac{1}{sC} + \frac{R R_L}{R + R_L} \right)}$$

$$V_o = \frac{R R_L}{R + R_L} \left(\frac{V_i}{\frac{1}{sC} + \frac{R R_L}{R + R_L}} \right)$$

$$H(s) = \frac{R R_L}{R + R_L} \left(\frac{s}{\frac{1}{C} + s \left(\frac{R R_L}{R + R_L} \right)} \right)$$

$$H(s) = \frac{\left(\frac{R R_L}{R + R_L} \right) s}{\frac{R R_L}{R + R_L} \left(s + \frac{(R + R_L)}{R R_L C} \right)}$$


$$H(s) = \frac{s}{s + \underbrace{\left(\frac{R + R_L}{R_L} \right) \frac{1}{RC}}_{\omega_c}}$$

$$\omega_c = \frac{R + R_L}{R_L} \left(\frac{1}{RC} \right)$$


3

CIRCUITS II
EXAM 3 REVIEW

Problem 14.8

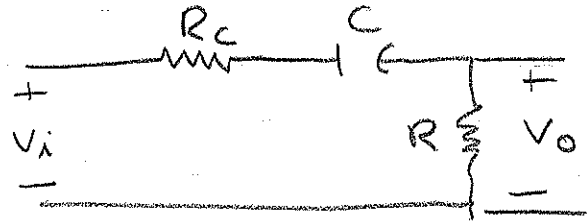

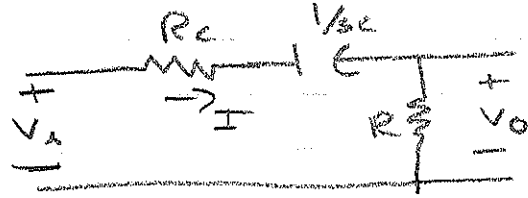(a) Derive the transfer function for V_o .



$$-V_i + IR_c + \frac{1}{sC} I + IR = 0$$

$$I = \frac{V_i}{R + R_c + \frac{1}{sC}} \quad V_o = IR$$

$$H(s) = \frac{R}{(R + R_c) + \frac{1}{sC}}$$

$$H(s) = \frac{sR}{s(R + R_c) + \frac{1}{C}}$$

$$H(s) = \frac{s \left(\frac{R}{R + R_c} \right)}{s + \frac{1}{(R + R_c)C}}$$

$$H(s) = \left(\frac{R}{R + R_c} \right) \frac{s}{s + \frac{1}{(R + R_c)C}}$$

(b) At what Frequency will the magnitude of $H(j\omega)$ be a maximum

(c) What is the $f = \infty$ maximum magnitude of $H(j\omega)$

$$H(j\omega) = \left(\frac{R}{R + R_c} \right) \frac{j\omega}{j\omega + \frac{1}{(R + R_c)C}}$$

$$|H(j\omega)| = \left(\frac{R}{R + R_c} \right) \frac{\omega}{\sqrt{\omega^2 + \left[\frac{1}{(R + R_c)C} \right]^2}} = \left(\frac{R}{R + R_c} \right) \frac{\omega}{\omega \sqrt{1 + \left[\frac{1}{\omega(R + R_c)C} \right]^2}}$$

4

CIRCUITS II
EXAM 3 REVIEW

$$|H(j\omega)| = \frac{R}{R+R_c} \frac{1}{\sqrt{1 + \frac{1}{\omega^2} \left[\frac{1}{(R+R_c)C} \right]^2}}$$

$$\lim_{\omega \rightarrow \infty} = \frac{R}{R+R_c} = H_{\max}$$

(c) What is ω_c

$$\omega_c = \frac{1}{(R+R_c)C}$$

5

CIRCUITS II
EXAM 3 REVIEW


Drill Exercise 14.6

Determine values for R and L such that the center

frequency = 12 kHz, and the quality factor = 6

Use 0.1 μ F capacitors.

Standard RLC Bandpass Filter

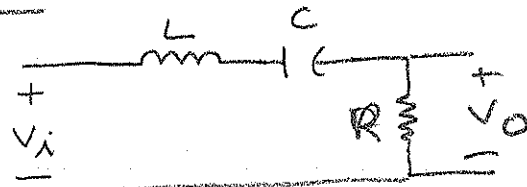

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

$$(2\pi)(12,000 \text{ Hz}) = \sqrt{\frac{1}{L(0.1 \times 10^{-6} \text{ F})}}$$

$$L = 1.76 \text{ mH}$$

$$Q = \sqrt{\frac{L}{CR^2}}$$

$$6 = \sqrt{\frac{1.76 \times 10^{-3} \text{ H}}{(0.1 \times 10^{-6} \text{ F})(R^2)}}$$

$$R = 22.1 \Omega$$

①

CIRCUITS II

EXAM 4 Review

Drill Exercise 15.4

Design a unity-gain ^{Active} bandpass filter with a center frequency of 200 Hz, and a bandwidth of 1000 Hz. Use 5 μ F capacitors

$$\omega_0 = 2\pi f_0 = 2\pi(200 \text{ Hz}) = 400\pi \text{ rad/s}$$

$$B = 2\pi(1000 \text{ Hz}) = 2000\pi$$

Need ω_{c1} & ω_{c2}

$$B = \omega_{c2} - \omega_{c1}$$

$$\boxed{\omega_{c2} - \omega_{c1} = 2000\pi} \quad (1)$$

$$\omega_0 = \sqrt{\omega_{c1} \omega_{c2}}$$

$$\omega_{c1} \omega_{c2} = 16 \times 10^4 \pi^2$$

$$\boxed{\omega_{c2} = \frac{16 \times 10^4 \pi^2}{\omega_{c1}}} \quad (2)$$

$$\frac{16 \times 10^4 \pi^2}{\omega_{c1}} - \omega_{c1} = 2000\pi$$

$$16 \times 10^4 \pi^2 - \omega_{c1}^2 = (2000\pi) \omega_{c1}$$

$$\omega_{c1}^2 + (2000\pi) \omega_{c1} - 16 \times 10^4 \pi^2 = 0$$

$$\omega_{c1} = \frac{-2000\pi \pm \sqrt{(2000\pi)^2 + (4)(16 \times 10^4 \pi^2)}}{2}$$

$$= -1000\pi \pm 3383.6$$

$$\boxed{\omega_{c1} = 242 \text{ rad/s}}$$

$$\boxed{\omega_{c2} = 6525.2 \text{ rad/s}}$$

$$\omega_{c2}/\omega_{c1} = 27$$

②

Drill Exercise 15.4


$$\frac{1}{R_L C_2} = \omega_{c2} \Rightarrow 6525.2 = \frac{1}{R_L (5 \times 10^{-6} \text{F})}$$

$$R_L = 30.65 \Omega$$

$$\frac{1}{R_H C_1} = \omega_{c1} \Rightarrow 242 = \frac{1}{R_H (5 \times 10^{-6} \text{F})}$$

$$R_H = 826.4 \Omega$$
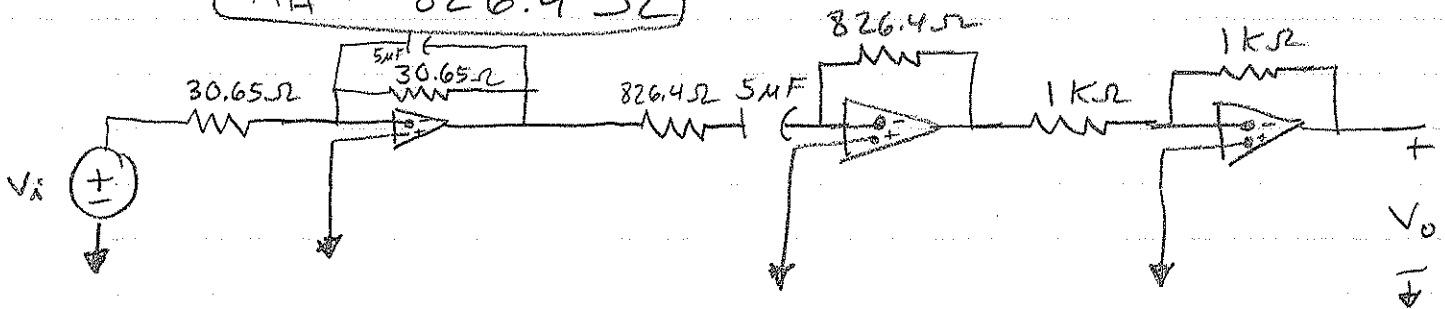
$$K=1 \Rightarrow R_F = R_i = 1 \text{ k}\Omega$$




3

Problem 16.8

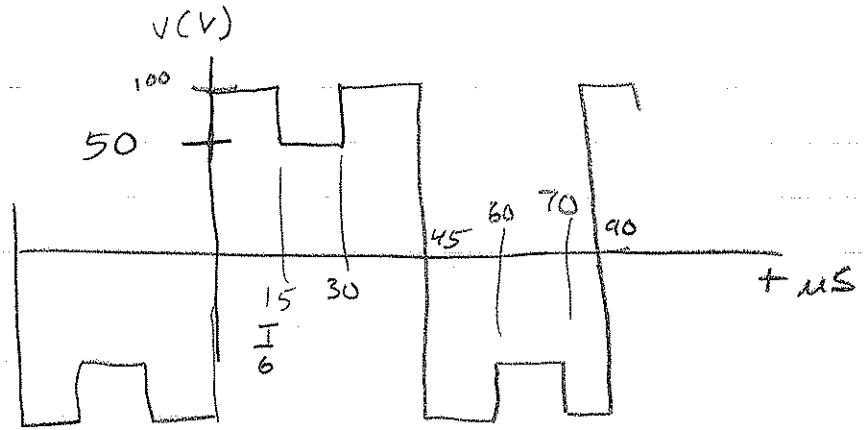(a) Find ω_0

$$T = 90 \mu\text{S}$$

$$f = \frac{1}{90 \times 10^{-6}} = 11,111 \text{ Hz}$$



$$\omega_0 = 2\pi (11,111 \text{ Hz}) = \boxed{69,813.2 \text{ rad/s}}$$

(b) Find $f_0 \Rightarrow f_0 = 11,111 \text{ Hz} = 11.1 \text{ kHz}$

(c) Find a_v

Even or odd
 Half Wave? Yes
 Quarter Wave? Yes

$$a_v = 0$$

(d) Find equations for a_k & b_k

$a_k = 0$ for all k , $b_k = 0$ for k even

$$b_k = \frac{8}{T} \int_0^{T/4} f(t) \sin(k\omega_0 t) dt \quad k \text{ odd} \quad \frac{15}{90} = \frac{1}{6} \quad T = 90 \mu\text{S}$$

$$\omega_0 = \frac{2\pi}{T}$$

$$= \frac{8}{T} \int_0^{T/6} 100 \sin\left(\frac{2\pi k t}{T}\right) dt + \frac{8}{T} \int_{T/6}^{T/4} 50 \sin\left(\frac{2\pi k t}{T}\right) dt$$

$$= -\left(\frac{800}{T}\right) \left(\frac{T}{2\pi k}\right) \left[\cos\left(\frac{2\pi k t}{T}\right)\right]_0^{T/6} - \left(\frac{400}{T}\right) \left(\frac{T}{2\pi k}\right) \left[\cos\left(\frac{2\pi k t}{T}\right)\right]_{T/6}^{T/4}$$

$$= -\frac{400}{k\pi} \left(\cos\left(\frac{k\pi}{3}\right) - 1\right) - \frac{200}{k\pi} \left(\cos\left(\frac{k\pi}{2}\right) - \cos\left(\frac{k\pi}{3}\right)\right)$$

$$b_k = \frac{400}{k\pi} - \frac{200}{k\pi} \cos\frac{k\pi}{3} = \boxed{\frac{200}{k\pi} (2 - \cos\left(\frac{k\pi}{3}\right))} \quad k \text{ odd}$$

4

Problem 16.8


(e) Find $v(t)$

$$v(t) = \sum_{n=1,3,5,\dots}^{\infty} \frac{200}{n\pi} \left(2 - \cos\left(\frac{n\pi}{3}\right) \right) \sin(n\omega_0 t)$$

$$v(t) = \frac{200}{\pi} \sum_{n=1,3,5}^{\infty} \frac{1}{n} \left[2 - \cos\left(\frac{n\pi}{3}\right) \right] \sin(n\omega_0 t)$$

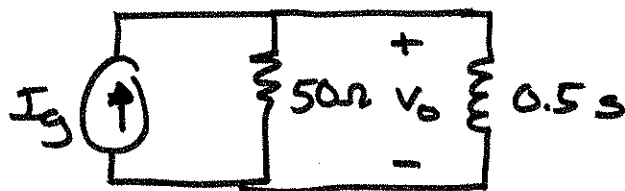17.21)

$$\frac{V_o}{50} + \frac{V_o}{0.5s} = I_g$$



$$V_o = \frac{I_g}{\left(\frac{1}{50} + \frac{2}{s}\right)}$$

$$H(s) = \frac{V_o}{I_g} = \frac{50s}{s+100}$$

$$H(j\omega) = \frac{j\omega 50}{j\omega + 100}$$

$$I_g(\omega) = \frac{4}{j\omega}$$

$$V_o(\omega) = H(j\omega) \cdot I_g(\omega) = \left(\frac{j\omega 50}{j\omega + 100}\right) \left(\frac{4}{j\omega}\right)$$

$$= \frac{200}{j\omega + 100}$$

$$V_o(t) = 200 e^{-100t} u(t) \text{ V}$$


18.7) $z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$

$$= (5 + 20) \Omega = \underline{25 \Omega}$$

$$z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = \frac{20 I_1}{I_1} = \underline{20 \Omega}$$

$$z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = 60 \Omega + 20 \Omega = \underline{80 \Omega}$$

$$z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = \frac{20 I_2}{I_2} = \underline{20 \Omega}$$

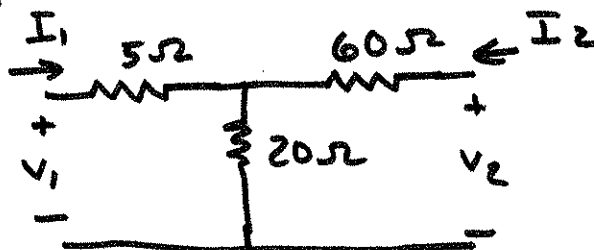

18.9 $a_{11} = \frac{V_1}{V_2} \Big|_{I_2=0} \quad V_2 = \frac{V_1}{R_1+R_3} R_3$

$a_{11} = \frac{R_1+R_3}{R_3} = 1 + \frac{R_1}{R_3} = 1.2 \Rightarrow \frac{R_1}{R_3} = 0.2$

$a_{21} = \frac{I_1}{V_2} \Big|_{I_2=0} ; V_2 = I_1 R_3$

$a_{21} = \frac{1}{R_3} = 20 \times 10^{-3} \Rightarrow R_3 = 50 \Omega$

$R_1 = 0.2 R_3 = 10 \Omega$

$a_{22} = -\frac{I_1}{I_2} \Big|_{V_2=0} \quad I_2 = \frac{-I_1 R_3}{R_3+R_2}$

$a_{22} = \frac{R_2+R_3}{R_3} = 1.4 \Rightarrow \frac{R_2}{R_3} = 0.4 \Rightarrow R_2 = 0.4 R_3 = 20 \Omega$

$R_1 = 10 \Omega, R_2 = 20 \Omega, R_3 = 50 \Omega$

18.12) Port 1 open ($I_1=0$) $\Rightarrow V_1=1mV, V_2=10V, I_2=200\mu A$
 Port 1 short-circuited ($V_1=0$) $\Rightarrow I_1=-0.5\mu A, I_2=80\mu A, V_2=5V$

a) $V_1 = a_{11} V_2 - a_{12} I_2$

$I_1 = a_{21} V_2 - a_{22} I_2$

$I_1=0 \Rightarrow 1 \times 10^{-3} = a_{11}(10) - a_{12}(200 \times 10^{-6}) \quad (1)$

$V_1=0 \Rightarrow 0 = a_{11}(5) - a_{12}(80 \times 10^{-6}) \quad (2)$

Solving \Rightarrow ~~$a_{11} = 5 \times 10^{-4}$~~ ~~$a_{12} = 0.025$~~

$a_{11} = -4 \times 10^{-4} \quad a_{12} = -25 \Omega$

$I_1=0 \Rightarrow 0 = a_{21}(10) - a_{22}(200 \times 10^{-6}) \quad (3)$

$V_1=0 \Rightarrow -0.5 \times 10^{-6} = a_{21}(5) - a_{22}(80 \times 10^{-6}) \quad (4)$

Solving $\Rightarrow a_{21} = -5 \times 10^{-7} \Omega^{-1} \quad a_{22} = -0.025$

$$\underline{18.12(b)} \quad b_{11} = \frac{v_2}{v_1} \Big|_{I_1=0} = \frac{10}{1 \times 10^{-3}} = 10,000$$

$$b_{12} = -\frac{v_2}{I_1} \Big|_{v_1=0} = \frac{-5}{-0.5 \times 10^{-6}} = 1 \times 10^7 \Omega$$

$$b_{21} = \frac{I_2}{v_1} \Big|_{I_1=0} = \frac{200 \times 10^{-6}}{1 \times 10^{-3}} = 0.2 \Omega^{-1}$$

$$b_{22} = -\frac{I_2}{v_1} \Big|_{I_1=0} = \frac{-80 \times 10^{-6}}{-0.5 \times 10^{-6}} = 160$$

$$\Delta b = \begin{vmatrix} 10,000 & 1 \times 10^7 \\ 0.2 & 160 \end{vmatrix} = -4 \times 10^5$$

$$h_{11} = \frac{b_{12}}{b_{11}} = \frac{1 \times 10^7}{10,000} = 1000 \Omega, \quad h_{12} = \frac{1}{b_{11}} = 1 \times 10^{-4}$$

$$h_{21} = -\frac{\Delta b}{b_{11}} = \frac{-(-4 \times 10^5)}{10,000} = 40 \Omega, \quad h_{22} = \frac{b_{21}}{b_{11}} = \frac{0.2}{10,000} = 2 \times 10^{-5} \Omega^{-1}$$

$$\Delta h = \begin{vmatrix} 1000 & 1 \times 10^{-4} \\ 40 & 2 \times 10^{-5} \end{vmatrix} = 0.016$$

$$a_{11} = -\frac{\Delta h}{h_{21}} = -\frac{0.016}{40} = \boxed{-4 \times 10^{-4}}$$

$$a_{12} = -\frac{h_{11}}{h_{21}} = \frac{-1000}{40} = \boxed{-25 \Omega}$$

$$a_{21} = -\frac{h_{22}}{h_{21}} = \frac{-2 \times 10^{-5}}{40} = \boxed{-5 \times 10^{-7} \Omega^{-1}}$$

$$a_{22} = -\frac{1}{h_{21}} = -\frac{1}{40} = \boxed{-0.025}$$