

Determine  $I_C$  and  $V_{CE}$  for each of the following circuits.

