

Topic

Kirchhoff's Laws

Governing Equations and Assumptions

KVL

KCL

$$v = iR$$

$$P = vi$$

$$P_{\text{resistor}} = i^2 R = \frac{v^2}{R}$$

Process

- ① Label all voltages and currents
Resistor \Rightarrow Passive Sign Convention



- ② Select Loops and/or nodes
 \Rightarrow Isolate unknowns if possible

- ③ Apply KVL and/or KCL
KVL \Rightarrow Select CW or CCW
(+) to (-) \Rightarrow positive voltage
(-) to (+) \Rightarrow negative voltage

KCL \Rightarrow Towards the node \Rightarrow negative current
Away from the node \Rightarrow positive current

- ④ Determine the power

$$i \xrightarrow{+} v - \Rightarrow p = vi$$

$$i \xrightarrow{-} v + \Rightarrow p = -vi$$

$p > 0 \Rightarrow$ Absorbed

$p < 0 \Rightarrow$ Developed