

Topic

Natural Response of RL and RC Circuits

Governing Equations and Assumptions

$$\begin{aligned} \underline{RL} \quad i(t) &= I_0 e^{-(R/L)t} \\ V_R(t) &= I_0 R e^{-(R/L)t} \\ P_R(t) &= I_0^2 R e^{-2(R/L)t} \\ W_R(t) &= \frac{1}{2} L I_0^2 (1 - e^{-2(R/L)t}) \end{aligned}$$

$$\begin{aligned} \underline{RC} \quad v(t) &= V_0 e^{-(1/RC)t} \\ i_R(t) &= \frac{V_0}{R} e^{-(1/RC)t} \\ P_R(t) &= \frac{V_0^2}{R} e^{-2(1/RC)t} \\ W_R(t) &= \frac{1}{2} C V_0^2 (1 - e^{-2(1/RC)t}) \end{aligned}$$

Circuit Analysis

Process

① Find I_0 or V_0 (After a "long" time)
 $\Rightarrow V_{\text{inductor}} = 0, i_{\text{capacitor}} = 0$

② Apply the equations for the RL or RC Circuit