

Topic

BJT's

Governing Equations and Assumptions

Equivalent Models and checks for the Active, Saturation and cutoff regions

Circuit Analysis

Process

- ① Assume a Region
- ② Analyze the circuit based on the assumption
- ③ Check the assumption
- ④ Repeat ①-③ if necessary, or solve for any other quantities