

Determine i_c & V_{CE}

