




Problem 2

Determine: - V_o



- i_o

- $P_{15\Omega}$

- P_{120V}

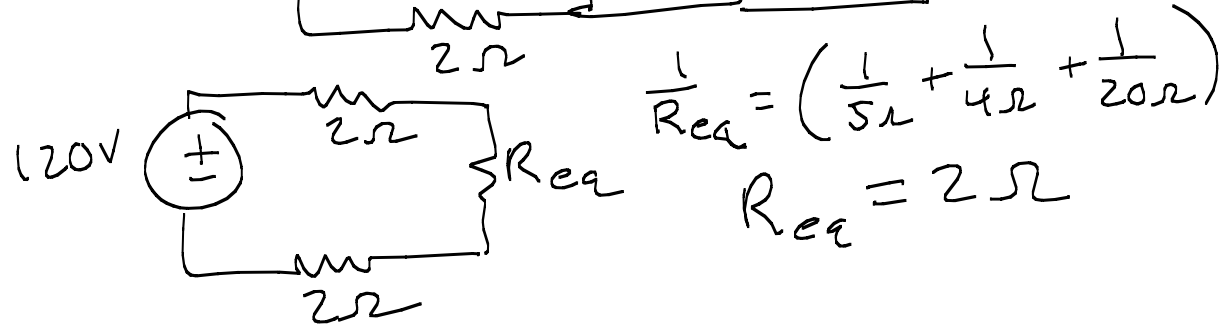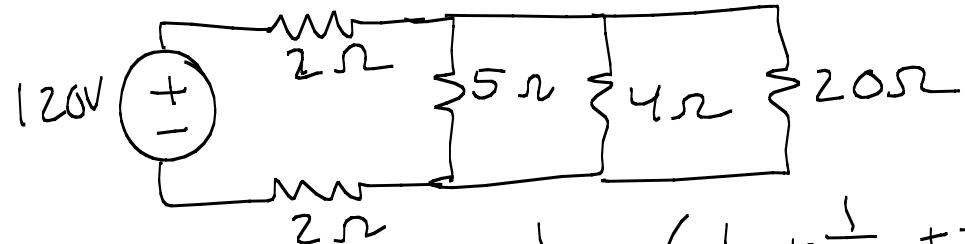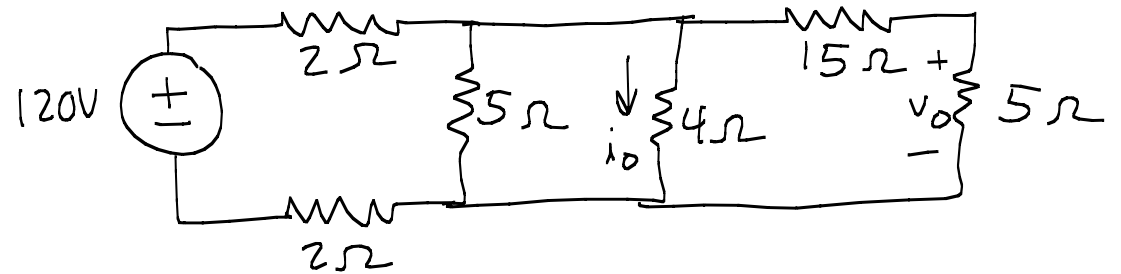

$$i_s = \frac{120V}{6\Omega} = 20A$$

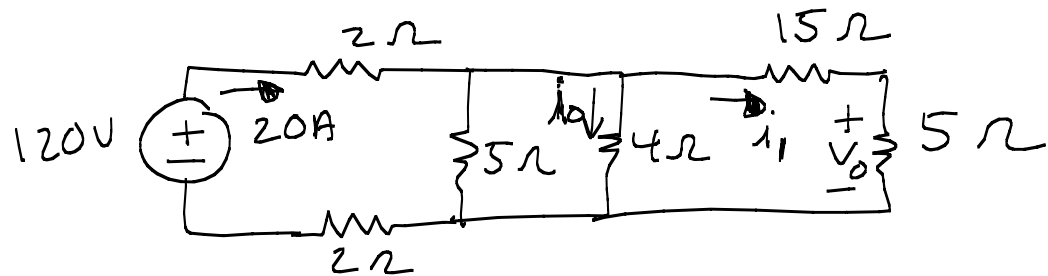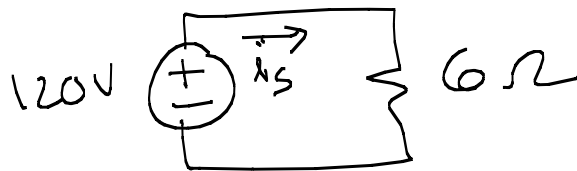

KVL (Left + Middle Perimeter, cw)

$$-120V + (20A)(2\Omega) + i_0(4\Omega) + (20A)(2\Omega) = 0$$

$$i_0 = 10A$$

KVL (Perimeter, cw)

$$-120V + (20A)(2\Omega) + i_1(15\Omega) + i_1(5\Omega) + (20A)(2\Omega) = 0$$

$$i_1 = 2A$$

$$V_o = (2A)(5\Omega) = 10V$$

$$P_{15\Omega} = i^2 R = (2A)^2(15\Omega) = 60W \text{ (abs)}$$

$$P_{120V} = -vi = -(120V)(20A) = -2400W \text{ (dev)}$$