
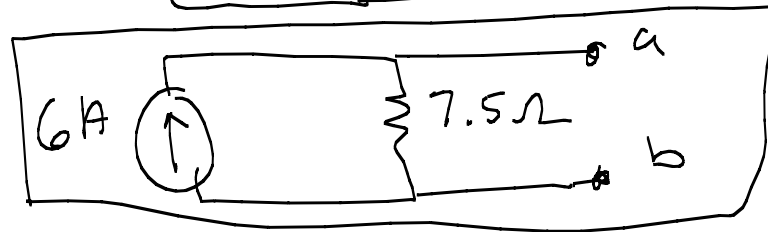
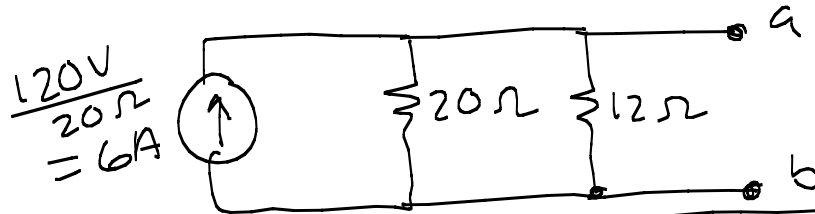
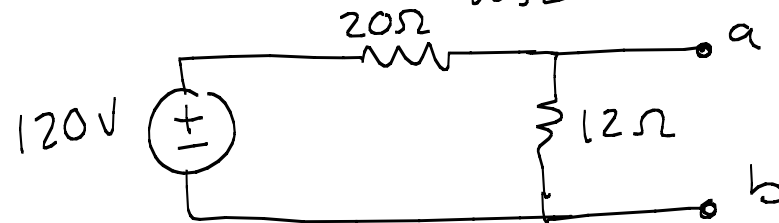
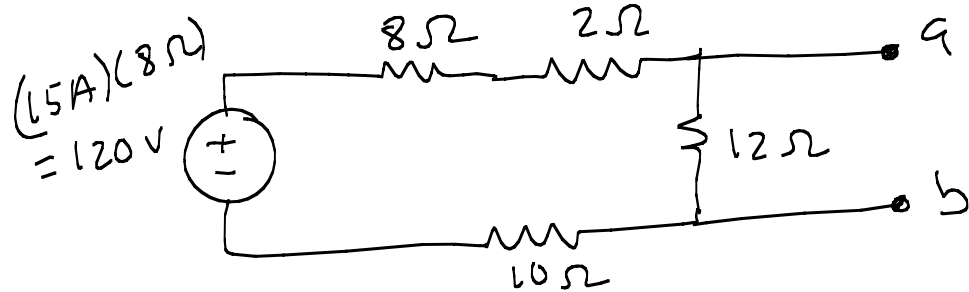


Problem 3

Determine: The Norton Equivalent

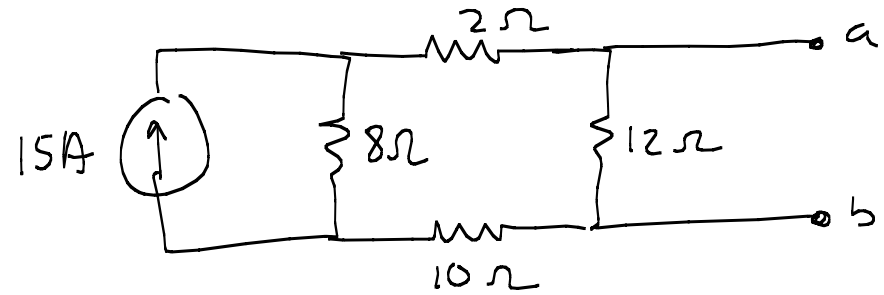

$$\left(\frac{1}{20\Omega} + \frac{1}{12\Omega} \right)^{-1} = 7.5\Omega$$