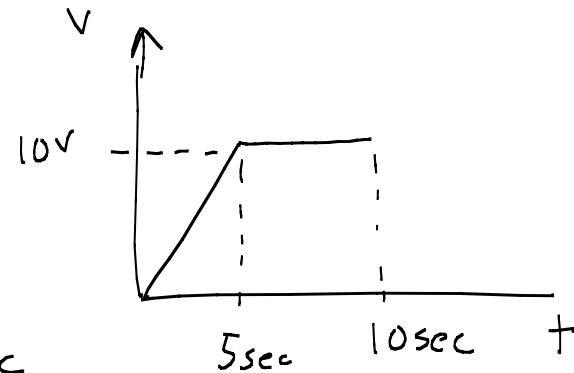


Problem 2

100mH Inductor

$$i(0) = 0$$

Determine: The current @ $t = 10\text{sec}$



$$i(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

$0 \leq t \leq 5\text{sec}$

$$i_1(t) = \frac{1}{0.1\text{H}} \int_0^t v_1(t) dt + i(0)$$

$$i_1(t) = 10 \int_0^t 2t dt + 0$$

$$\boxed{i_1(t) = 10t^2}$$

$$i(0) = 0$$
$$v_1(t) = 2t$$

$$\underline{5 \leq t \leq 10 \text{ sec}}$$

$$i_2(t) = \frac{1}{L} \int_5^t v_2(t) dt + i(5)$$

$$i_2(t) = \frac{1}{0.1} \int_5^t 10 dt + 250$$

$$i_2(t) = 10(10t - 50) + 250$$

$$\boxed{i_2(t) = 100t - 250}$$

$$\textcircled{a} \quad t = 10 \text{ sec}$$

$$i_2(10) = 100(10) - 250$$

$$\boxed{i_2(10) = 750 \text{ A}}$$

$$i_1(5) = 10(5)^2 = \underline{250 \text{ A}}$$

$$v_2(t) = 10$$