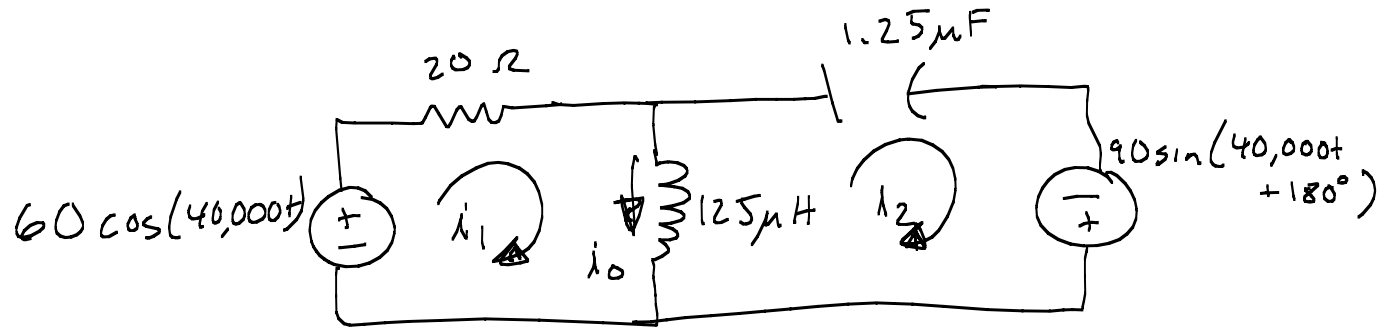


Problem 2

Determine i_o




$$60 \angle 0^\circ = 60 + j0$$

$$90 \sin(40,000t + 180) = 90 \cos(40,000t + 90^\circ)$$

$$90 \angle 90^\circ = j90$$

$$Z_L = j\omega L = j(40,000)(125 \times 10^{-6}) = j5 \Omega$$

$$Z_C = \frac{-j}{\omega C} = \frac{-j}{(40,000)(1.25 \times 10^{-6})} = -j20 \Omega$$

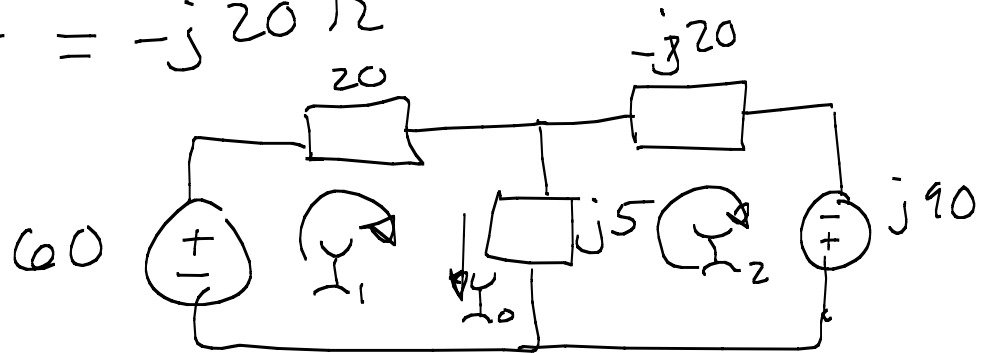

Mesh 1

$$-60 + 20I_1 + j5(I_1 - I_2) = 0$$

$$\boxed{I_1(20 + j5) - j5I_2 = 60}$$

Mesh 2

$$j5(I_2 - I_1) - j20(I_2) - j90 = 0$$

$$j5I_2 - j5I_1 - j20I_2 - j90 = 0$$

$$I_1 = -(18 + 3I_2)$$

$$-(18 + 3I_2)(20 + j5) - j5I_2 = 60$$

$$I_2 = \frac{-420 - j90}{60 + j120}$$

$$I_2 = -6.75 + j0.75 \text{ A}$$

$$I_1 = -(18 + 3I_2) = 2.25 - j2.25$$

$$I_0 = I_1 - I_2 = 9 - j3 = 9.49 \angle -18.43^\circ \text{ A}$$

$$i_0 = 9.49 \cos(40,000t - 18.43^\circ) \text{ A}$$