

KVL

$$-v_s + iR + L \frac{di}{dt} = 0$$

$$i(t) = \underbrace{\frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta) e^{-\frac{R}{L}t}}_{\text{Transient Component}} + \underbrace{\frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)}_{\text{Steady State}}$$

$\theta = \text{Angle whose tangent is } \frac{\omega L}{R}$

Transient Component

- Goes to zero after a "long" time

Steady State Solution

- Exists as long as the switch is closed
- Sinusoidal function
- Amplitude is different between the source and response
- The phase angle also is different
- The angular frequency is the same

Phasors

- Complex numbers that contain information about the amplitude and phase angle of a sinusoidal function
- Can use phasors as long as the angular frequencies are the same between the source and the response

Phasor Transform

$$\mathcal{P} \{ V_m \cos(\omega t + \phi) \} = V_m e^{j\phi}$$

$$e^{j\phi} = \cos \phi + j \sin \phi$$

$$\underline{V} = V_m e^{j\phi} = V_m \cos \phi + j V_m \sin \phi$$

Phasor

$$e^{j\phi} \equiv \angle \phi^\circ$$

$$v = 100 \cos(\omega t - 50^\circ)$$

$$\underline{V} = 100 \angle -50^\circ$$


Inverse Phasor Transform

$$\mathcal{P}^{-1}\{20 \angle 40^\circ\} = 20 \cos(\omega t + 40^\circ)$$

rms Value

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

The Phasor Transform for a Resistor

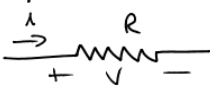If  $i(t) = I_m \cos(\omega t + \theta)$  

$$v(t) = I_m R \cos(\omega t + \theta)$$

$$\underline{I} = I_m \angle \theta^\circ$$


Phasor current

$$\underline{V} = I_m R \angle \theta^\circ$$

$$\underline{V} = R \underbrace{I_m \angle \theta^\circ}_I$$

$$\underline{V} = R \underline{I}$$

The Phasor Transform for an Inductor

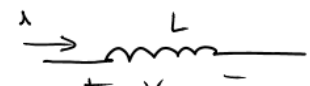If  $i(t) = I_m \cos(\omega t + \theta)$  

$$v(t) = L \frac{di}{dt}$$

$$= L I_m (-\omega \sin(\omega t + \theta))$$

$$= -\omega L I_m \sin(\omega t + \theta)$$

$$= -\omega L I_m [\cos(\omega t + \theta + 90^\circ)]$$


$$= \omega L I_m \cos(\omega t + \theta + 90^\circ)$$

$$\begin{aligned}
 & \left( \begin{array}{l} \underline{V} = \omega L I_m \angle \theta + 90^\circ \\ \underline{I} = I_m \angle \theta \end{array} \right) \\
 & \underline{V} = j\omega L \underbrace{I_m \angle \theta}_{\underline{I}} \\
 & \boxed{\underline{V} = j\omega L \underline{I}}
 \end{aligned}$$

$$\begin{aligned}
 & e^{j(\theta+90^\circ)} \\
 & = e^{j\theta} e^{j90} \\
 & = e^{j\theta} (\cos 90^\circ + j\sin 90^\circ) \\
 & = j e^{j\theta} = j \angle \theta
 \end{aligned}$$

The Phasor Transform for a Capacitor

If  $v(t) = V_m \cos(\omega t + \theta)$

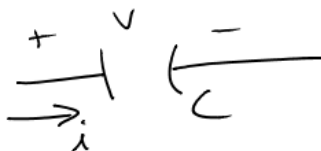

The diagram shows a capacitor symbol with a plus sign at the top and a minus sign at the bottom. A voltage  $v$  is indicated across it, and a current  $i$  is shown entering the positive terminal.

$$\begin{aligned}
 i(t) &= C \frac{dv}{dt} \\
 &= -C \omega V_m \sin(\omega t + \theta) \\
 &= -\omega C V_m (-\cos(\omega t + \theta + 90^\circ))
 \end{aligned}$$

$$i(t) = \omega C V_m \cos(\omega t + \theta + 90^\circ)$$

$$\underline{I} = \omega C V_m \angle \theta + 90^\circ$$

$$\underline{V} = V_m \angle \theta$$

$$\underline{I} = j\omega C \underbrace{V_m \angle \theta}_{\underline{V}}$$

$$\underline{I} = j\omega C \underline{V}$$

$$\boxed{\underline{V} = \frac{1}{j\omega C} \underline{I}}$$

Impedance

$$\bar{V} = \bar{Z} \bar{I}$$

└ Impedance

Resistor

$$\bar{z}_R = R$$

Inductor

$$\bar{z}_L = j\omega L$$

Capacitor

$$\bar{z}_C = \frac{1}{j\omega C} \left( \frac{j}{j} \right) \Rightarrow \bar{z}_C = \frac{-j}{\omega C}$$

$\bar{V} = \bar{Z} \bar{I} \Rightarrow$  All resistive circuit analysis  
methods apply to impedances