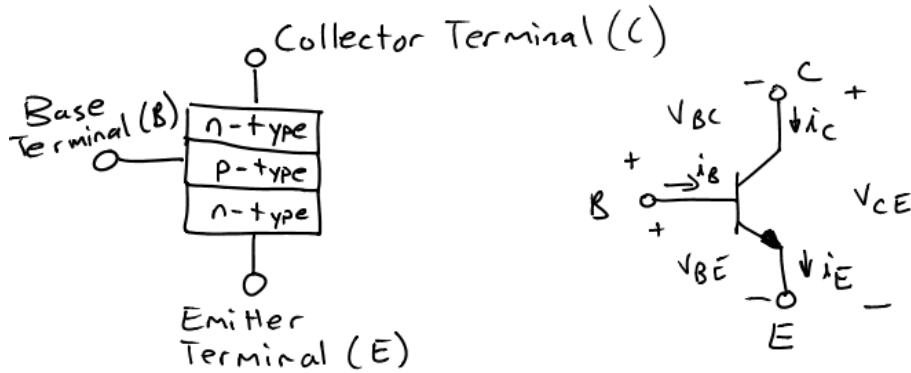


Bipolar Junction Transistors


- Used for amplifiers and switches
- Consists of three layers (two n-type layers and one p-type layer (npn transistor) or two p-type layers and one n-type layer (pnp transistor))
- Has three terminals (base, collector, and emitter)

npn BJT



- Two pn-junctions (Base-Emitter and Base-Collector)

- Characteristic Curves

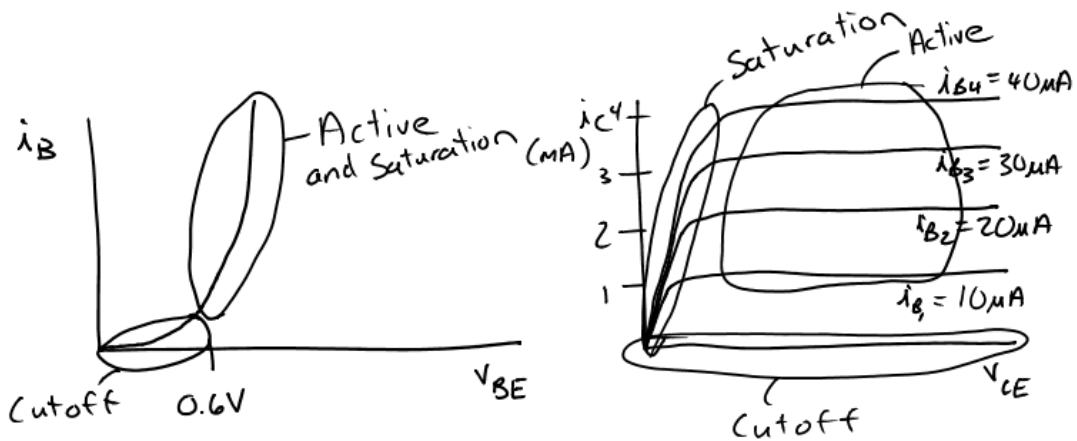

- Four possibilities for the states of the pn-junctions, but only three are used

	<u>Base-Emitter</u>	<u>Base-Collector</u>	<u>Region</u>
①	ON	OFF	Active
②	ON	ON	Saturation
③	OFF	OFF	Cutoff

ENGR 2219 – Linear Circuits I
 Electronics – Bipolar Junction Transistors (BJT's)


- For a pn-junction in the OFF state, the current is typically zero, but this not the case for the Active Region of a BJT due to the coupling effect of the shared p-type layer

- Amplification in the Active Region

$$i_C = \beta i_B \quad \text{Want } \beta \text{ to be large}$$

$$\alpha = \frac{i_C}{i_E} \quad 0.9 < \alpha < 0.999$$


- Load Line Analysis

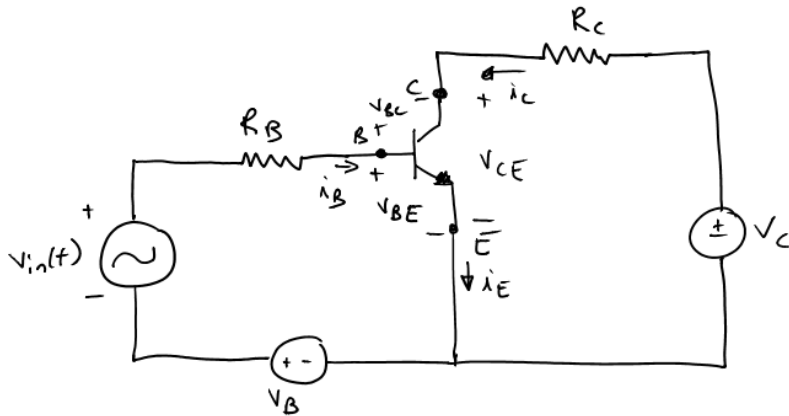

Input Circuit
 KVL (Left, cw)

$$-V_B - v_{in} + i_B R_B + V_{BE} = 0$$
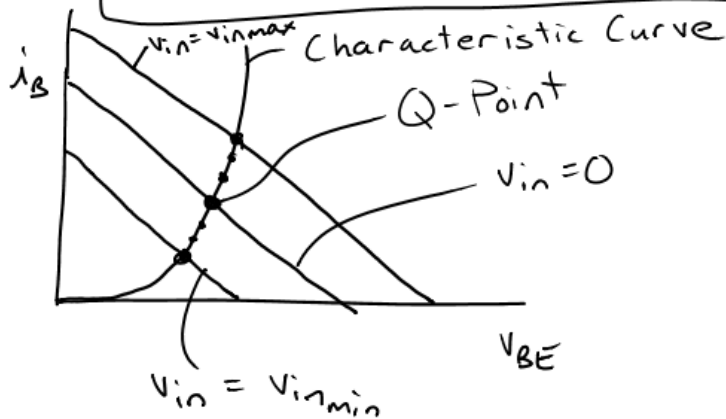
$$i_B = \frac{V_B + v_{in}}{R_B} - \frac{1}{R_B} V_{BE}$$




Output Circuit



KVL (Right, cw)

$$-V_{CE} - i_C R_C + V_C = 0$$


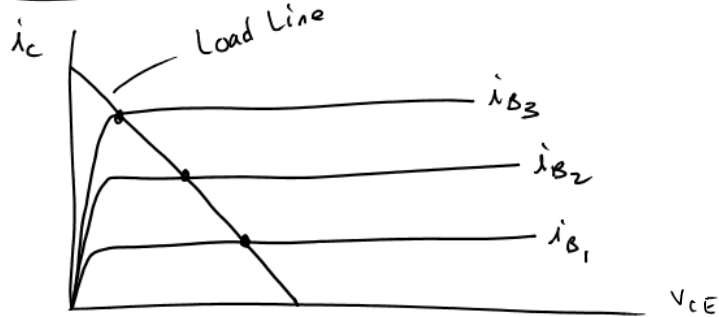
$$i_C = -\frac{1}{R} V_{CE} + \frac{V_C}{R}$$



npn BJT

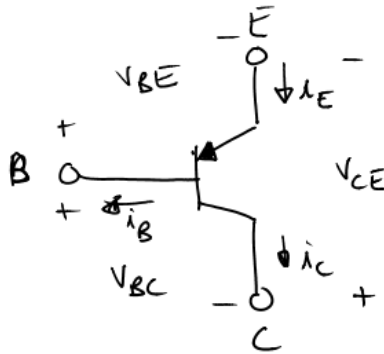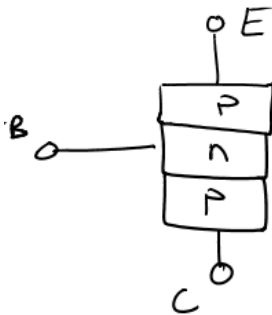
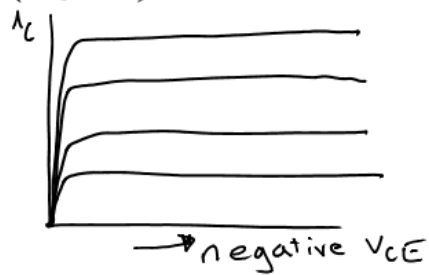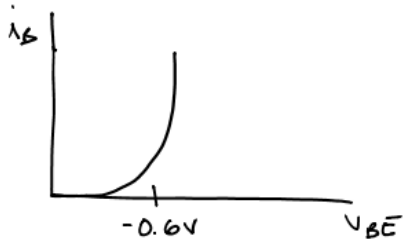
$$i_C = \beta i_B \text{ (Active Region)}$$




Large Signal DC Analysis of BJT's

- Replace the BJT with circuit elements that can be more readily analyzed
- Three regions: Active, Saturation, and Cutoff
- The ON/OFF voltages are modified versus a diode

Forward Bias: 0.7 V

Reverse Bias: 0.5 V

- Active Region (npn)

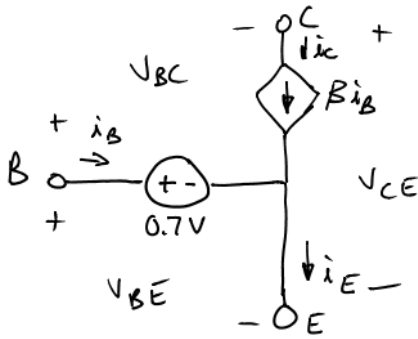

Check

$i_B > 0$
 $V_{CE} > 0.2V$


KVL (BJT)

$$V_{BC} + V_{CE} - V_{BE} = 0$$

$$V_{BC} = 0.7V - V_{CE}$$

For $V_{BC} < 0.5V$
 $\Rightarrow V_{CE} > 0.2V$


- Saturation Region (npn)

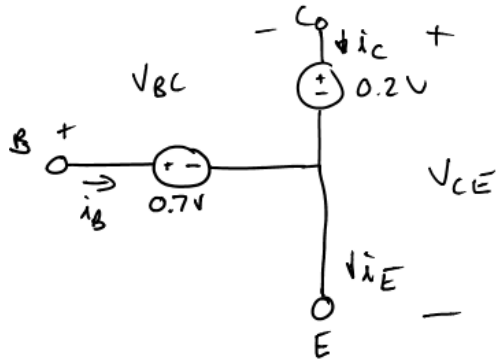

Checks

 $i_B > 0$
 $0 < i_C < \beta i_B$



- Cutoff Region (npn)

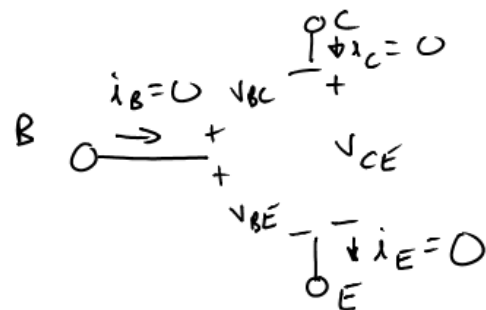



Checks

 $V_{BE} < 0.5V$
 $V_{BC} < 0.5V$



- Active Region (pnp)

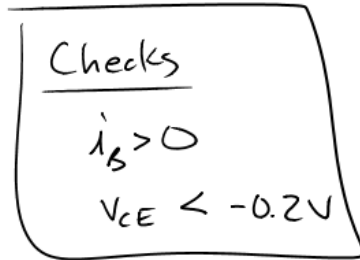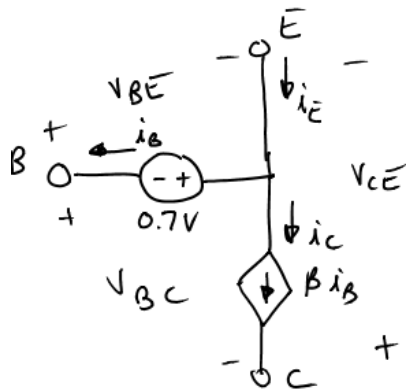

- Saturation Region (pnp)

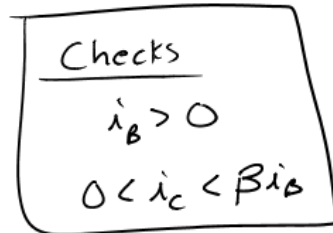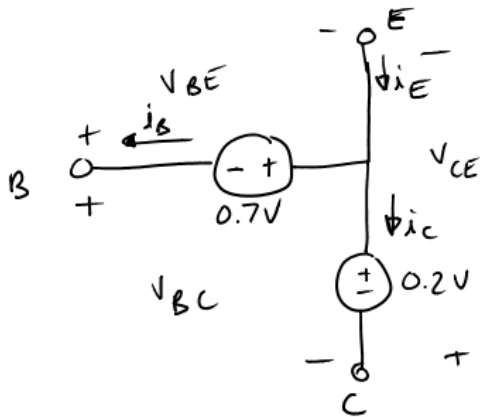

- Cutoff Region (pnp)

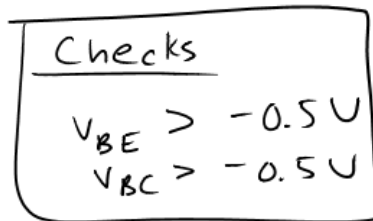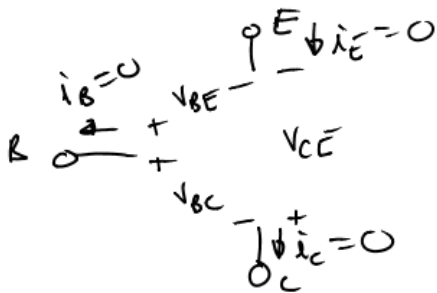

ENGR 2219 – Linear Circuits I
Electronics – Bipolar Junction Transistors (BJT's)