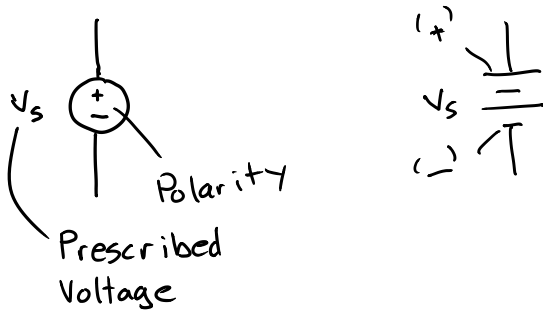



DC Voltage Source

- Prescribed voltage remains constant




DC Current Source

- Prescribed current is constant

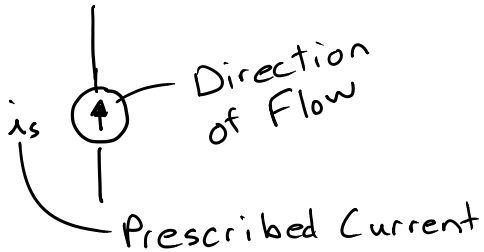


Dependent Source

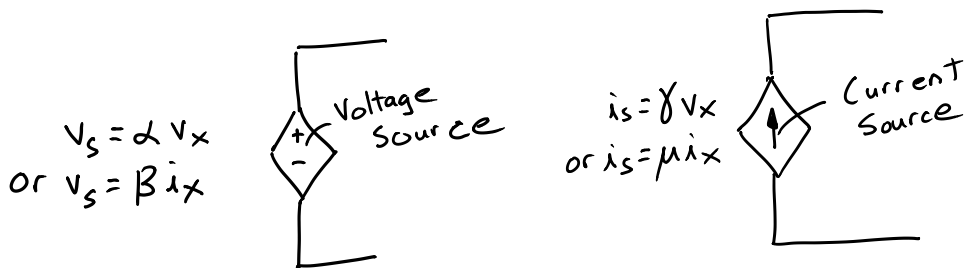The prescribed value depends on the value of voltage or current somewhere else in the circuit



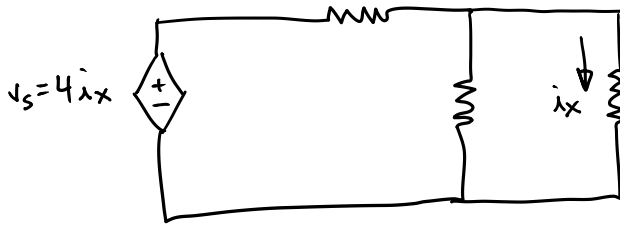$v_x, i_x \Rightarrow$ Values of voltage or current elsewhere
in the circuit
 $\alpha, \beta, \gamma, \mu \Rightarrow$ Multiplication Factors




If $i_x = 2\text{ A}$, then $v_s = (4)(2) = 8\text{ V}$

Ohm's Law

Resistor

- Impedes the flow of current

Symbol


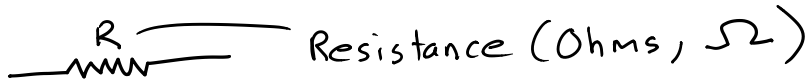


$$V = iR$$

voltage across the terminals of the resistor

Current flowing through the resistor

Sign Convention

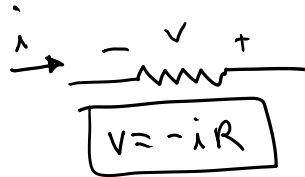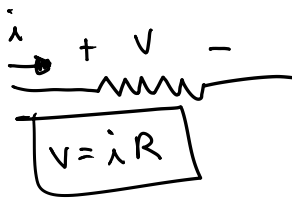

Power in a Resistor

$$P = v i \quad v = iR \quad \text{or} \quad i = \frac{v}{R}$$

$$P = i^2 R \quad \text{or} \quad P = \frac{v^2}{R}$$

$P > 0$ for a resistor \Rightarrow Resistors always absorb power


Conductance

$$G = \frac{1}{R} \quad \text{conductance}$$

Kirchhoff's Laws

Node

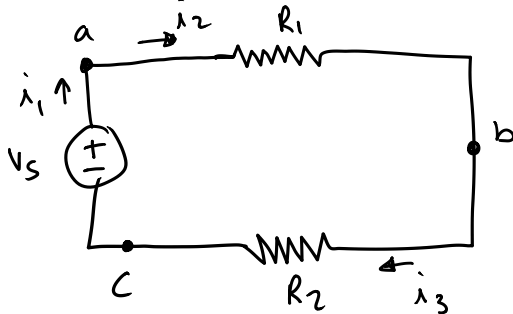- Point in a circuit that connects two or more circuit elements



a, b, c are Nodes
 $a \Rightarrow$ Connects v_s & R_1
 $b \Rightarrow$ Connects R_1 & R_2
 $c \Rightarrow$ Connects R_2 & v_s


Kirchhoff's Current Law (KCL)

- The sum of all currents entering and exiting a node is zero


Sign Convention

- If the current is directed towards the node: Negative in the KCL equation
- If the current is directed away from the node: Positive in the KCL equation

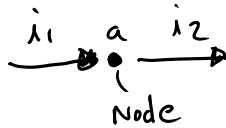Nodes Connecting only Two Circuit Elements



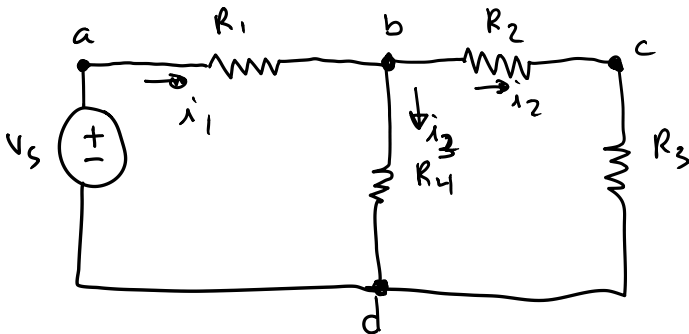KCL (a)
 $-i_1 + i_2 = 0$
 $i_1 = i_2$ (currents are equal)




$a, b, c,$ and d are nodes
 $a, c \Rightarrow$ Connect only two elements (KCL equation not needed)

Node b



KCL (b)
 $-i_1 + i_2 + i_3 = 0$

Node d

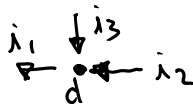


KCL (d)
 $i_1 - i_2 - i_3 = 0$ (Same as KCL(b) Equation)

ENGR 2219 – Linear Circuits I
Circuit Elements and Kirchhoff's Laws

Closed Path (Loop)

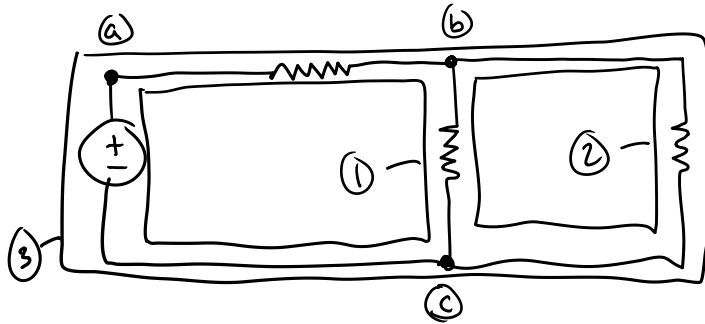- Start at one node in the circuit, and return to that same node
- Can't pass through any node more than once




a,b,c => Nodes
1,2,3 => Loops

Kirchhoff's Voltage Law

- Sum of all voltage drops ('+' to '-') or rises ('-' to '+') along a closed path (loop) is zero
- Go through the loop in a Clockwise (CW) or Counterclockwise (CCW) direction

Sign Convention

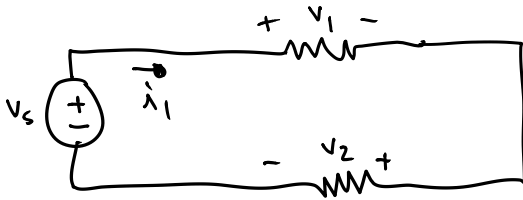- For a voltage drop: Positive in the KVL equation
- For a voltage rise: Negative in the KVL equation



KVL (CW)

$$-v_s + v_1 + v_2 = 0$$