

Diodes

- Have two terminals: Anode and Cathode
- Made up of a p-type (Anode) and n-type (Cathode) layer


Symbol



Characteristic Regions of a Diode


- **Forward Bias:** If $i_D > 0$, then current flows easily through the diode
- **Reverse Bias:** If $v_D < 0$, but not very large, then the current is very small
- **Reverse Breakdown:** If $v_D < 0$ and is very large, then the current becomes large and negative (OK if the heat does not get too high)

Graph of the Diode Characteristic Curve

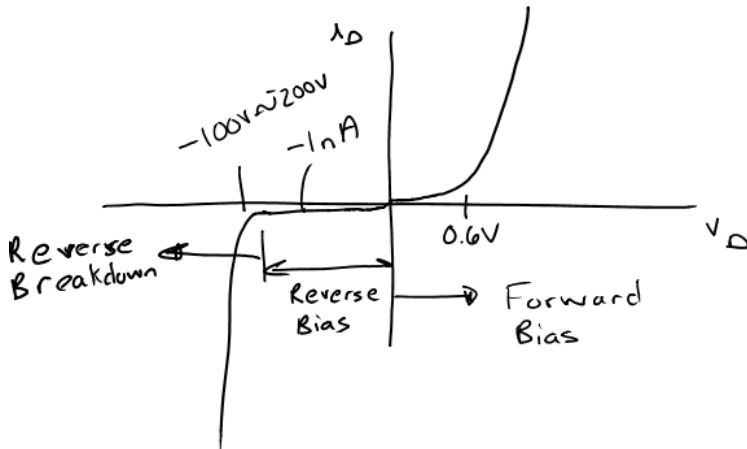


Zener Diode

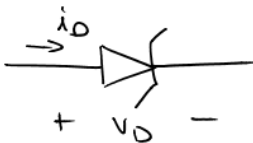- Intended to operate in the reverse breakdown region
- Voltages are much smaller (3, 5, 12... Volts)
- Used when a constant voltage is needed
- Has a different symbol



Load Line Analysis of a Diode

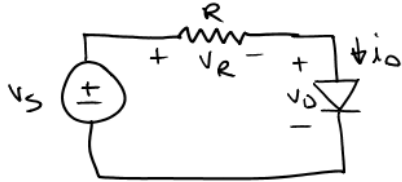- Places a diode in a basic circuit
- Use KVL to get the equation for the load line
- Use the load line and diode characteristic curve to solve for the operating voltage and current of the diode in the circuit




KVL (CW)


$$-v_s + v_R + v_D = 0$$

$$-v_s + i_D R + v_D = 0$$
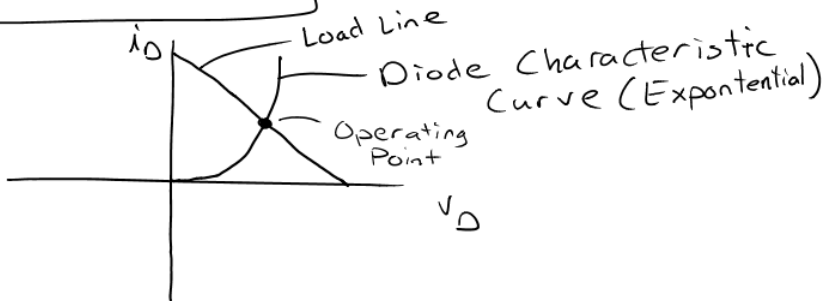
$$i_D = -\frac{1}{R}v_D + \frac{v_s}{R} \quad \text{Load Line}$$



The Ideal Diode Model

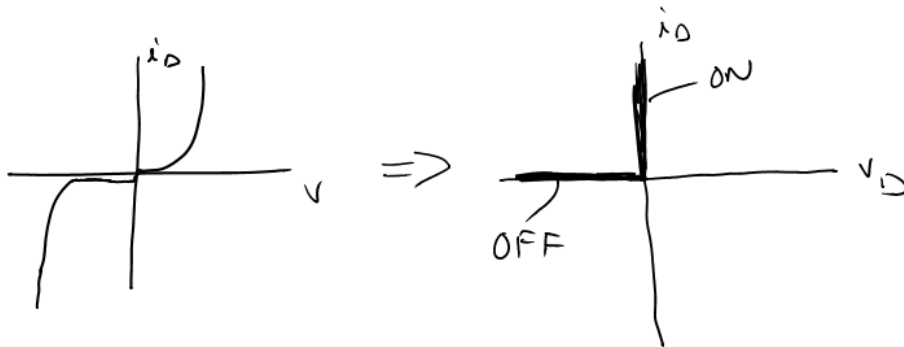

- Two operating states

ON: Perfect conductor ($v_D = 0$), $i_D > 0$
OFF: Open circuit ($i_D = 0$), $v_D < 0$

Assumed State of a Diode

- Either ON or OFF
- May not know the state in advance
- Assume a state, perform circuit analysis, and check if the assumed state is correct
 - ON: Set $v_D = 0$, Check if $i_D > 0$
 - OFF: Set $i_D = 0$, Check if $v_D < 0$
- For multiple diode circuits, all diodes must pass the checks for the assumed state to be correct


Diode Applications

Rectifiers

- Used to convert AC to DC
- AC: Not constant (sine wave)



- Half-Wave Rectifier

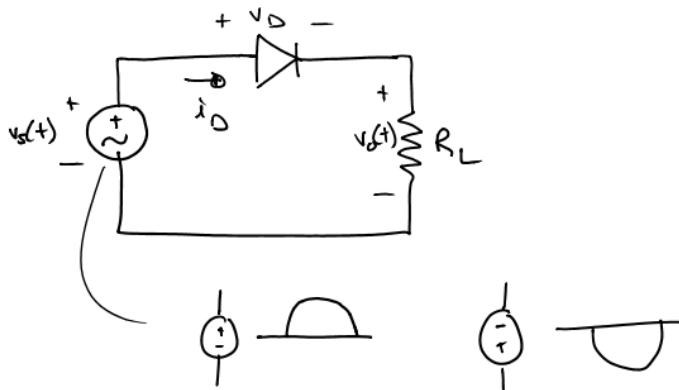

KVL

$$-v_s(t) + v_D + v_o(t) = 0$$

$$\boxed{-v_s(t) + v_D + i_D R_L = 0}$$


If $v_s > 0$ Diode \Rightarrow ON

$$\boxed{i_D = \frac{v_s(t)}{R_L}}$$


$$v_o(t) = i_D R_L = \left(\frac{v_s(t)}{R_L}\right) (R_L)$$

$$\boxed{v_o(t) = v_s(t)}$$

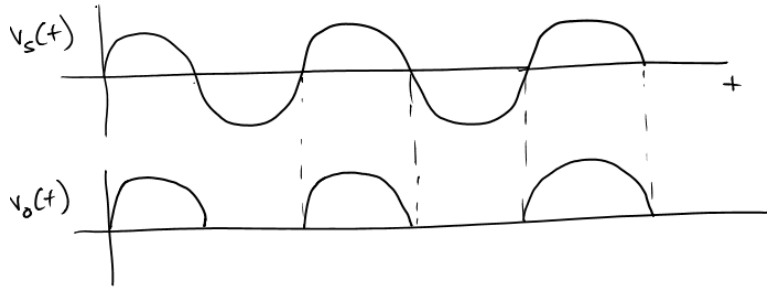
If $v_s < 0$ Diode \Rightarrow OFF
 $i_D = 0 \Rightarrow V_o = 0$




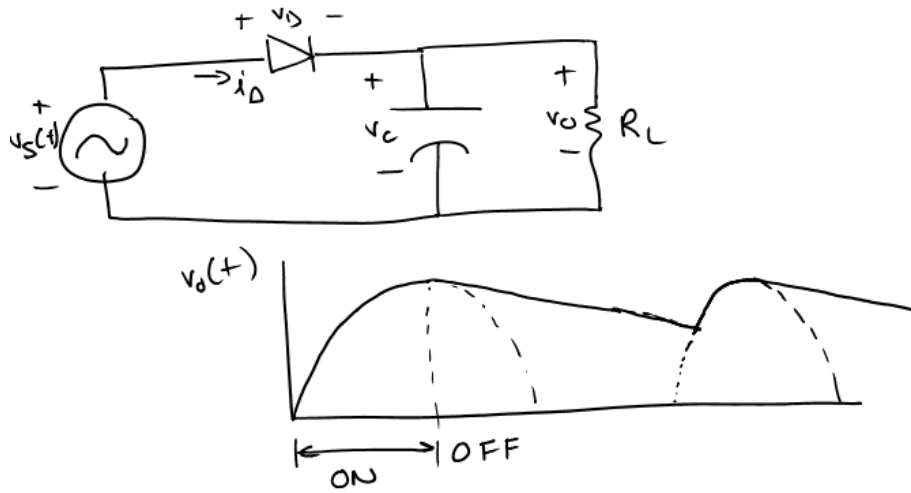- Half-Wave Rectifier with smoothing capacitor




- Full-Wave Bridge Rectifier

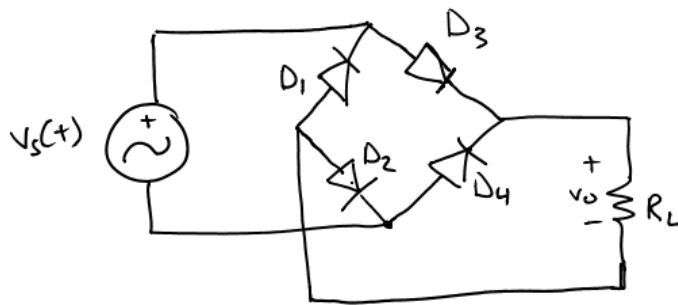

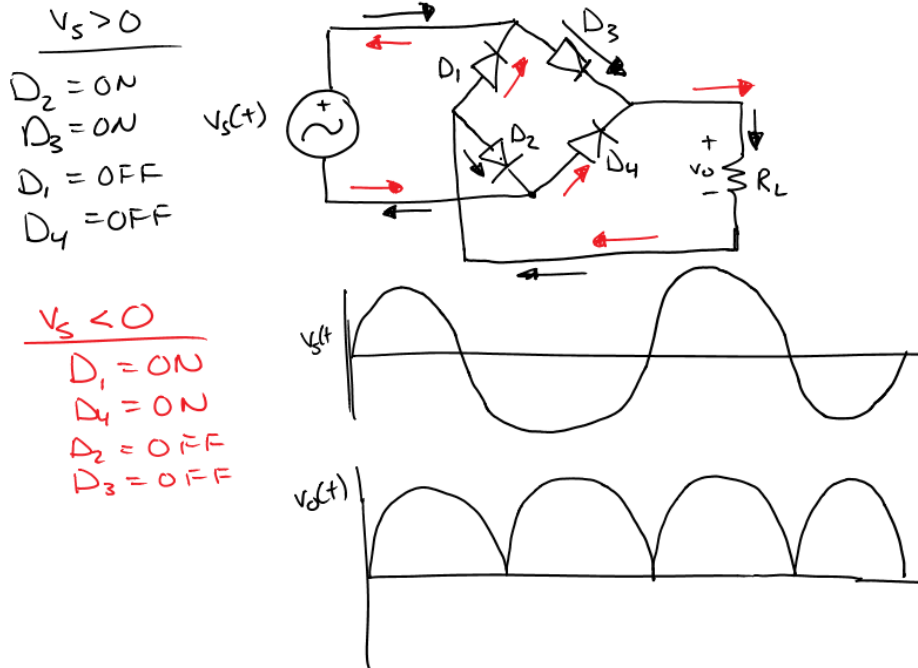



- Full-Wave Rectifier

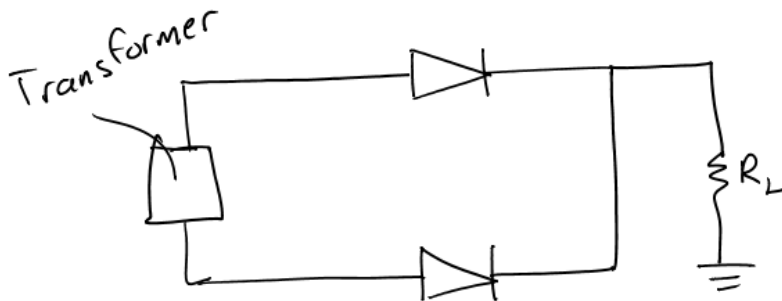

- Voltage Regulator Circuit

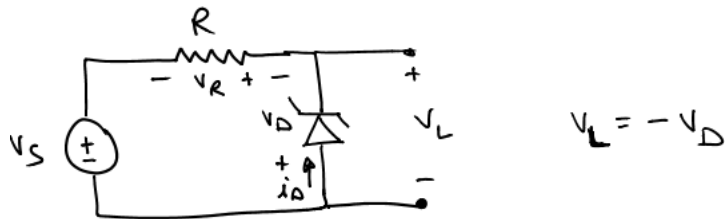- Zener diode operating in the Reverse Breakdown Region




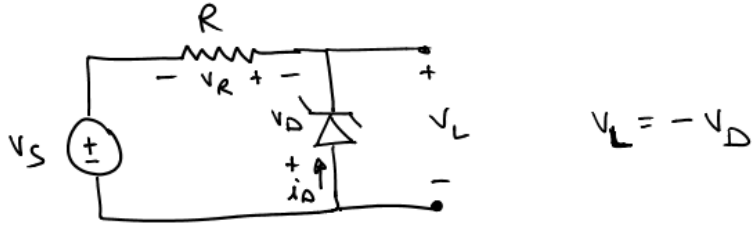

KVL (cw)

$$-v_s - i_D R - v_D = 0$$


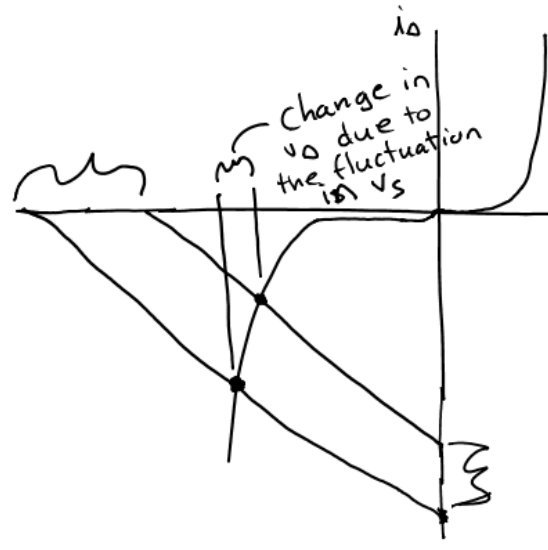
$$i_D = -\frac{1}{R} v_D - \frac{v_s}{R}$$



If v_s fluctuates, then the load line will shift

- Clipper Circuit

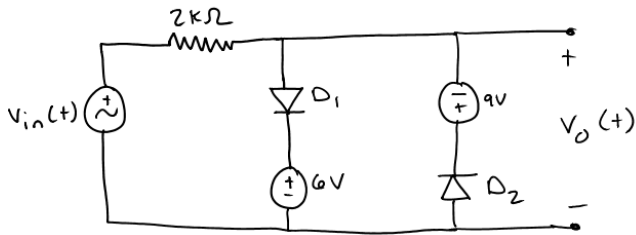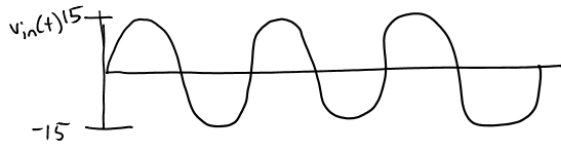
- Wave shaping circuit
- Transform one waveform into another
- A portion of the input signal is "clipped" off
- Function generators



Cases

- $-15V < v_{in} < -9V$
- $-9V < v_{in} < 6V$
- $6V < v_{in} < 15V$

$-15V < v_{in} < -9V$

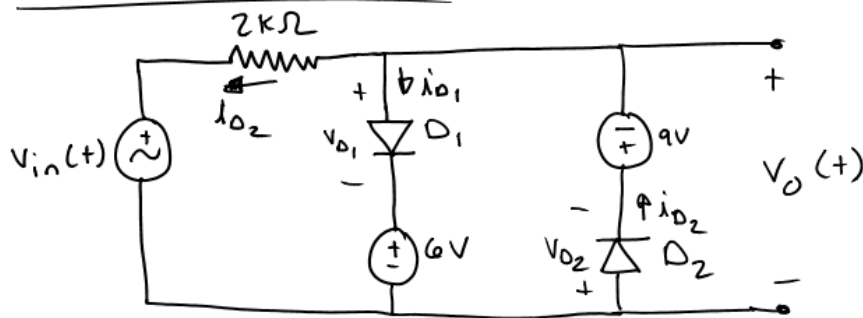

$D_1 = \text{OFF}, D_2 = \text{ON}$

$i_{D1} = 0, v_{D2} = 0$

KVL (CCW)

$$v_{in} + v_{D2} + 9V + i_{D2}(2k\Omega) = 0$$

$$i_{D_2} = \frac{-v_{in} - 9V}{2}$$

$$i_{D_2} > 0 \text{ as long as } v_{in} < -9V \checkmark$$

KVL (Middle, cw)

$$-6V - v_{D_1} - 9V = 0$$

$$v_{D_1} = -15V < 0$$


$D_1 = \text{OFF}, D_2 = \text{ON}$ for $-15V < v_{in} < -9V$

KVL (Right, cw)

$$v_{D_2}^0 + 9V + v_o = 0$$

$$v_o = -9V$$

$-9V < v_{in} < 6V$

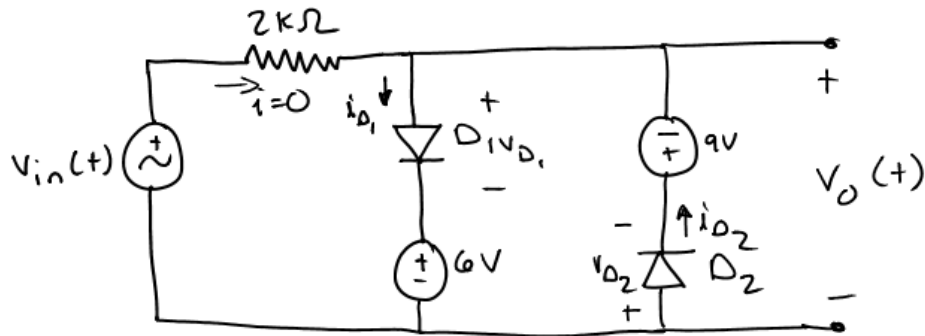

$D_1 = \text{OFF}, D_2 = \text{OFF}$

$$i_{D_1} = 0 \quad i_{D_2} = 0$$

KVL (Left, cw)

$$-v_{in} + v_{D_1} + 6V = 0$$

$$v_{D_1} = v_{in} - 6V$$

$v_{D_1} < 0$ for $v_{in} < 6V$

KVL (Left Two Loops, cw)

$$-v_{in} - 9V - v_{D_2} = 0$$

$$v_{D_2} = -v_{in} - 9V$$

$$v_{D_2} < 0 \quad \text{for } v_{in} > 9V$$


$D_1 = \text{OFF}, D_2 = \text{OFF}$

KVL (Perimeter, cw)

$$-v_{in} + v_o = 0$$

$$v_o = v_{in}$$

$6V < v_{in} < 15V$

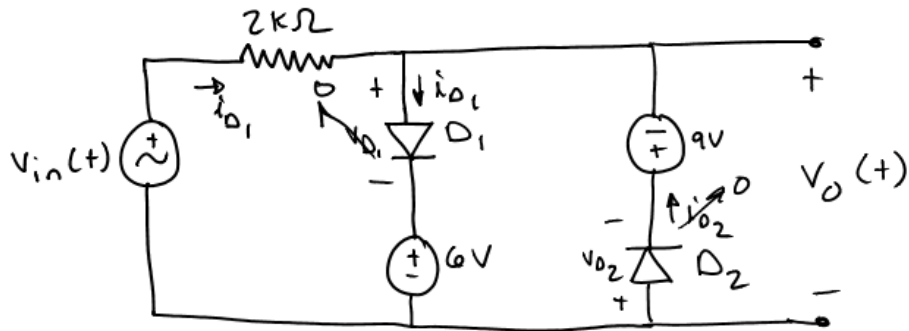

$D_1 = \text{ON}, D_2 = \text{OFF}$

$$v_{D_1} = 0 \quad i_{D_2} = 0$$

KVL (Left, cw)

$$-v_{in} + i_{D_1}(2k\Omega) + 6V = 0$$

$$i_{D_1} = \frac{v_{in} - 6V}{2}$$

$$i_{D_1} > 0 \quad \text{for } v_{in} > 6V$$

KVL (Middle, cw)

$$-6V - 9V - V_{D_2} = 0$$


$$V_{D_2} = -15V < 0 \quad \checkmark$$

$D_1 = \text{ON}, D_2 = \text{OFF}$


KVL (Right Two Loops, cw)

$$-6V + V_o = 0$$

$$V_o = 6V$$

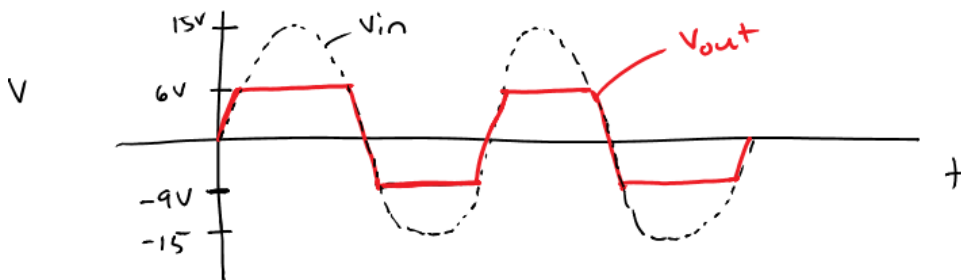


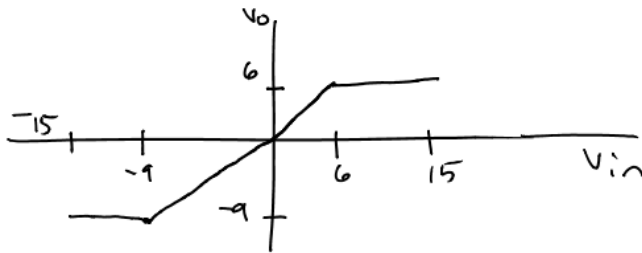- Transfer Function: Graphs output versus input



Shockley Equation

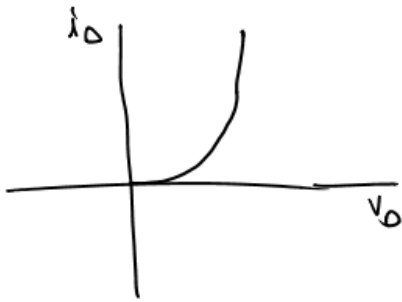- Provides the current versus voltage characteristic equation for a pn-junction (diode) in the Forward Bias Region



$$i_D = I_S \left[e^{\left(\frac{v_D}{nV_T}\right)} - 1 \right]$$

I_S = Saturation Current
in order of 10^{-14} A for small-signal
diodes at 300 K

n = Emission Coefficient
 $1 < n < 2$

V_T = Thermal Voltage

$$= \frac{kT}{q}$$

k = Boltzmann's Constant
 $= 1.38 \times 10^{-23}$ J/K

T = Temperature

q = Electron Charge
 $= 1.6 \times 10^{-19}$ Coulombs