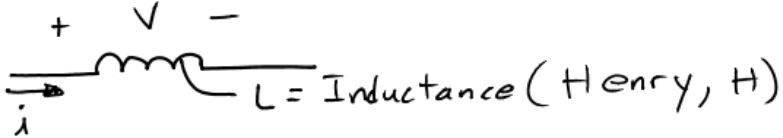


Inductors

- Oppose any change in current
- A basic inductor consists of a coil of wire wound around a magnetic or non-magnetic core
- Behavior is associated with magnetic fields




- Characteristic Equation

$$V = L \frac{di}{dt}$$

$$i \Rightarrow \text{constant} \Rightarrow \frac{di}{dt} = 0 \Rightarrow v = 0$$

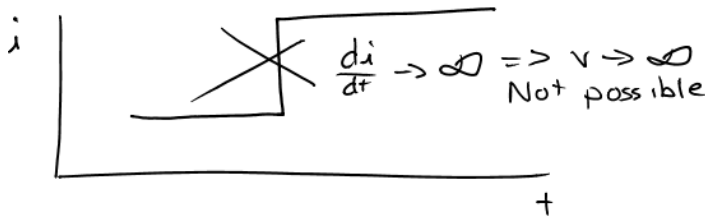- Current can't change instantaneously in an inductor



- Current in terms of voltage

$$v = L \frac{di}{dt}$$

Multiply both sides by dt

$$v dt = L di$$

Integrate both sides

$$\int_{t_0}^t v dt = \int_{i(t_0)}^{i(t)} L di$$

$$= L (i(t) - i(t_0))$$

$$i(t) = \frac{1}{L} \int_{t_0}^t v dt + i(t_0)$$

- Power

$$P = v i$$
$$P = \left(L \frac{di}{dt} \right) i$$

$$P = L i \frac{di}{dt}$$

or

$$P = v \left[\frac{1}{L} \int_{t_0}^+ v dt + i(t_0) \right]$$

- Energy

$$P = \frac{dw}{dt}$$

Energy

$$L i \frac{di}{dt}$$

$$L i \frac{di}{dt} = \frac{dw}{dt}$$


$$\int_0^i L i di = \int_0^w dw$$

$$\frac{1}{2} L i^2 = w$$

$$w = \frac{1}{2} L i^2$$

Capacitors

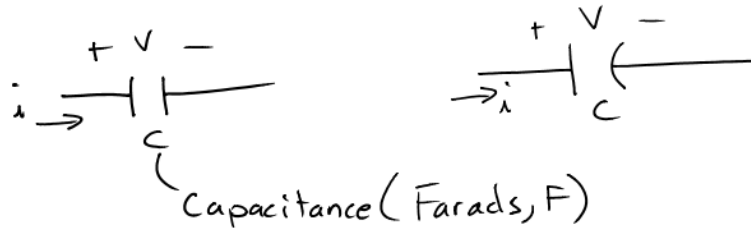- Two conductors separated by an insulator
- Behavior is associated with electric fields
- The electric field produces a displacement current
 - At the terminals of the capacitor, the displacement current is indistinguishable from the conduction current



- Characteristic Equation

$$i = C \frac{dv}{dt}$$

$$v = \text{constant} \Rightarrow \frac{dv}{dt} = 0 \Rightarrow i = 0$$

- Voltage can't change instantaneously in a capacitor

- Voltage in terms of current

$$v(t) = \frac{1}{C} \int_{t_0}^+ i dt + v(t_0)$$

- Power

$$p = vi$$

$$p = C v \frac{dv}{dt} \quad \text{or} \quad p = i \left[\frac{1}{C} \int_{t_0}^+ i dt + v(t_0) \right]$$


- Energy

$$p = \frac{dw}{dt}$$

$$w = \frac{1}{2} C v^2$$

Series and Parallel Combinations of Inductors and Capacitors


- Inductors in Series

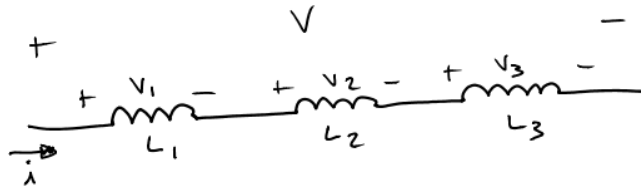

$$\begin{aligned}
 V &= v_1 + v_2 + v_3 \\
 &= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt} \\
 V &= \underbrace{(L_1 + L_2 + L_3)}_{L_{eq}} \frac{di}{dt}
 \end{aligned}$$

$$L_{eq} = \sum L_n$$

- Inductors in Parallel

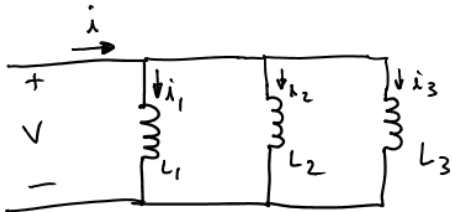


$$i = i_1 + i_2 + i_3$$

$$\begin{aligned}
 i &= \left[\frac{1}{L_1} \int v dt + i_1(t_0) \right] + \left[\frac{1}{L_2} \int v dt + i_2(t_0) \right] \\
 &\quad + \left[\frac{1}{L_3} \int v dt + i_3(t_0) \right]
 \end{aligned}$$

$$i = \underbrace{\left(\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right)}_{\frac{1}{L_{eq}}} \int v dt + \underbrace{\left[i_1(t_0) + i_2(t_0) + i_3(t_0) \right]}_{i(t_0)}$$

$$\frac{1}{L_{eq}} = \sum \frac{1}{L_n} \Rightarrow L_{eq} = \left(\sum \frac{1}{L_n} \right)^{-1}$$


- Capacitors in Series

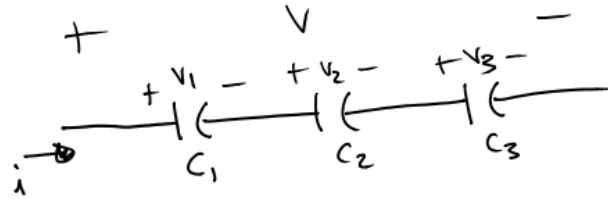

$$\begin{aligned}
 V &= v_1 + v_2 + v_3 \\
 &= \left[\frac{1}{C_1} \int i dt + v_1(t_0) \right] + \left[\frac{1}{C_2} \int i dt + v_2(t_0) \right] \\
 &\quad + \left[\frac{1}{C_3} \int i dt + v_3(t_0) \right] \\
 V &= \underbrace{\left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)}_{\frac{1}{C_{eq}}} \int i dt + \underbrace{\left[v_1(t_0) + v_2(t_0) + v_3(t_0) \right]}_{v(t_0)}
 \end{aligned}$$

$$\boxed{\frac{1}{C_{eq}} = \sum \frac{1}{C_n} \quad C_{eq} = \left(\sum \frac{1}{C_n} \right)^{-1}}$$

- Capacitors in Parallel

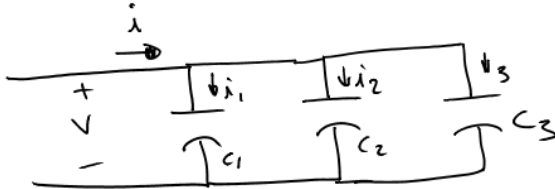

$$\boxed{C_{eq} = \sum C_n}$$