

Essential Node



- Connects three or more circuit elements

Essential Branch


- Connects two essential nodes

Node Voltage Method

- Define the essential nodes
- One of the essential nodes is selected as the reference node (Typically the reference node connects the most essential branches)
- Define the node voltages
 - Voltage between the reference node and each of the other essential nodes
 - The reference node has the negative polarity
- KCL at each reference node
 - Determine each current in terms of the node voltages using Ohm's Law

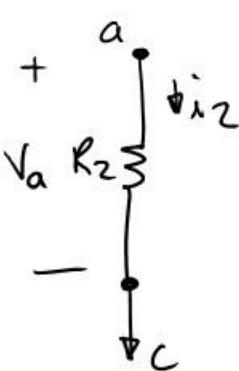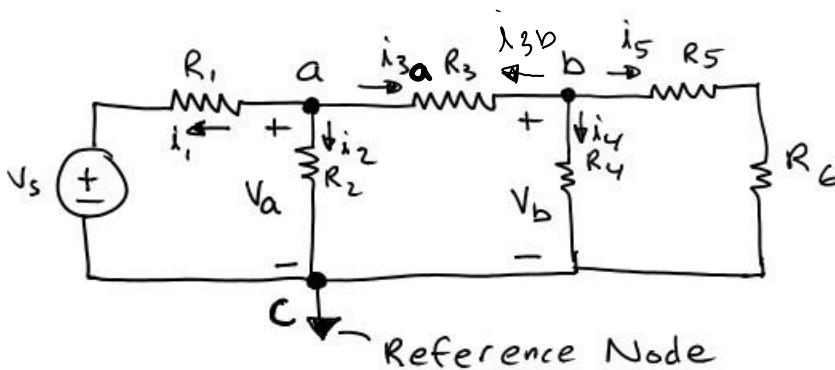


$$i_2 = \frac{v_a}{R_2}$$

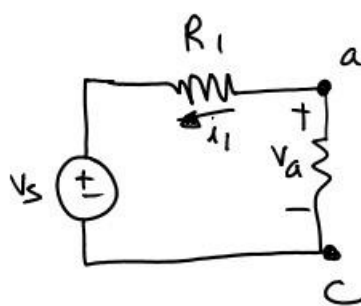

KVL (CCW)

$$i_1 R_1 + v_s - v_a = 0$$


$$i_1 = \frac{v_a - v_s}{R_1}$$

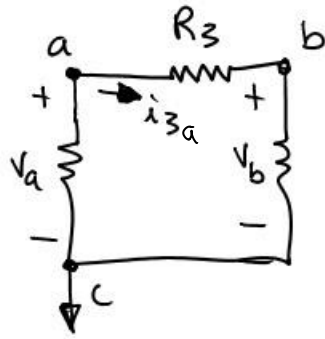


KVL (cw)
 $i_{3a}R_3 + V_b - V_a = 0$

$$i_{3a} = \frac{V_a - V_b}{R_3}$$
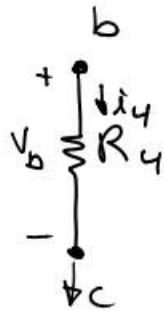
$$i_{3b} = -i_{3a} = \frac{V_b - V_a}{R_3}$$



$$i_4 = \frac{V_b}{R_4}$$

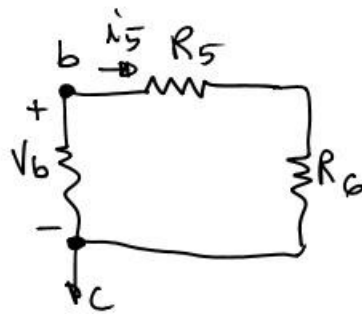

$$i_5 = \frac{V_b}{R_5 + R_6}$$

KCL
a

$$i_1 + i_2 + i_{3a} = 0$$


$$\frac{V_a - V_s}{R_1} + \frac{V_a}{R_2} + \frac{V_a - V_b}{R_3} = 0$$

b.
 $i_{3b} + i_4 + i_5 = 0$


$$\frac{V_b - V_a}{R_3} + \frac{V_b}{R_4} + \frac{V_b}{R_5 + R_6} = 0$$

Special Cases

- Current Source

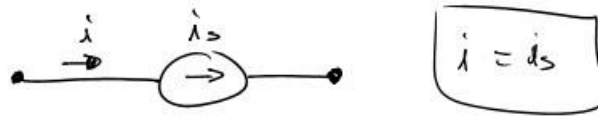


- Voltage Source

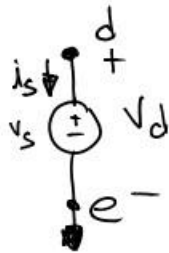

- Node voltage is known

$$v_d = v_s$$

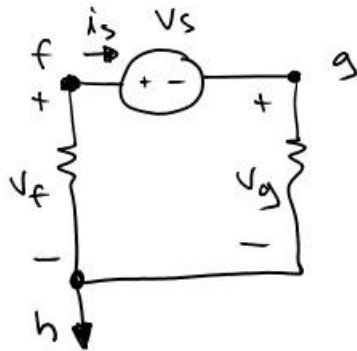- i_s can't be solved for in terms of the node voltages
 \Rightarrow includes i_s as an unknown



- i_s is added as an unknown
 - Add a constraint equation (KVL)
 KVL (cw)

$$-v_f + v_s + v_g = 0$$

OR

Create a Supernode

Combine nodes f & g into a supernode

KCL at the supernode

\Rightarrow Eliminate i_s

\Rightarrow Add a constraint equation