

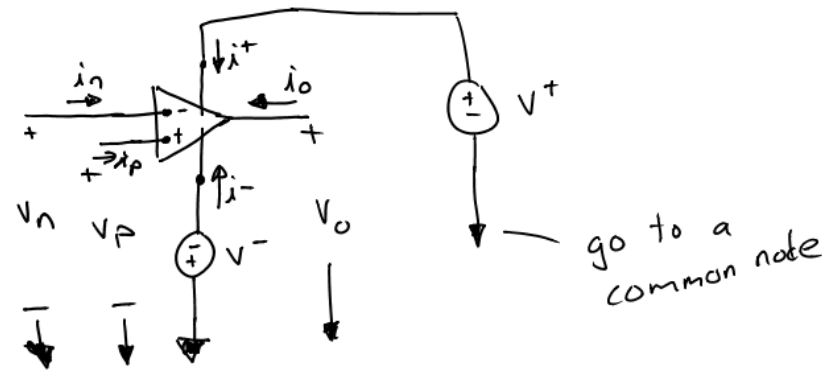
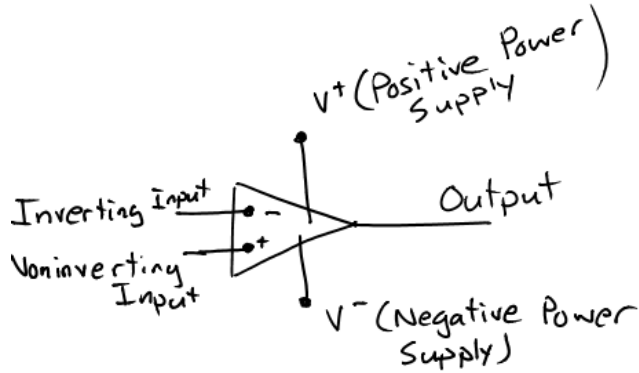


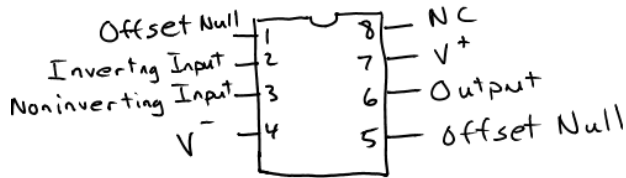**The Operational Amplifier (Op Amp)**

- Electronic Circuit
- Used for scaling, summing, sign changing, subtracting, integrating, etc.



Characteristic Equation

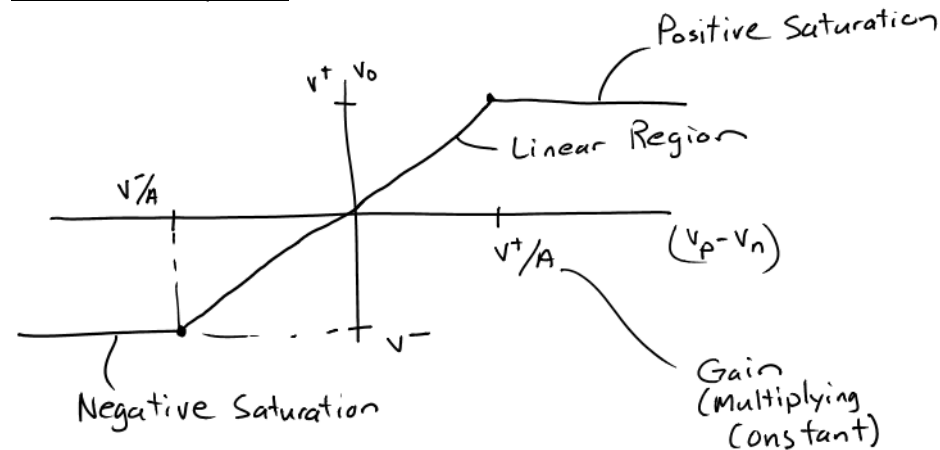

$$V_o = \begin{cases} -V^- \\ A(V_p - V_n) \\ V^+ \end{cases} \quad \begin{aligned} (V_p - V_n) &< \frac{V^-}{A} \\ \frac{-V^-}{A} &\leq V_p - V_n \leq \frac{V^+}{A} \\ V_p - V_n &> \frac{V^+}{A} \end{aligned}$$

- Typically, the magnitude of  $v^+$  and  $v^-$  is no more than 20 V, and A is more than 10,000

Linear Operating Region

$$\begin{aligned} |V_p - V_n| &\leq \left| \frac{V^+, V^-}{A} \right| \\ &\leq \frac{20V}{10,000} \\ &\leq 0.002V \\ &\Rightarrow \text{Small} \approx 0 \\ A &\rightarrow \infty \end{aligned}$$

$$V_p - V_n = 0$$


$V_p = V_n$

Ideal Op Amp

Assume 
 $i_p = i_n = 0$ 
 Ideal Op Amp

Standard Op Amp Circuits

- Inverting Amplifier

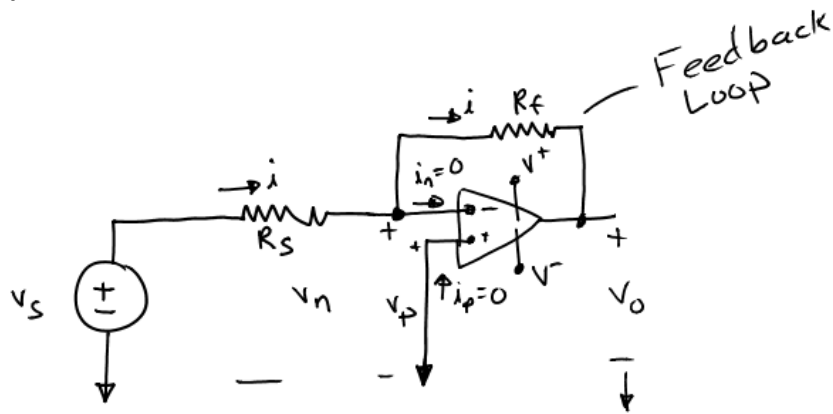

$$v_p = 0 \Rightarrow v_n = v_p = 0$$

KVL (Left, cw)

$$-v_s + i R_s + v_n = 0 \Rightarrow i = \frac{v_s - v_n}{R_s}$$

KVL (Perimeter)

$$-v_n + i R_f + v_o = 0$$


$$\left(\frac{v_s}{R_s}\right) R_f + v_o = 0$$

$$v_o = -\frac{R_f}{R_s} v_s$$

Also must check for saturation

$$-V^- \leq v_o \leq V^+$$

- Summing Amplifier

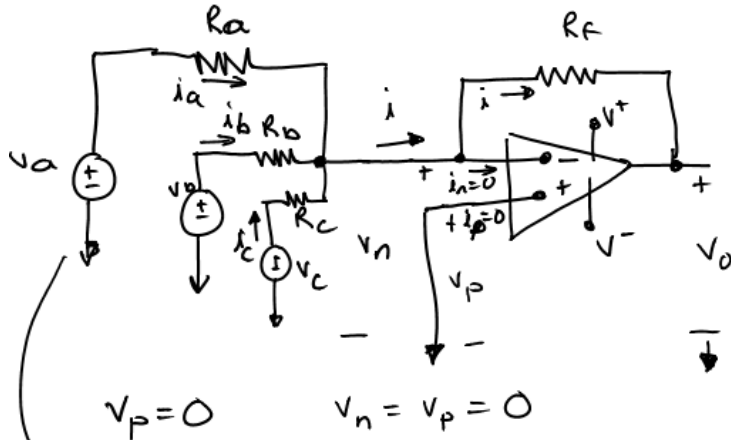

$$i = i_a + i_b + i_c$$

$$V_p = 0 \quad V_n = V_p = 0$$

KVL

$$-V_a + i_a R_a + V_n = 0$$

$$i_a = \frac{V_a}{R_a}$$

Similarly,  $i_b = \frac{V_b}{R_b}$

$$i_c = \frac{V_c}{R_c}$$

$$i = \frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c}$$

KVL (Perimeter, cw)


$$-V_n + i R_f + V_o = 0$$

$$\left( \frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} \right) R_f + V_o = 0$$

$$V_o = - \left( \frac{R_f}{R_a} V_a + \frac{R_f}{R_b} V_b + \frac{R_f}{R_c} V_c \right)$$

Check for saturation

- Noninverting Amplifier

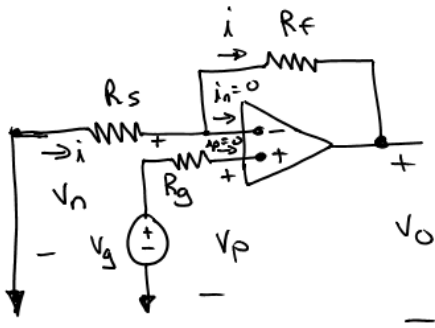

$$v_p = v_g \Rightarrow v_n = v_g$$

KVL (Left, cw)

$$i R_s + v_n - v_g = 0$$

$$i = -\frac{v_g}{R_s}$$

KVL (Perimeter, cw)

$$-v_n + i(R_f) + v_o = 0$$

$$-v_g + \left(\frac{-v_g}{R_s}\right)R_f + v_o = 0$$


$$v_o = v_g \left(1 + \frac{R_f}{R_s}\right)$$

$$v_o = v_g \left(\frac{R_f + R_s}{R_s}\right)$$

$$v_o = \left(\frac{R_s + R_f}{R_s}\right) v_g$$

Check for saturation

- Difference Amplifier

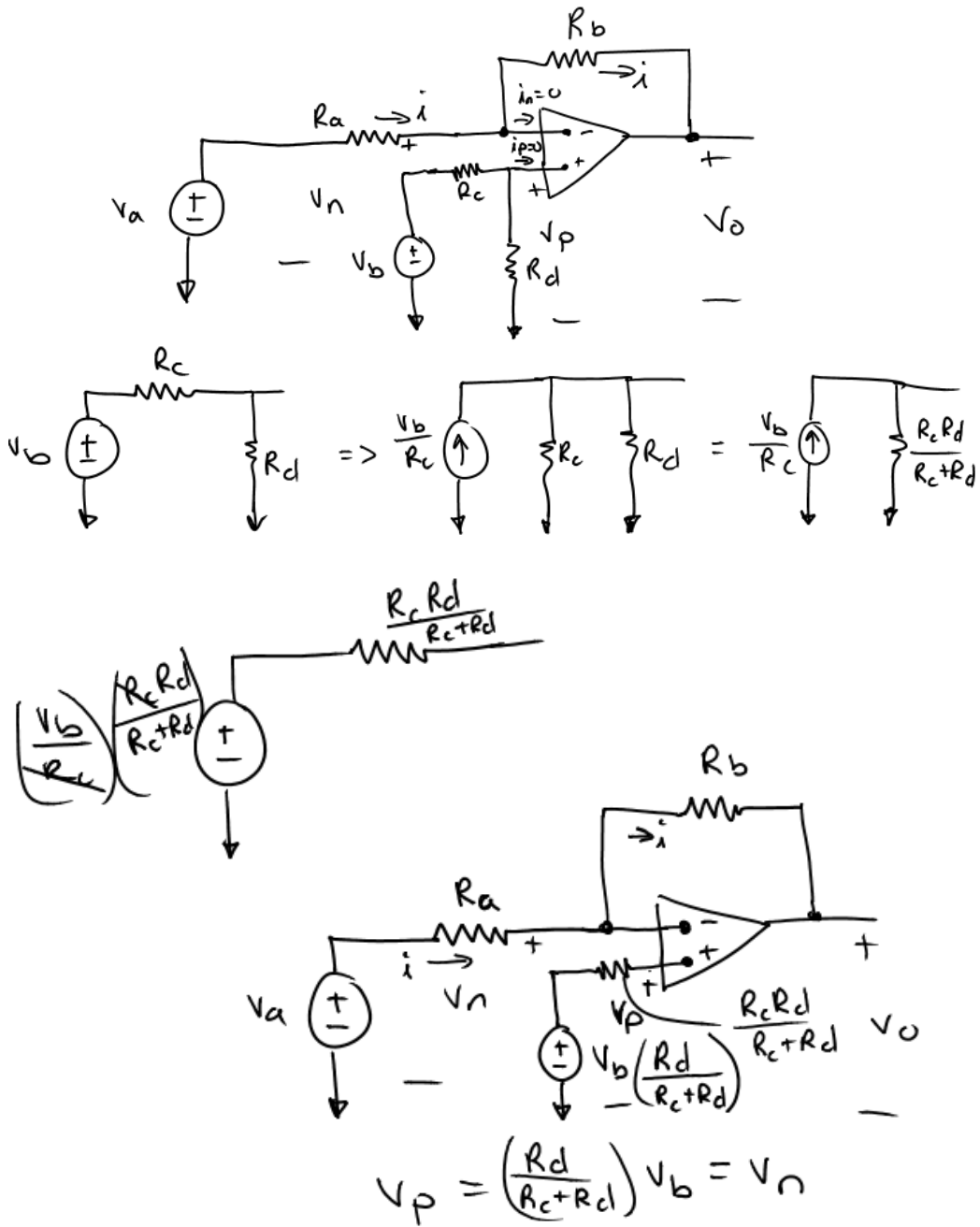

KVL (Left, cw)

$$-v_a + i R_a + v_n = 0$$

$$i = \frac{v_a - \left(\frac{R_d}{R_c + R_d}\right)v_b}{R_a}$$

KVL (Perimeter, cw)

$$-v_n + i(R_b) + v_o = 0$$
$$\left(\frac{R_d}{R_c + R_d}\right)v_b \left( \frac{v_a - \left(\frac{R_d}{R_c + R_d}\right)v_b}{R_a} \right)$$

ASA


$$v_o = \frac{R_d(R_a + R_b)}{R_a(R_c + R_d)}v_b - \frac{R_b}{R_a}v_a$$

If  $\frac{R_a}{R_b} = \frac{R_c}{R_d}$


$$v_o = \frac{R_b}{R_a}(v_b - v_a)$$

Check for Saturation

A More Realistic Op Amp Model

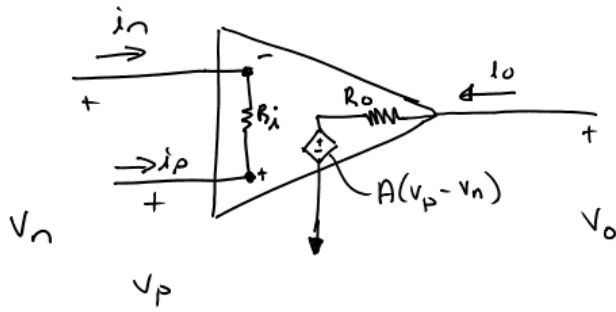

- For the Inverting Amplifier

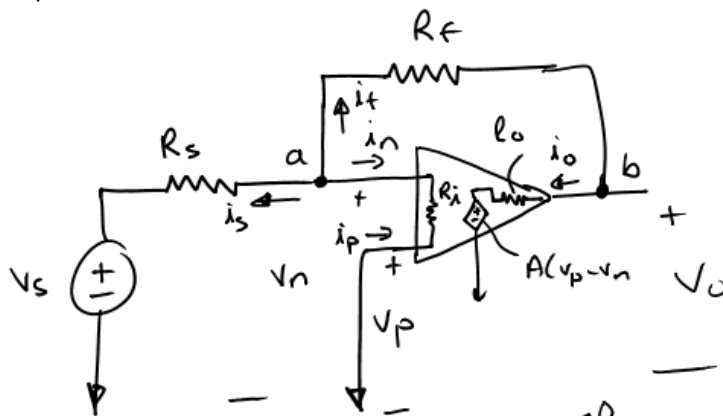

$$i_s = \frac{V_n - V_s}{R_s}$$

$$i_f = \frac{V_n - V_o}{R_f}$$

$$i_n = \frac{V_n - V_p}{R_i}$$

$$i_o = \frac{V_o - A(V_p - V_n)}{R_o}$$

a  $i_s + i_f + i_n = 0$

$$\frac{V_n - V_s}{R_s} + \frac{V_n - V_o}{R_f} + \frac{V_n}{R_i} = 0$$

b  $i_f + i_o = 0$

$$-\left(\frac{V_n - V_o}{R_f}\right) + \frac{V_o + AV_n}{R_o} = 0$$

Eliminate  $V_n$

$$V_o = \frac{-A + \frac{R_o}{R_f}}{\frac{R_s}{R_f} \left(1 + A + \frac{R_o}{R_i}\right) + \left(\frac{R_s}{R_i} + 1\right) + \frac{R_o}{R_f}} V_s$$

- To get the Ideal Op Amp Model:

$$A \rightarrow \infty, R_o \rightarrow 0, R_i \rightarrow \infty$$

$$V_o = \frac{-A}{\frac{R_s}{R_f}(1+A) + \left(\frac{R_s}{R_i} + 1\right)} v_s$$

$$= \frac{-A}{A \left[ \frac{R_s}{R_f} \left( \frac{1}{A} + 1 \right) + \frac{1}{A} \left( \frac{R_s}{R_i} + 1 \right) \right]} v_s$$

$$V_o = \frac{-1}{\frac{R_s}{R_f}} v_s$$

$$V_o = - \frac{R_f}{R_s} v_s$$