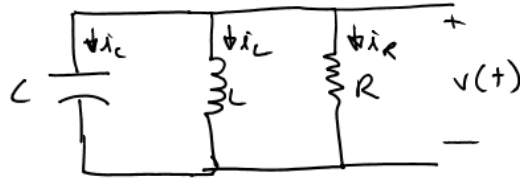


Natural Response of a Parallel RLC Circuit



KCL

$$i_C + i_L + i_R = 0$$

$$C \frac{dv}{dt} + \left(\frac{1}{L} \int_0^+ v dt + I_0 \right) + \frac{v}{R} = 0$$

Differentiate with respect to time

$$C \frac{d^2v}{dt^2} + \frac{1}{L} v + \frac{1}{R} \frac{dv}{dt} = 0$$

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{1}{LC} v = 0$$

Second Order Circuit

Guess

$$v(t) = A e^{st} \quad \text{Constants}$$

$$\frac{dv}{dt} = A s e^{st}$$

$$\frac{d^2v}{dt^2} = A s^2 e^{st}$$

$$A s^2 e^{st} + \frac{1}{RC} (A s e^{st}) + \frac{1}{LC} (A e^{st}) = 0$$

$$\underbrace{A e^{st}}_{=0} \underbrace{\left(s^2 + \frac{1}{RC} s + \frac{1}{LC} \right)}_{=0} = 0$$

→ $A=0 \Rightarrow v=0 \Rightarrow$ Trivial Solution

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0 \quad \text{(Characteristic Equation)}$$

Quadratic Formula

$$s = \frac{-\frac{1}{RC} \pm \sqrt{\left(\frac{1}{RC}\right)^2 - 4\left(\frac{1}{LC}\right)}}{2}$$

$$s = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$\alpha = \frac{1}{2RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$


Case 1: Overdamped

$$\omega_0^2 < \alpha^2 \Rightarrow \text{Two real, unique roots}$$

$$\Rightarrow \text{Overdamped}$$

$$v = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

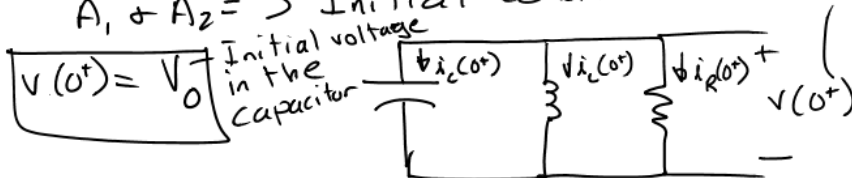A_1 & $A_2 \Rightarrow$ Initial Conditions



$$i_L(0^+) = I_0$$

$$i_R(0^+) = \frac{V_0}{R}$$

KCL

$$i_c(0^+) + i_L(0^+) + i_R(0^+) = 0$$

$$C \frac{dv(0^+)}{dt} + I_0 + \frac{V_0}{R} = 0$$

$$\boxed{\frac{dv(0^+)}{dt} = \frac{1}{C} \left(-I_0 - \frac{V_0}{R} \right)}$$

Case 2: Underdamped

$$\omega_0^2 > \alpha^2 \Rightarrow \sqrt{\text{Negative Number}}$$

$$\Rightarrow \text{Underdamped}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$= -\alpha + \sqrt{(-1)(\omega_0^2 - \alpha^2)}$$

$$= -\alpha + \underbrace{\sqrt{-1}}_{\substack{\sqrt{-1} = j \\ (\text{i in math})}} \underbrace{\sqrt{\omega_0^2 - \alpha^2}}_{\omega_d}$$

$$s_1 = -\alpha + j\omega_d \quad s_2 = -\alpha - j\omega_d$$

$$v(t) = A e^{s_1 t}$$

$$v(t) = B_1 e^{(-\alpha + j\omega_d)t} + B_2 e^{(-\alpha - j\omega_d)t}$$

Using $e^{\pm j\theta} = \cos\theta + j\sin\theta$

$$\boxed{v(t) = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t)}$$

$B_1 + B_2 \Rightarrow$ Initial Conditions

Case 3: Critically Damped

$$\omega_0^2 = \alpha^2 \Rightarrow \text{Double Root}$$
$$\Rightarrow \text{Critically Damped}$$

$$s_1 = s_2 = -\alpha$$

$$v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

D_1 & $D_2 \Rightarrow$ Initial Conditions

Note on Determining the Current in the Inductor

$$i_R(t), i_C(t), i_L(t)$$

$$i_R(t) = \frac{v(t)}{R}$$


$$i_C(t) = C \frac{dv}{dt}$$

~~$$i_L(t) = \frac{1}{L} \int_0^+ v dt + I_0$$~~

KCL $i_C(t) + i_R(t) + i_L(t) = 0$

$$i_L(t) = -i_C(t) - i_R(t)$$

Natural Response of a Series RLC Circuit

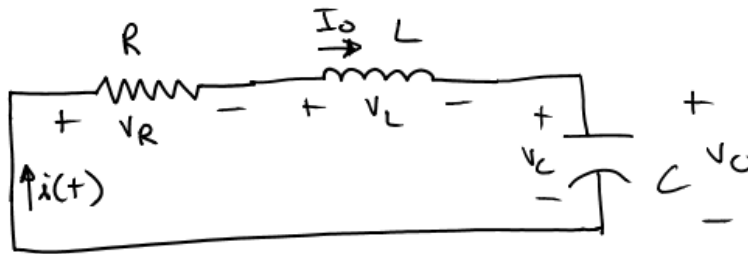

KVL

$$v_R + v_L + v_C = 0$$

$$iR + L \frac{di}{dt} + \left(\frac{1}{C} \int_0^t i dt + v_0 \right) = 0$$

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

$$s = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

Case 1: Overdamped

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Case 2: Underdamped

$$i(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

Case 3: Critically Damped

$$i(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

Solving for the Constants Using Initial Conditions

① $i(0^+) = I_0$

② KVL

$$v_R(0^+) + v_L(0^+) + v_C(0^+) = 0$$

$$I_0 R + L \frac{di(0^+)}{dt} + V_0 = 0$$

$$\boxed{\frac{di(0^+)}{dt} = \frac{1}{L} (-I_0 R - V_0)}$$

Note on Determining the Voltage in the Capacitor

$$v_R(t) = i R$$

$$v_L(t) = L \frac{di}{dt}$$

~~$$v_C(t) = \frac{1}{C} \int_0^t i dt + V_0$$~~

KVL

$$v_R(t) + v_L(t) + v_C(t) = 0$$

$$\boxed{v_C(t) = -v_R(t) - v_L(t)}$$