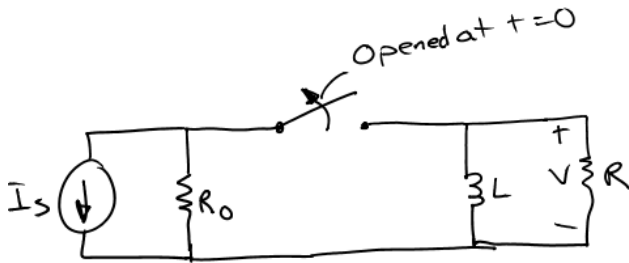


Natural Response


- Behavior is free of excitation (sources)

Natural Response of an RL Circuit



- Prior to $t = 0$

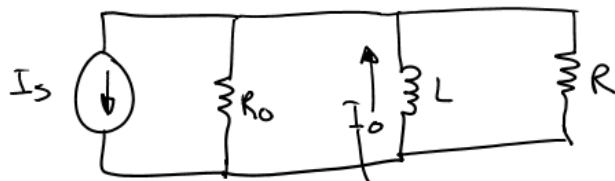- The switch has been closed for a "long" time such that all currents and voltages have reached constant values



Current in the inductor at $t=0$


Inductor \Rightarrow "long" time $\Rightarrow \frac{di}{dt} = 0 \Rightarrow v_{\text{inductor}} = 0$

$\Rightarrow R_0$ & R are in parallel with L

$v_{R_0} + v_R = 0$ before the switch is opened

$I_0 = I_s$

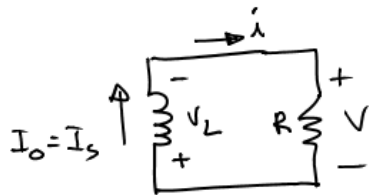- Then the switch is opened ($t = 0$ and later)



KVL

$v_L + v = 0$

$L \frac{di}{dt} + iR = 0$

$$\frac{di}{dt} = -\frac{R}{L} i$$

$$\int_{I_0}^{i(t)} \frac{di}{i} = -\int_0^t \frac{R}{L} dt$$

$$\ln(i(t)) - \ln(I_0) = -\frac{R}{L} t$$

$$\ln\left(\frac{i(t)}{I_0}\right) = -\frac{R}{L} t$$

$$\frac{i(t)}{I_0} = e^{-\frac{R}{L} t}$$

$$i(t) = I_0 e^{-\frac{R}{L} t}$$

- Time constant

$$\tau = \frac{L}{R} \quad i(t) = I_0 e^{-t/\tau}$$

- Voltage in the resistor

$$v_R = i R$$

$$v_R = I_0 R e^{-t/\tau}$$

- Voltage in the inductor

$$v_L = L \frac{di}{dt} \quad \text{or} \quad v_L + v_R = 0$$

$$v_L = -I_0 R e^{-t/\tau}$$

- Power in the resistor

$$P = i^2 R = \frac{v_R^2}{R} = v_R i$$

$$P = I_0^2 R e^{-2t/\tau}$$


- Power in the inductor

$$P_{\text{inductor}} = L i \frac{di}{dt} = v_L i$$
$$P_{\text{inductor}} = -I_0^2 R e^{-2t/\tau}$$


- Energy in the resistor

$$P = \frac{dw}{dt} \quad dw = p dt$$
$$W = \int_0^+ I_0^2 R e^{-2t/\tau} dt$$
$$W = \frac{1}{2} L I_0^2 (1 - e^{-2t/\tau})$$


Natural Response of an RC Circuit

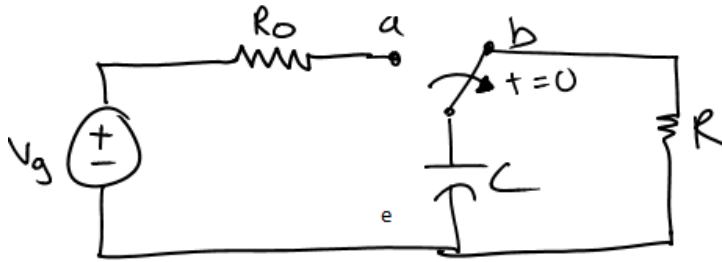

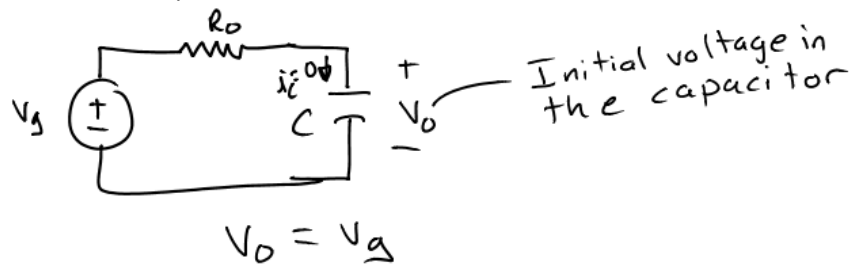- Prior to $t = 0$
 - The switch has been at position 'a' for a "long" time
 - The current in the capacitor is then zero



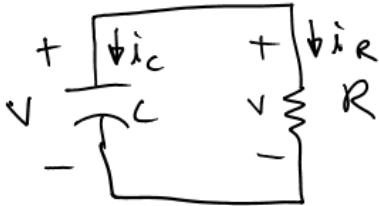- Then the switch is moved to position 'b'



$$i_c + i_R = 0$$

$$C \frac{dv}{dt} + \frac{v}{R} = 0$$

$$\int_{v_0}^v \frac{dv}{v} = \int_0^t -\frac{1}{RC} dt$$

$$v(t) = v_0 e^{-\frac{1}{RC} t}$$

$\tau = RC$ $v(t) = v_0 e^{-t/\tau}$

- Current in the resistor

$$i_R = \frac{v}{R} = \frac{V_0}{R} e^{-t/\tau}$$

- Current in the capacitor

$$i_C = -i_R = C \frac{dv}{dt}$$
$$i_C = -\frac{V_0}{R} e^{-t/\tau}$$

- Power in the resistor

$$P_R = i^2 R = \frac{v^2}{R} = v i$$
$$P_R = \frac{V_0^2}{R} e^{-2t/\tau}$$

- Power in the capacitor

$$P_C = -P_R = -\frac{V_0^2}{R} e^{-2t/\tau}$$

- Energy in the resistor

$$w_R = \int_0^t P dt$$
$$w_R(t) = \frac{1}{2} C V_0^2 (1 - e^{-2t/\tau})$$


- Energy in the capacitor

$$w_C(t) = \frac{1}{2} C V^2$$
$$w_C(t) = \frac{1}{2} C V_0^2 e^{-2t/\tau}$$

Step Response

- A DC voltage or current source is connected


Step Response of an RL Circuit

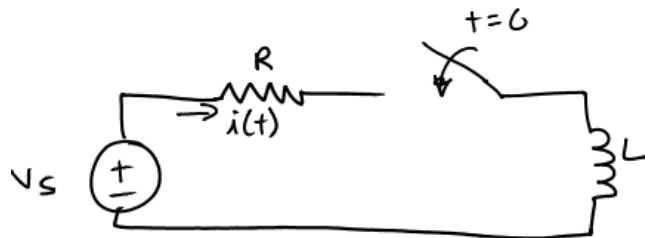

Initial Current in the inductor = I_0
 Long time (opened) $\Rightarrow I_0 = 0$

$$i(t) = \frac{v_s}{R} + \left(I_0 - \frac{v_s}{R} \right) e^{-t/\tau} \quad \tau = \frac{L}{R}$$

Step Response of an RC Circuit

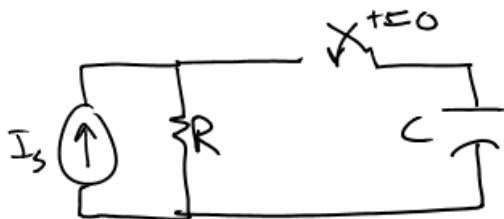

Initial Voltage in the capacitor = V_0

$$v(t) = I_s R + (V_0 - I_s R) e^{-t/\tau} \quad \tau = RC$$

General Solution for Both Step and Natural Responses of RL and RC Circuits

$$x(t) = x_f + (x(t_0) - x_f) e^{-(t-t_0)/\tau}$$

$x_f \Rightarrow$ Final value of x
 $x(t_0) \Rightarrow$ Initial value of x
 $t_0 \Rightarrow$ Initial time