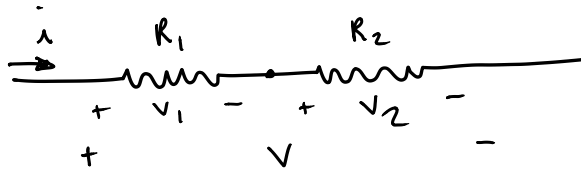


### Equivalent Resistive Circuit

- Start with a network of resistors, and end with a single equivalent circuit

#### Resistors in Series

- Have the same current




$$V = V_1 + V_2$$

$$V = iR_1 + iR_2$$

$$V = i \underbrace{(R_1 + R_2)}_{R_{eq}}$$

$$V = iR_{eq}$$

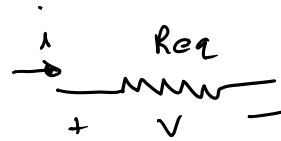


In General:

$$R_{eq} = \sum R$$

#### Resistors in Parallel

- Have the same voltage

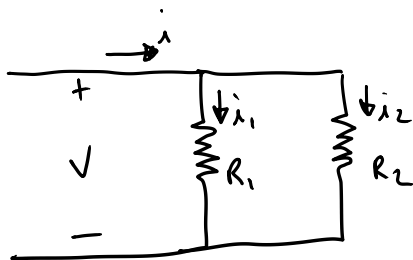

$$\text{KCL}$$

$$-i + i_1 + i_2 = 0$$


$$i = i_1 + i_2$$

$$\bar{i} = \bar{i}_1 + \bar{i}_2 \quad v = \bar{i} R \Rightarrow \bar{i} = \frac{v}{R}$$

$$\bar{i} = \frac{v}{R_1} + \frac{v}{R_2}$$

$$\bar{i} = v \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$
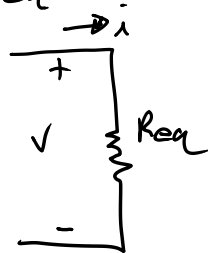
$$v = \bar{i} \underbrace{\left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}}_{R_{eq}}$$



In General:


$$R_{eq} = \left[ \bar{Z} \left( \frac{1}{R} \right) \right]^{-1} \quad \text{or} \quad \frac{1}{R_{eq}} = \bar{Z} \frac{1}{R}$$

For Two Resistors:

$$\begin{aligned} R_{eq} &= \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} \\ &= \left( \frac{R_2}{R_1 R_2} + \frac{R_1}{R_1 R_2} \right)^{-1} \\ &= \left( \frac{R_1 + R_2}{R_1 R_2} \right)^{-1} \end{aligned}$$

$$\boxed{R_{eq} = \frac{R_1 R_2}{R_1 + R_2}}$$

Voltage-Divider Circuit

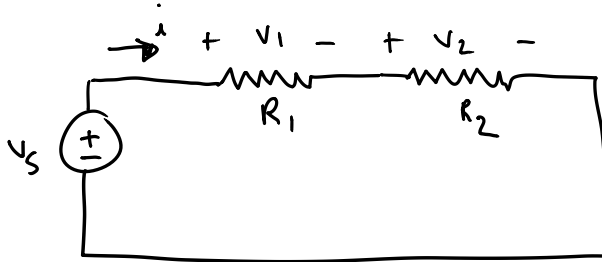

KVL (CW)

$$-v_s + v_1 + v_2 = 0$$

$$-v_s + iR_1 + iR_2 = 0$$

$$-v_s + i(R_1 + R_2) = 0$$

$$i = \frac{v_s}{R_1 + R_2}$$


$$v_1 = iR_1 = \left( \frac{v_s}{R_1 + R_2} \right) R_1$$

$$v_1 = \left( \frac{R_1}{R_1 + R_2} \right) v_s$$

$$v_2 = iR_2 = \left( \frac{v_s}{R_1 + R_2} \right) R_2$$

$$v_2 = \left( \frac{R_2}{R_1 + R_2} \right) v_s$$

Current-Divider Circuit

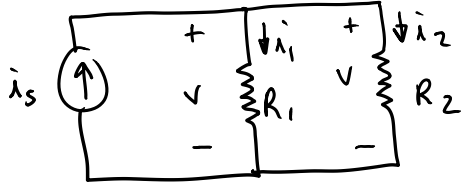

KCL

$$-i_s + i_1 + i_2 = 0$$

$$i_s = i_1 + i_2$$

$$i_s = \frac{V}{R_1} + \frac{V}{R_2}$$

$$i_s = V \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$V = \left[ \frac{1}{R_1} + \frac{1}{R_2} \right]^{-1} i_s$$

$$V = \left( \frac{R_1 R_2}{R_1 + R_2} \right) i_s$$

$$i_1 = \frac{V}{R_1} = \left( \frac{R_1 R_2}{R_1 + R_2} \right) i_s \left( \frac{1}{R_1} \right)$$

$$\boxed{i_1 = \frac{R_2}{R_1 + R_2} i_s}$$

$$i_2 = \frac{V}{R_2} = \left( \frac{R_1 R_2}{R_1 + R_2} \right) i_s \left( \frac{1}{R_2} \right)$$

$$\boxed{i_2 = \frac{R_1}{R_1 + R_2} i_s}$$