
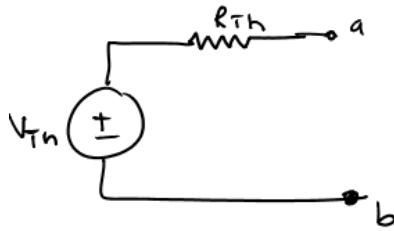


Thevenin Equivalent

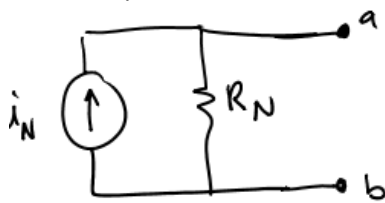

- If you add a resistor between terminals a and b, the voltage across and the current between the terminals will be the same as the original circuit

Norton Equivalent



The most efficient method for determining the Thevenin and/or Norton Equivalents is using source transformations